




Electronic Systems Simulators محاكيات الانظمة الالكترونية BY –KERIM .D.A

INTRODUCTION

The logic gates (AND, OR, NAND, NOR, INVERT) used in **combinational logic**. we will deal with data storage circuitry that will **latch** on to (remember) a digital state (1 or 0).

 This new type of digital circuitry is called **sequential logic**



because it is controlled by and used for controlling other circuitry in a specific sequence dictated by a control clock or enable/disable control signals.

The simplest form of data storage is the **Set–Reset (S-R)** flip-flop.

The types of logic circuit

1- **Synchronous** ...one of the inputs is clock ...no change in output without (**CLK**) pulses.

2- **ASynchronous** ...No clock pulses in inputs ...
output change dependent to inputs pulses.

S-R Flip-Flop

The **S-R flip-flop** is a data storage circuit that can be constructed using the basic gates Using a cross-coupling scheme with two NOR gates, we can form the flip-flop shown in Figure 1.



Electronic Systems Simulators محاكيات الانظمة الالكترونية

BY –KERIM .D.A

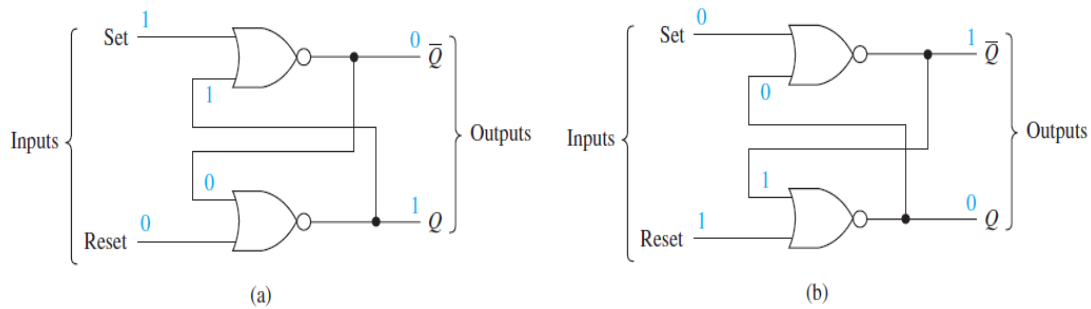


Figure 1 Cross-NOR S-R flip-flop: (a) Set condition; (b) Reset condition.

TABLE 1		Function Table for Figure 1-1		
<i>S</i>	<i>R</i>	<i>Q</i>	\bar{Q}	Comments
(b) 0	0	<i>Q</i>	\bar{Q}	<i>Hold</i> condition (no change)
(a) 1	0	1	0	Flip-flop Set
(c) 0	1	0	1	Flip-flop Reset
1	1	0	0	Not used

1-(case a) when $S=1$, and $R=0$. then $Q=1$, and $\bar{Q}=0$

If we change only ($S=0$), and still $R=0$, IT IS


CALLED NO CHANGE (CASE b)

2-(case c) when $S=0$, and $R=1$. then $Q=0$, and $\bar{Q}=1$

If we change only ($R=0$), and still $S=0$, IT IS

CALLED NO CHANGE (CASE b)

$Q=0$, and $\bar{Q}=1$

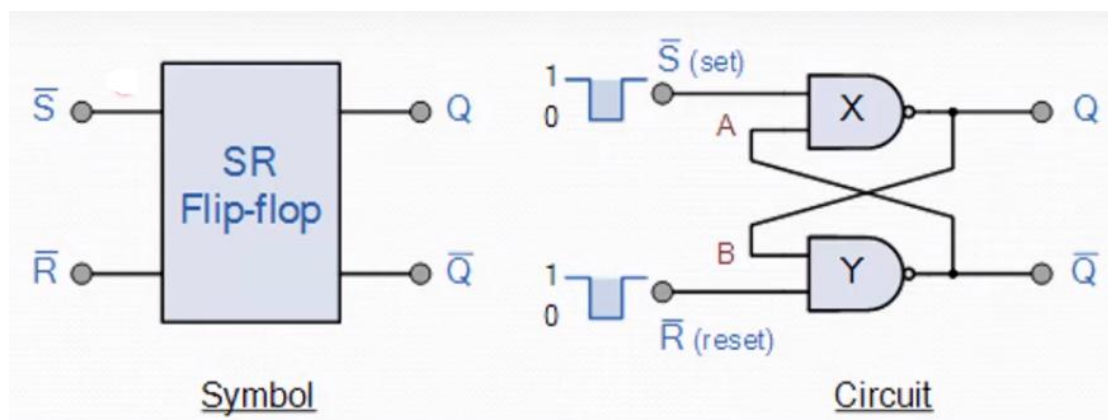


Electronic Systems Simulators محاكيات الانظمة الالكترونية

BY –KERIM .D.A

Figure–2 Cross-NAND S-R flip-flop.

State	S	R	Q	\bar{Q}	Description
Set	1	0	0	1	Set $\bar{Q} \gg 1$
	1	1	0	1	no change
Reset	0	1	1	0	Reset $\bar{Q} \gg 0$
	1	1	1	0	no change
Invalid	0	0	1	1	Invalid Condition

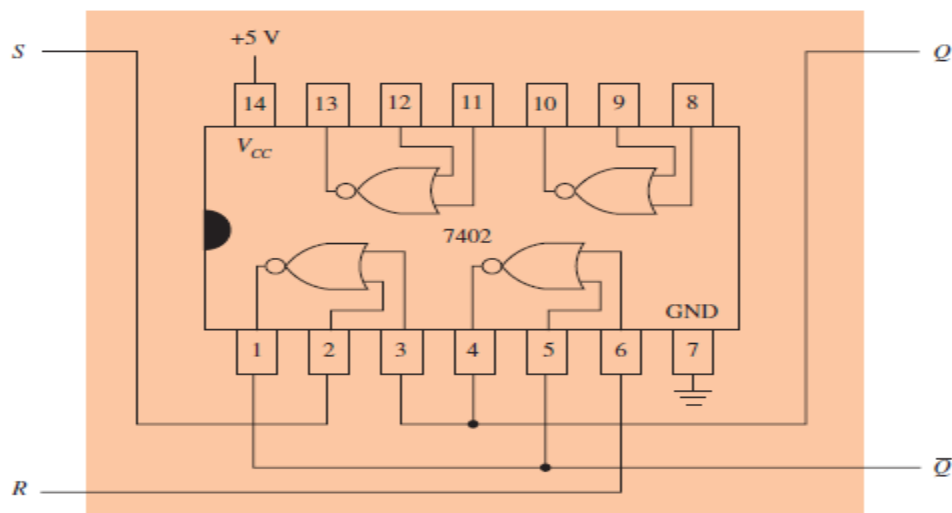

S-R flip-flop connections using a 7402 TTL IC.


EXAMPLE-1

To the S-R flip-flop shown in Figure, we connect the S and R waveforms given in Figure. Sketch the Q output waveform that will result.

Electronic Systems Simulators محاكيات الانظمة الالكترونية


BY –KERIM .D.A

Solution:

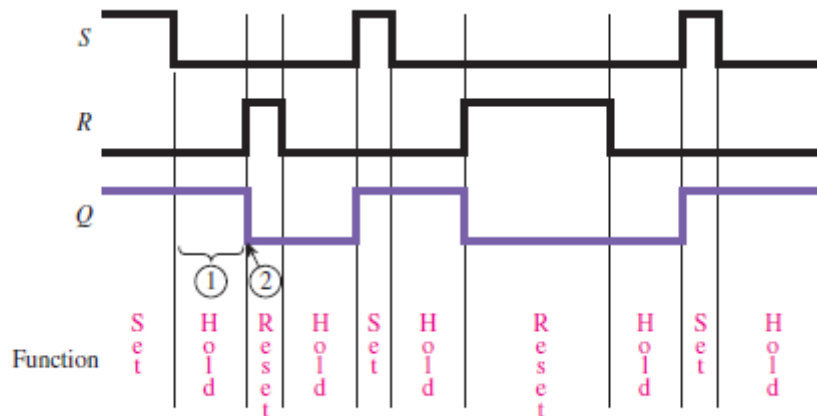

Notes:

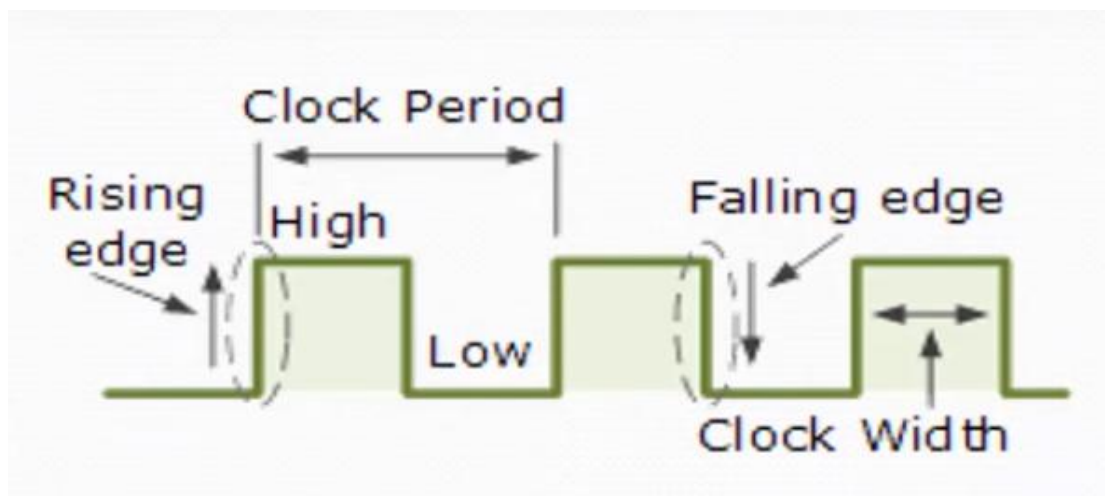1. The flip-flop is latched (held) in the Set condition even after the HIGH is removed from the S input.
2. The flip-flop is considered transparent because the Q output responds immediately to input changes.






Electronic Systems Simulators محاكيات الانظمة الالكترونية

BY -KERIM .D.A


Switching diagram



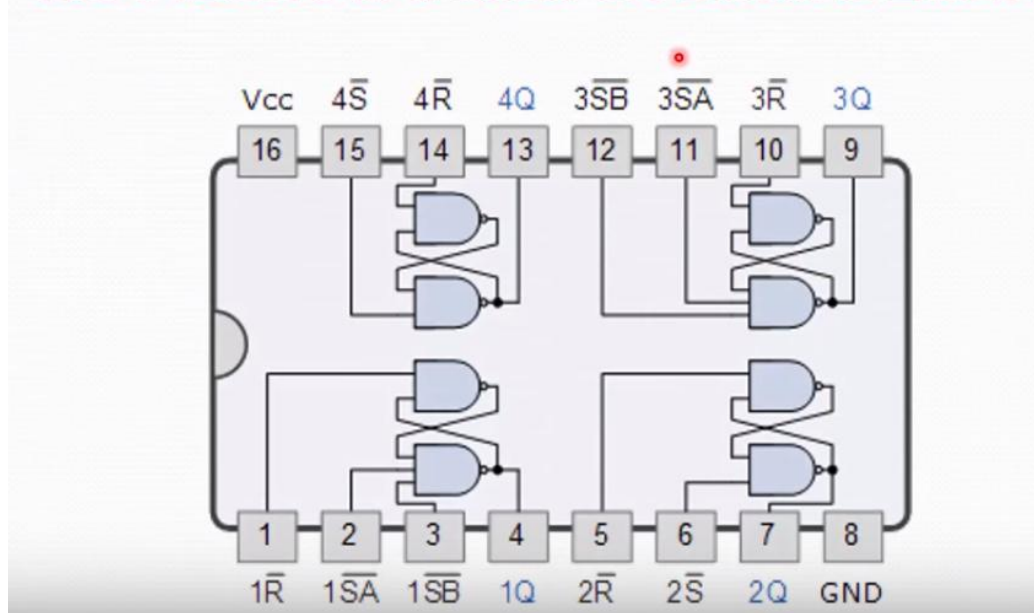The 74LS279 is a Quad SR Bistable Latch I



Gated SR Flip-flop

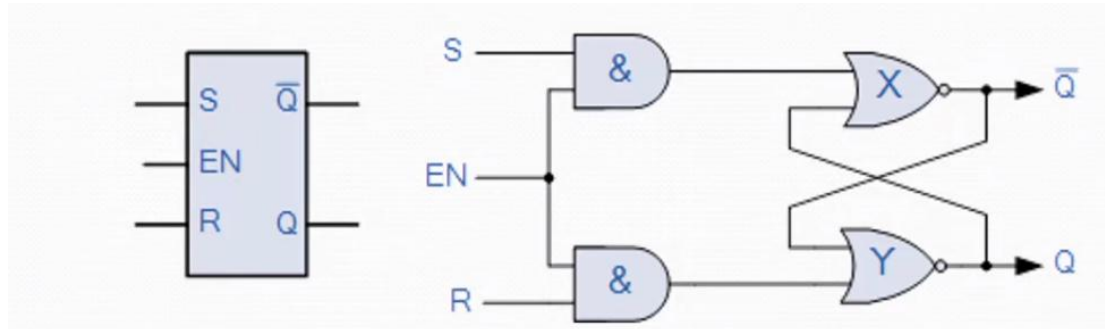

IF enable(EN=1) IT will be ACTIVE

EN=0 not active

To read switching diagram

1-when $S=0$, $R=0$, $CLK=0$, ...then $Q=0$

2- when $S=1$, $R=0$, $CLK=1$, ...then $Q=1$still to another clk pulls

3- when $S=0$, $R=1$, $CLK=0$, ...then $Q=1$...for the same pulls clk in 2

4-when the new CLK pulls come and when $S=0$, $R=1$

$CLK=1$,...then $Q=0$

5- when the new CLK pulls come and when $S=1$, $R=0$

$CLK=1$,...then $Q=1$

6- when the new CLK pulls come and continues then

When change S OR R changing Q ...if $S=1$, $R=0$, $Q=1$

And if $S=0$, $R=1$, $Q=0$


EXAMPLE -2

Feed the EN, S, and R inputs in Figure into the gated S-R flip-flop sketch the output wave at Q, and list the flip-flop functions.




Electronic Systems Simulators محاكيات الانظمة الالكترونية

BY –KERIM .D.A

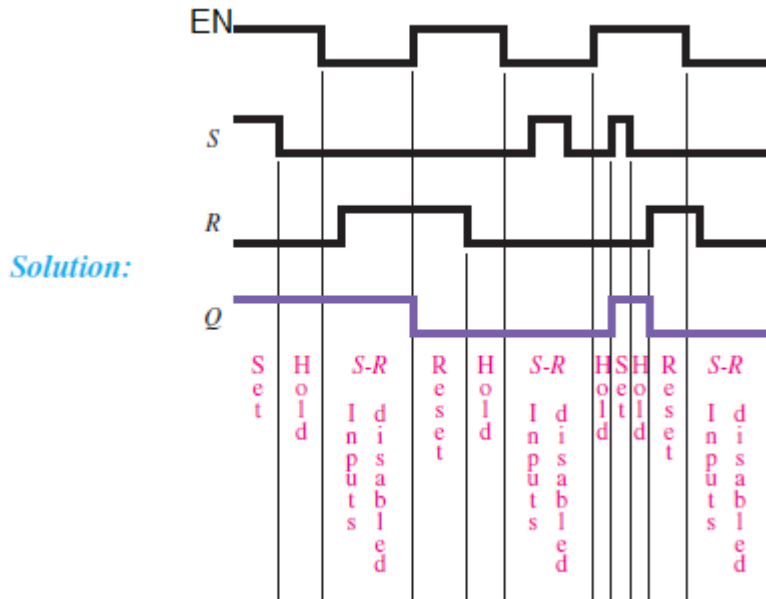

 EXAMPLE-3


Feed the EN , S , and R inputs in Figure into the gated S - R flip-flop, and sketch the output wave at Q .






Electronic Systems Simulators محاكيات الانظمة الالكترونية

BY –KERIM .D.A

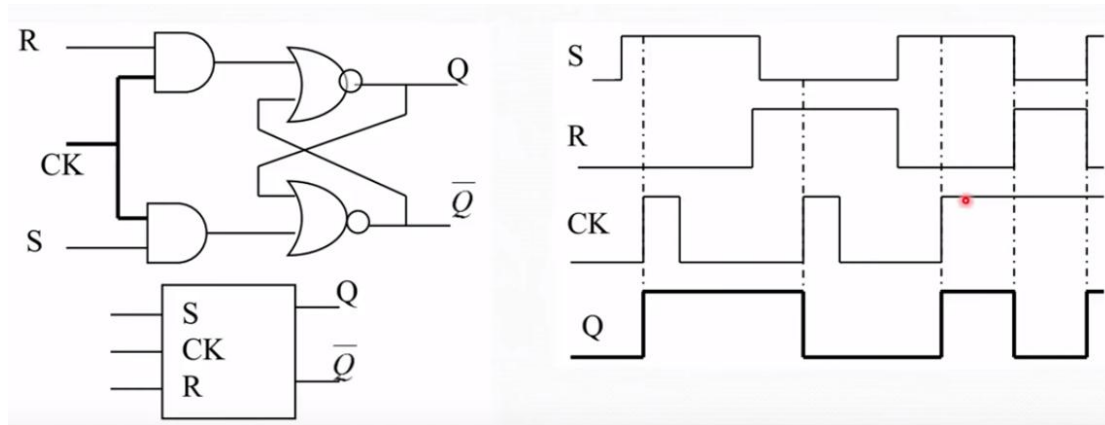

 EXAMPLE-4

Determine the Q output waveform if the inputs shown in Figure are applied to a gated S-R latch that is initially RESET.





D-FLIP-FLOP

D Flip-flop

Data Latch
Delay flip-flop

 


FIGURE Operation of a positive edge-triggered D flip-flop.

TABLE

Truth table for a positive edge-triggered D flip-flop.

Inputs		Outputs		Comments
D	CLK	Q	\bar{Q}	
0	↑	0	1	RESET
1	↑	1	0	SET

↑ = clock transition LOW to HIGH


EXAMPLE -5

Determine the Q and \bar{Q} output waveforms of the flip-flop for the D and CLK inputs in Figure Assume that the positive edge-triggered flip-flop is initially RESET.




Electronic Systems Simulators محاكيات الانظمة الالكترونية

BY –KERIM .D.A

 

 EXAMPLE-6

Given the waveforms in Figure for the D input and the clock, determine the Q output waveform if the flip-flop starts out RESET.




Gated D Flip-Flop

Another type of flip-flop is the D flip-flop (Data flip-flop). It can be formed from the gated S-R flip-flop by the addition of an inverter. This enables just a single input (D) to both Set and Reset the flip-flop. In Figure, we see that S and R will be complements of each other, and S is connected to a single line labeled D (Data). The operation is such that Q will be the same as D while G is HIGH, and Q will remain latched when G goes LOW. (Latched means that Q remains constant regardless of changes in D .)



Electronic Systems Simulators محاكيات الانظمة الالكترونية


BY –KERIM .D.A

 

Gated D flip-flop.

 EXAMPLE-7



Sketch the output waveform at Q for the inputs at D and G of the gated D flip-flop in Figure.





Electronic Systems Simulators محاكيات الانظمة الالكترونية

BY –KERIM .D.A

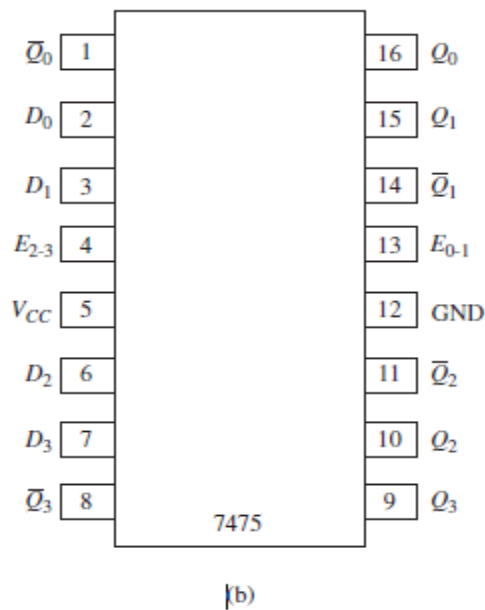 

The 7475 quad bistable D latch: (a) logic symbol; (b) pin configuration.

Operating Mode	Inputs		Outputs	
	E	D	Q	\bar{Q}
Data enabled	H	L	L	H
Data enabled	H	H	H	L
Data latched	L	x	q	\bar{q}

^a q = state of Q before the HIGH-to-LOW edge of E ; x = don't care.



EXAMPLE-8

For the inputs at D_0 and $E_0 - 1$ for the 7475 D latch shown in Figure sketch the output waveform at Q_0 in Figure




Electronic Systems Simulators محاكيات الانظمة الالكترونية

BY –KERIM .D.A

 
 


 EXAMPLE-9 Determine the Q output waveform if the inputs shown in Figure are applied to a gated D latch, which is initially RESET.






  Electronic Systems Simulators محاكيات الانظمة الالكترونية
 BY –KERIM .D.A




Rising Edge

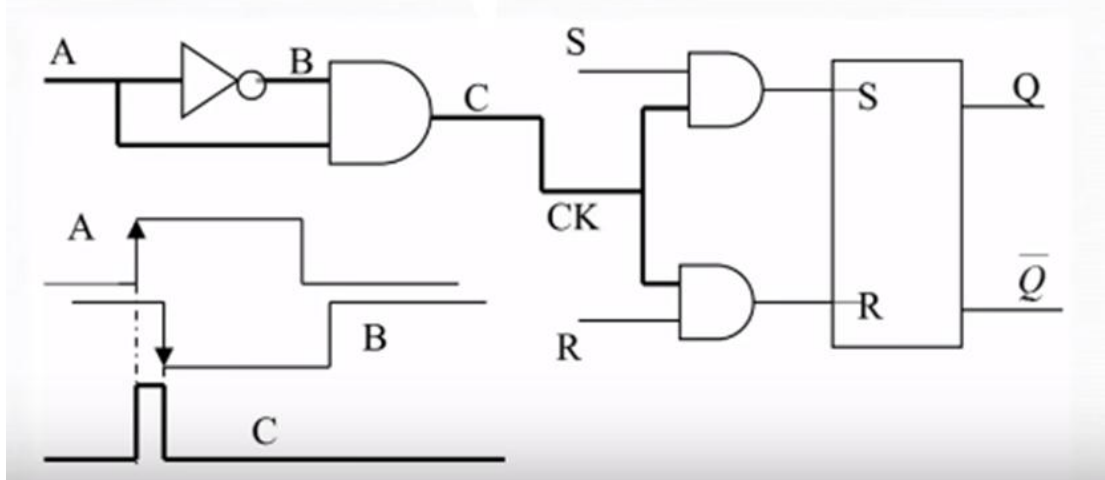




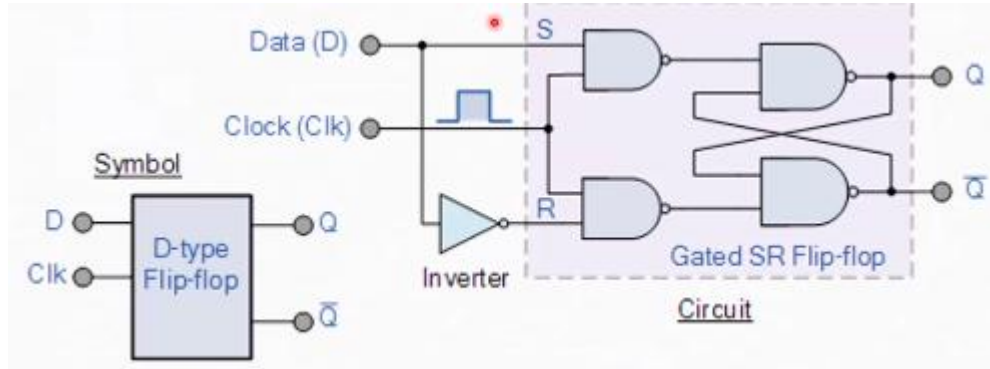Electronic Systems Simulators محاكيات الانظمة الالكترونية
 BY –KERIM .D.A




Clk	D	Q	\bar{Q}	Description
$\downarrow \gg 0$	X	Q	\bar{Q}	Memory no change
$\uparrow \gg 1$	0	0	1	Reset Q \gg 0
$\uparrow \gg 1$	1	1	0	Set Q \gg 1

 




Electronic Systems Simulators محاكيات الانظمة الالكترونية
BY –KERIM .D.A

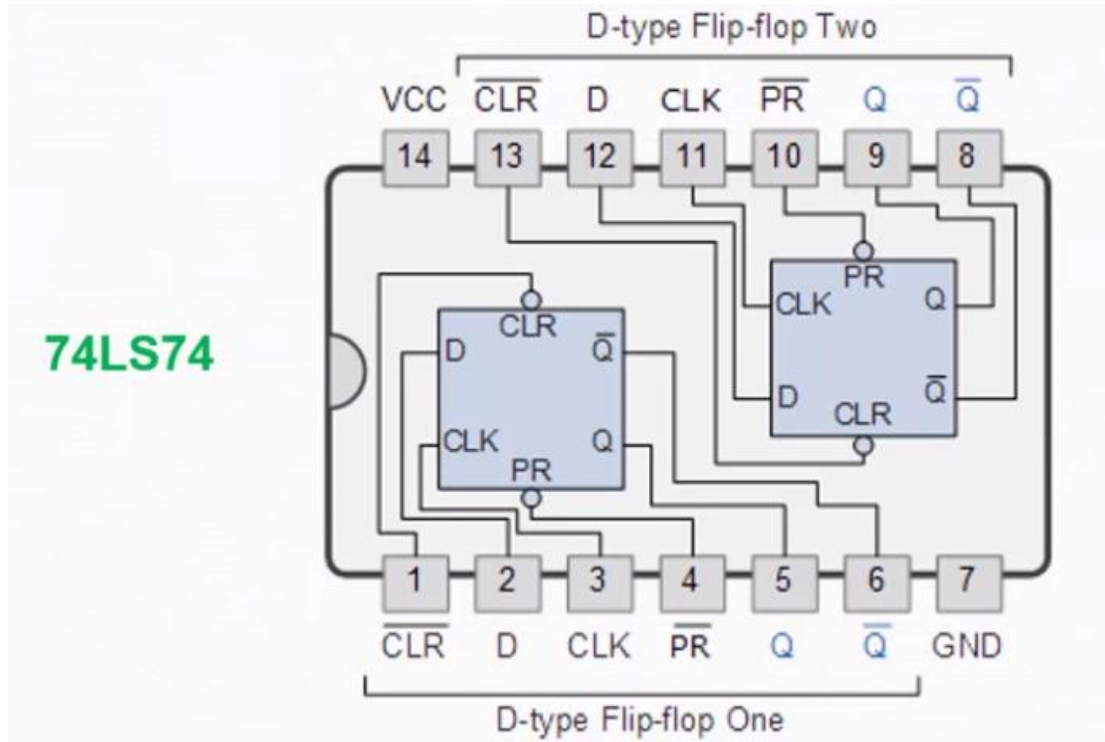74LS74 is a Dual D flip-flop
74LS174 HEX D flip-flop with direct clear input
74LS175 Quad D flip-flop with complementary outputs
74LS273 Octal D flip-flop containing eight D flip-flops with a clear input



Electronic Systems Simulators محاكيات الانظمة الالكترونية

BY -KERIM .D.A

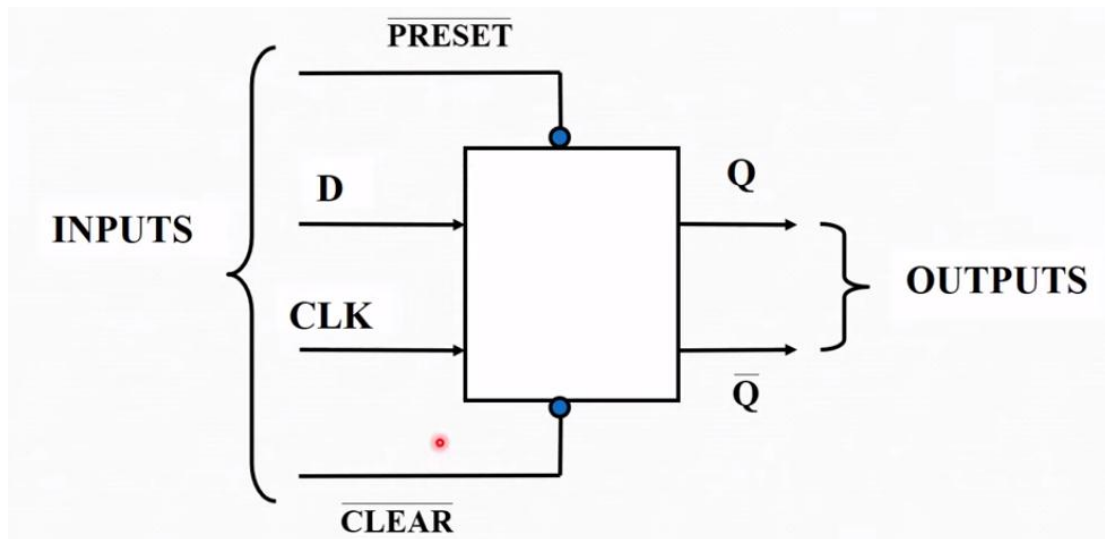


PRESET (PR) and **CLEAR (CLR)** ,,they are inputs no effect to clock in it .used to make the(F-F) in initial value

When PR=0 , then Q=1

When CLR=0, then Q=0



PR=0 ,, CLR=0...invalid condition

 



Electronic Systems Simulators محاكيات الانظمة الالكترونية

BY –KERIM .D.A

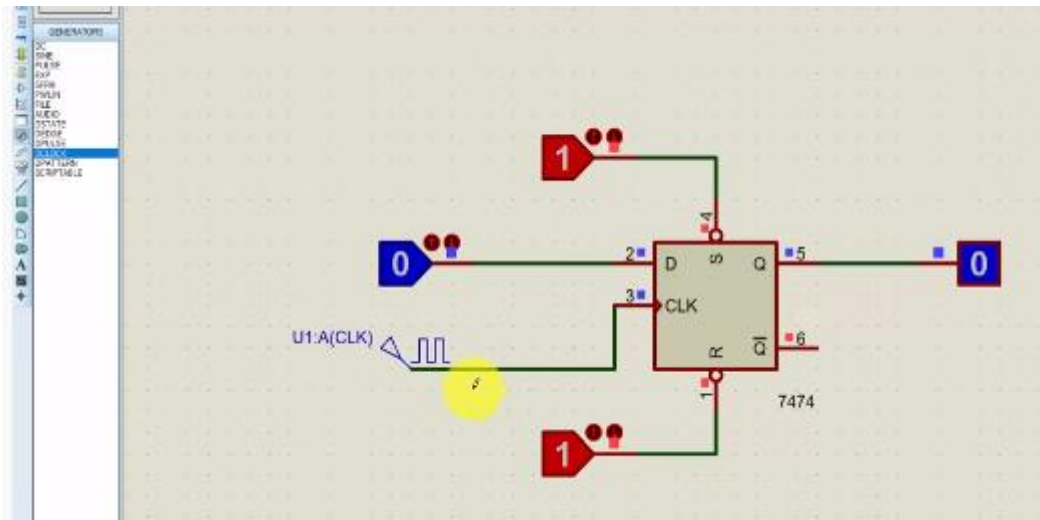 



محاكيات الانظمة الالكترونية Electronic Systems Simulators

BY -KERIM .D.A

