



**Ministry of Higher Education
University of Al-Maarif
Medical Instruments Engineering Techniques Department**



Power Electronic

*For
Students of Third class*


Lecture THREE Unijunction Transistor (UJT)

**By
Mr. Abdulla Saleh**

Department of Medical Instrumentation Engineering Techniques
2024-2025

UNIJUNCTION TRANSISTOR (UJT):

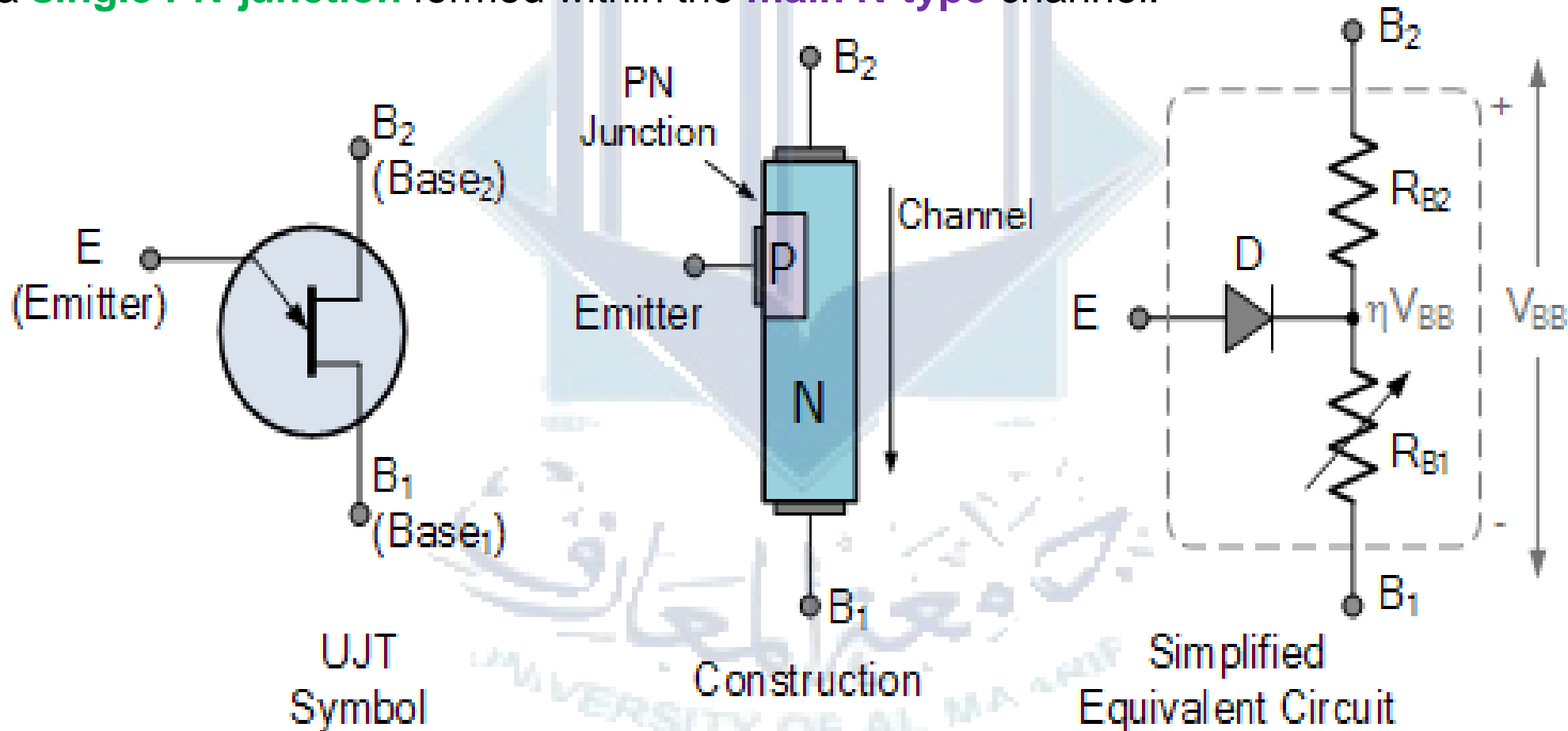- The Uni-junction Transistor (UJT) is a solid-state, **three-terminal device**.
- UJT is constructed using **P-type** and **N-type** semiconductor materials.
- It has a **single PN-junction** formed within the **main N-type** channel.



Equivalent circuit of UJT

- With no voltage applied to the (UJT) the **inter base resistance (R_{BB})** is given by:

$$R_{BB} = R_{B1} + R_{B2}$$

- The voltage across R_{B1} is given by:

$$V_A = V_{BB} \times \frac{R_{B1}}{R_{B1} + R_{B2}}$$

η

- Here, η is termed as an **intrinsic standoff ratio** and is given by,

$$\eta = \frac{R_{B1}}{R_{B1} + R_{B2}}$$


where η usually between **0.51 and 0.82**

- $V_A = \eta V_{BB}$ where V_A is called **stand off voltage**

- the forward voltage drop across silicon diode $V_D = 0.7 V$

$$V_E = V_D + \eta V_{BB} = V_P \quad \text{Peak point voltage}$$

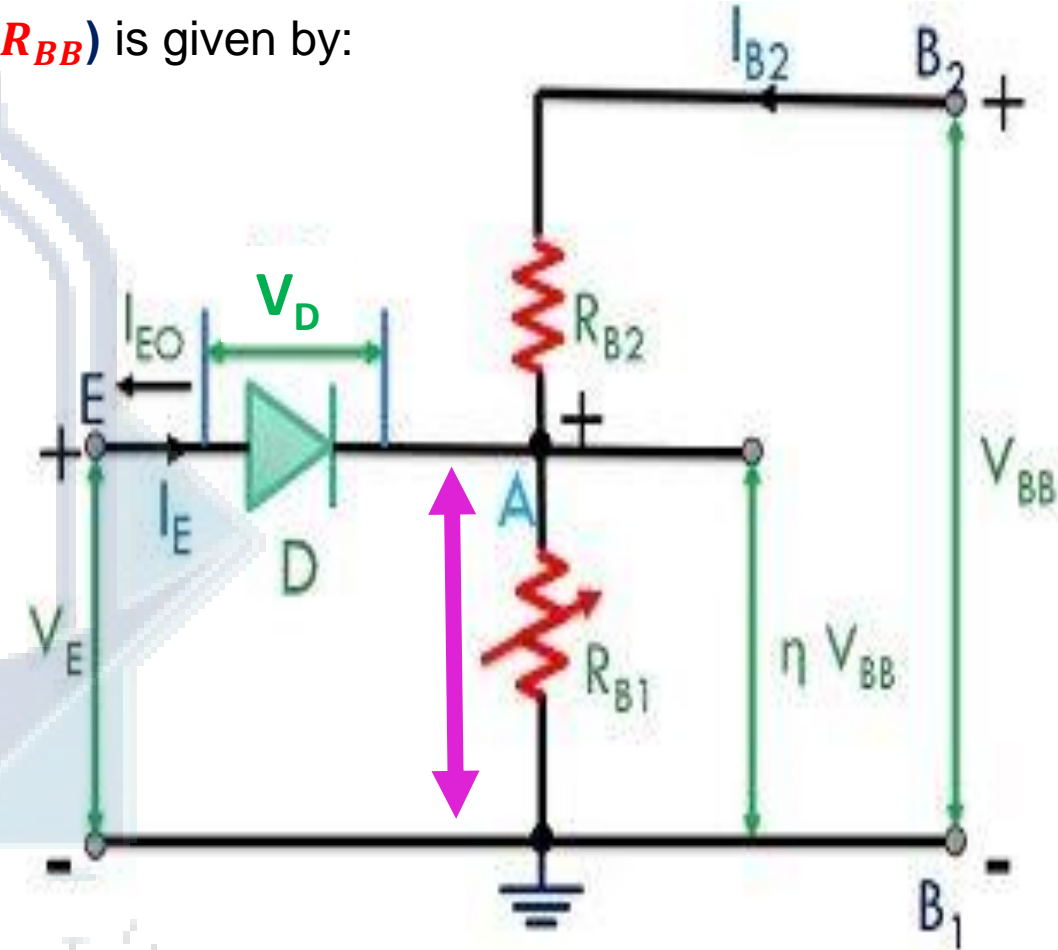When $V_E < \eta V_{BB} \therefore$ PN is reverse biased I_E is **negative**.
 When $V_E > \eta V_{BB} \therefore$ PN is forward & biased I_E is **positive**.



UJT OFF: When $I_E < I_P$
 UJT ON : When $I_E > I_P$

Ex 1:

The intrinsic stand - off ration for a (UJT) is determined to be (**0.6**) if the **inter - base resistance** is $10\text{ K}\Omega$ What are the value of R_{B1} and R_{B2}

Sol:

$$R_{BB} = R_{B1} + R_{B2} = 10\text{ K}\Omega \quad , \quad \eta = 0.6$$

$$\eta = \frac{R_{B1}}{R_{B1} + R_{B2}}$$

$$0.6 = \frac{R_{B1}}{10\text{ K}\Omega}$$

$$R_{B1} = 6\text{ K}\Omega$$

$$R_{B1} + R_{B2} = 10\text{ K}\Omega$$


$$6\text{ K}\Omega + R_{B2} = 10\text{ K}\Omega \quad \Rightarrow \quad R_{B2} = 10\text{ K}\Omega - 6\text{ K}\Omega \quad \Rightarrow \quad R_{B2} = 4\text{ K}\Omega$$

Home work(1)

A (UJT) has 10 V between the bases. if the intrinsic stand - off ration is (0.65) find the value of stand off voltage. What will be the peak -point voltage. if the forward voltage drop in the p-n junction is 0.7 v

Characteristics of Unijunction transistor

- The characteristic curve of the UJT shows the **relationship** between **emitter voltage (V_E)** and **emitter current (I_E)**.
- In the cut-off region, the emitter current (I_E) **remains below** the leakage current (I_{E0}).
- Conduction begins when the emitter voltage (V_E) reaches the peak voltage (V_P).
- After the peak voltage, as the emitter current (I_E) increases, the resistance of R_{B1} **decreases**.
- This decrease in R_{B1} demonstrates **negative resistance** in the negative resistance region.
- Once the **valley point** is reached, the device enters the **saturation region**, where further increases in emitter current (I_E) occur with little change in voltage.

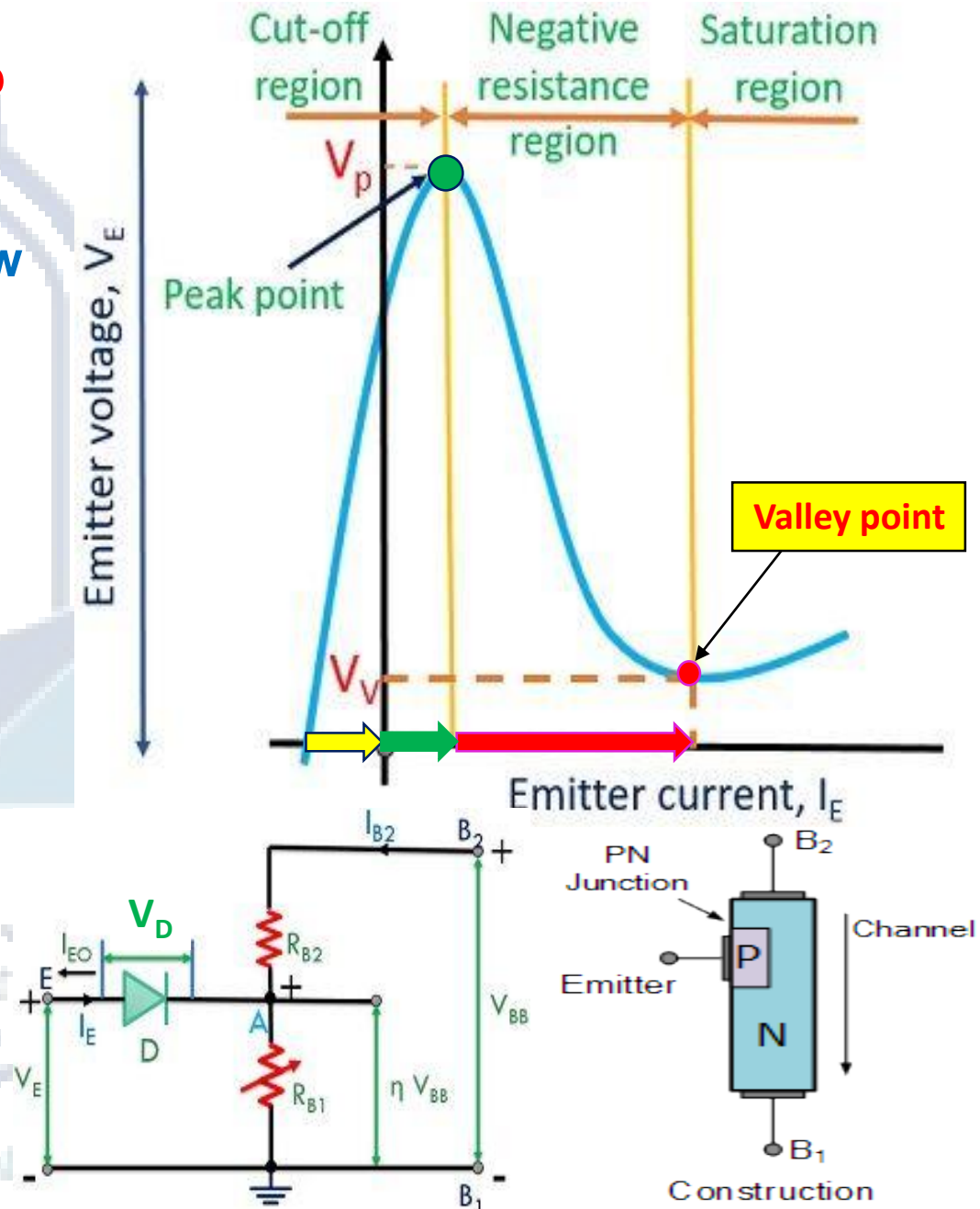

Applications of UJT

- UJT is mainly used as a trigger for SCRs and Triacs in AC power control.
- It's used in gate pulse generation, timing circuits, and trigger generators.
- UJT applications include sawtooth generators, oscillators and phase control.
- The simplest UJT circuit is the **Relaxation Oscillator**, producing non-sinusoidal waveforms.

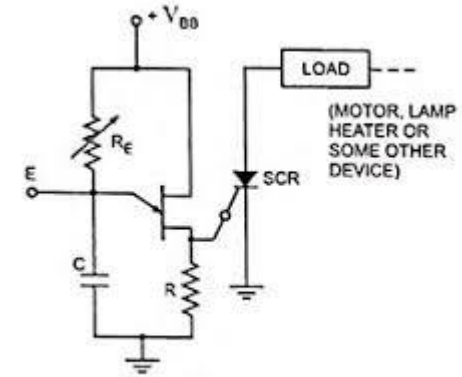


Fig. 26.91 UJT Triggering of An SCR



Relaxation Oscillator

- A UJT relaxation oscillator is a simple circuit that generates **non-sinusoidal** waveforms (usually **sawtooth** or **pulse**).
- It works by **charging a capacitor** through a resistor. When the capacitor voltage reaches a certain threshold, the UJT turns on,

$$V_C = \eta V_{BB} + V_D = V_P$$

- discharging** the capacitor rapidly and creating a sharp pulse.

$$V_C = V_{BB} \left(e^{-\frac{t}{R_3 C}} \right)$$

Discharge at certain time

$$V_C = V_{BB} \left(1 - e^{-\frac{t}{R_3 C}} \right)$$

charge at certain time



- This process repeats, producing an **oscillating** output.
- The frequency of oscillation is controlled by the **resistor** and **capacitor values (Time Constant)**.

$$\tau = R_3 C$$

$$F = \frac{1}{T}$$

F: the frequency (HZ)

$$T = R_3 C \ln \left(\frac{1}{1 - \eta} \right)$$

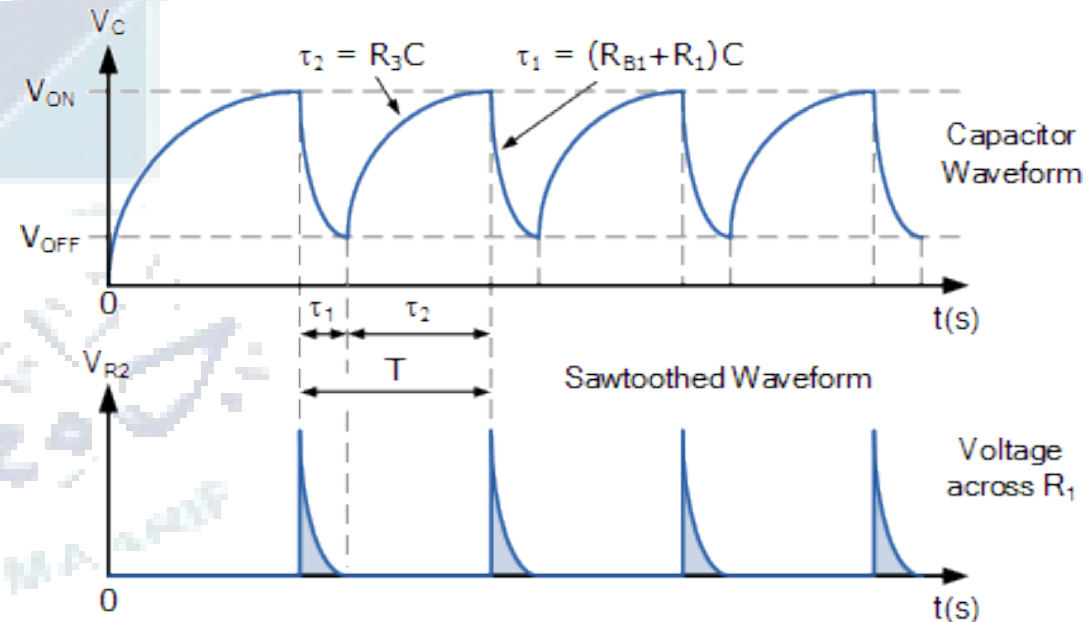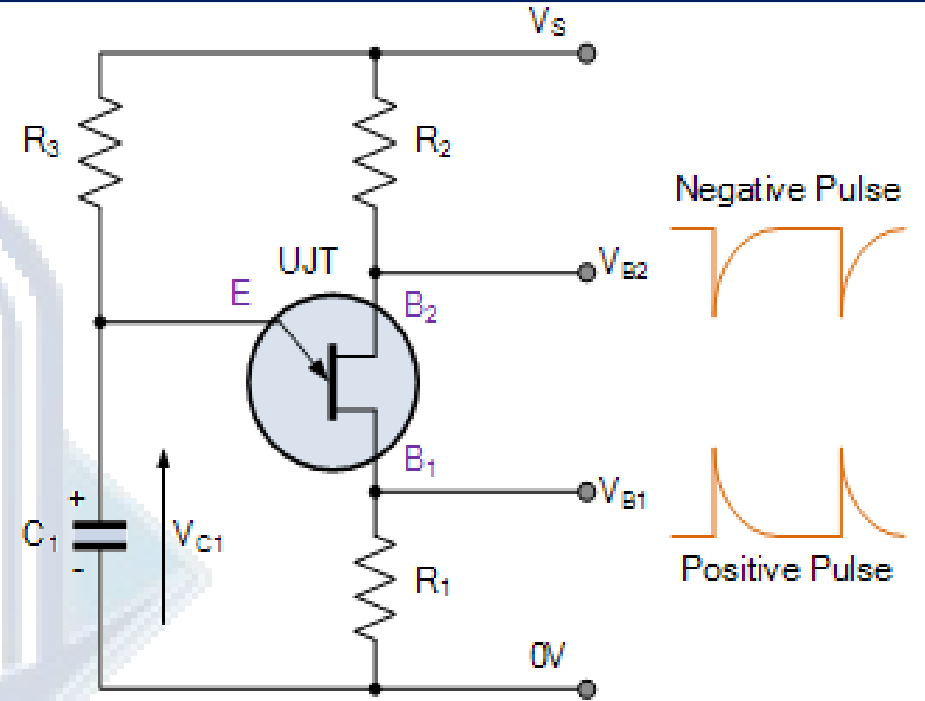

Ex 2: For the circuit Shown find T, F, V_o , using $\eta = 0.5$

Sol:

i

$$T = R_3 C \ln \left(\frac{1}{1 - \eta} \right)$$

$$T = 39 \text{ k}\Omega \times 0.1 \mu\text{f} \times \ln \left(\frac{1}{1 - 0.5} \right)$$

$$T = 2.7 \text{ ms}$$

ii

$$F = \frac{1}{T}$$

$$F = \frac{1}{2.7 \text{ ms}}$$


$$F = 370 \text{ HZ}$$

iii

$$V_o = \eta V_{BB} + V_D$$


$$V_o = 0.5 \times 20 + 0.6$$

$$V_o = 10.6 \text{ V}$$

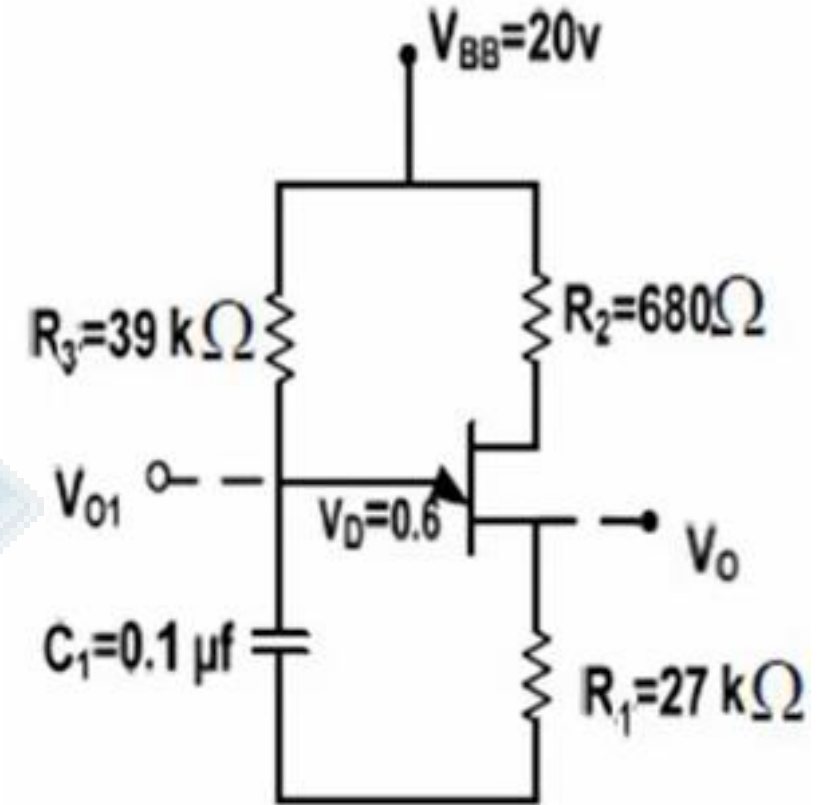

Home work(2)

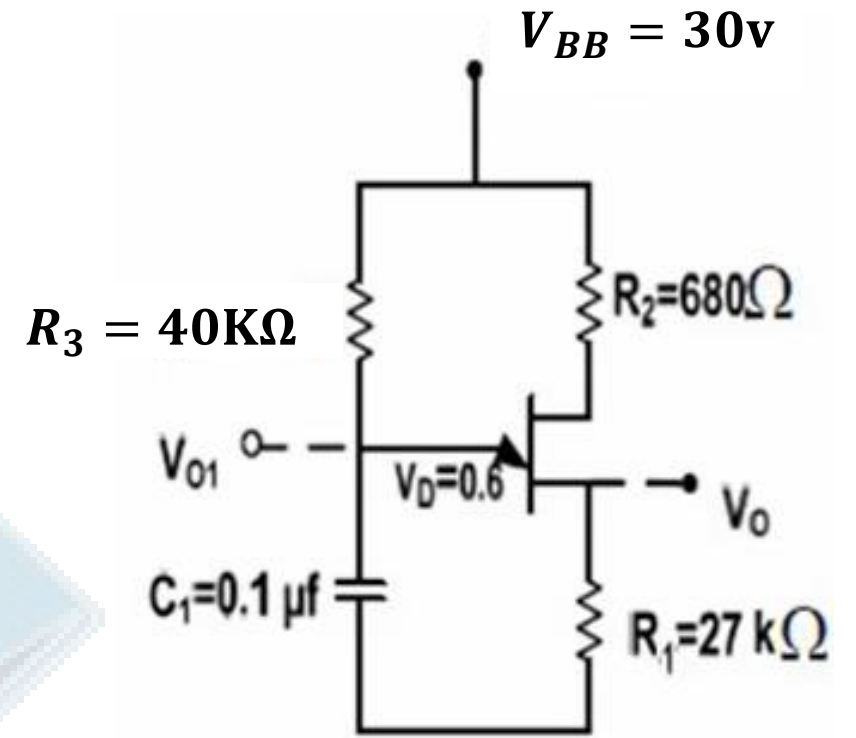For the circuit Shown find T, f, Vo, using $\eta = 0.6$



H.W
(3)

Using the UJT to construct an oscillator as shown below, calculate:

- 1- Minimum & Maximum frequency of pulses which can be generated.
- 2- Maximum capacitor voltage.

Sol:

$$T = (R_3 + R_{pot})C \ln\left(\frac{1}{1-\eta}\right)$$

Minimum frequency

When $R_{pot} = 0\Omega$


Maximum frequency

When $R_{pot} = 2.2\text{ K}\Omega$

Complete the solution

Answers:

- 1- 93.2 Hz , 4.33 kHz
- 2- 8.4 V

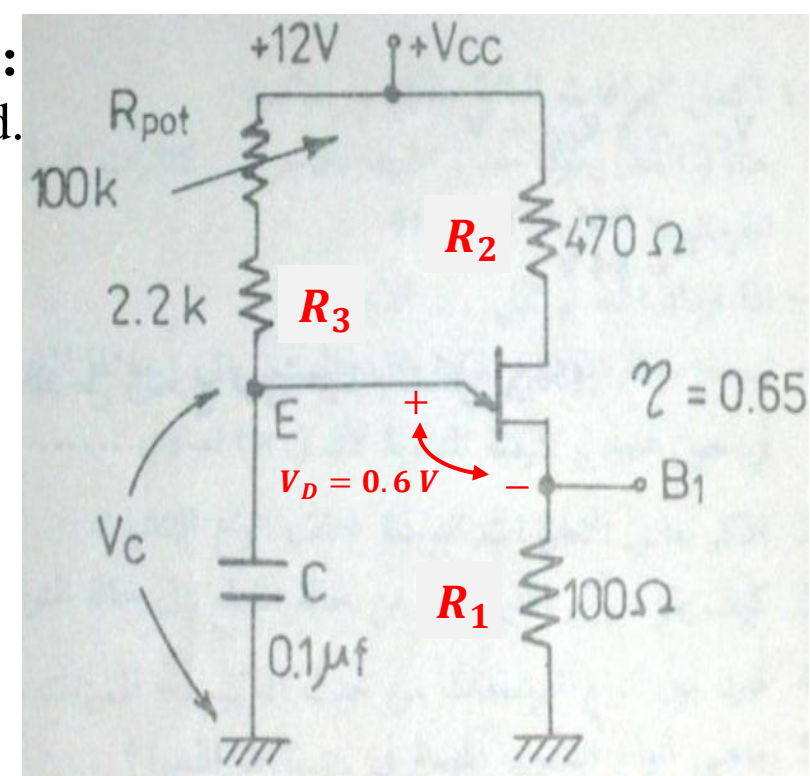

Home work(4)

The data sheet for a 2N2646 Unijunction transistor gives the intrinsic stand-off ratio as 0.65. If a 100nF capacitor is used to generate the timing pulses, calculate the timing resistor required to produce an oscillation frequency of 100Hz.

