



**Ministry of Higher Education  
University of Al-Maarif  
Medical Instruments Engineering Techniques Department**



# **Power Electronic**

*For  
Students of Third class*

**Lecture TWO  
Power Transistor**


**By  
Mr. Abdulla Saleh**

Department of Medical Instrumentation Engineering Techniques  
2024-2025

# Diode Principle

p-doping

n-doping

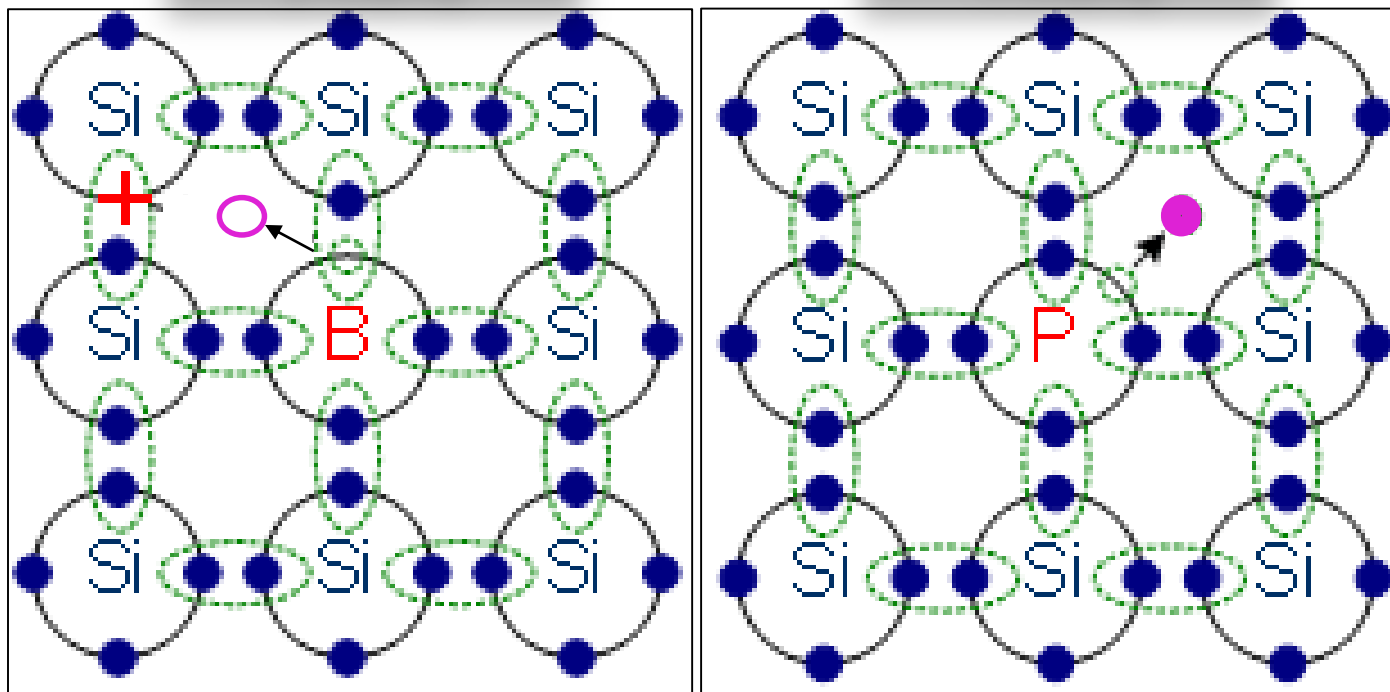


Free hole




Free electron



## PN-Junction

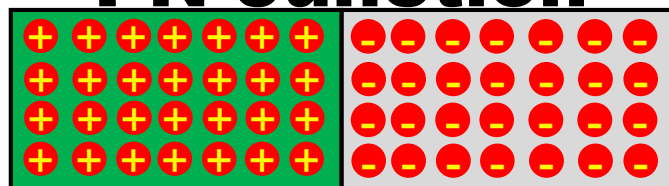


Anode (+)

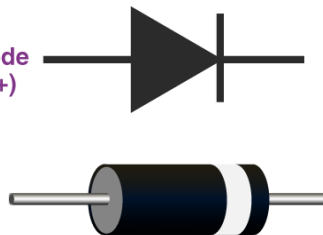


Cathode (-)



## Forward Biasing

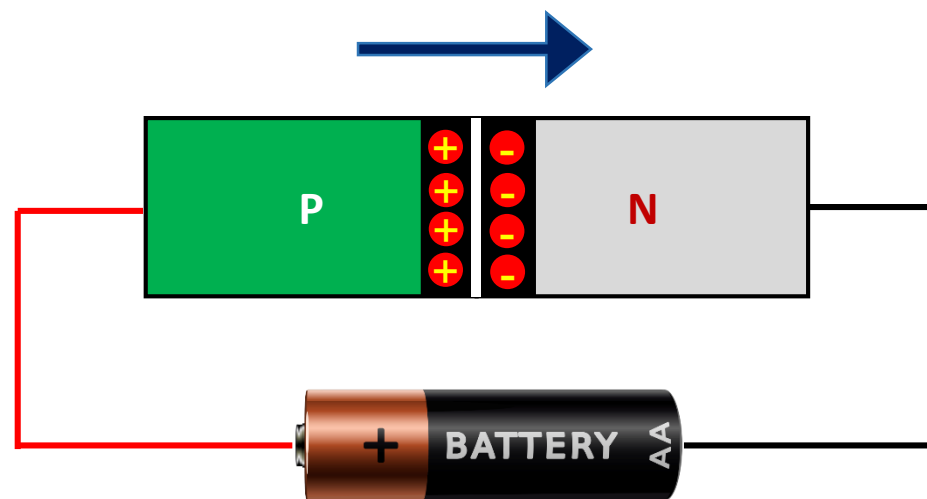

## Reverse Biasing

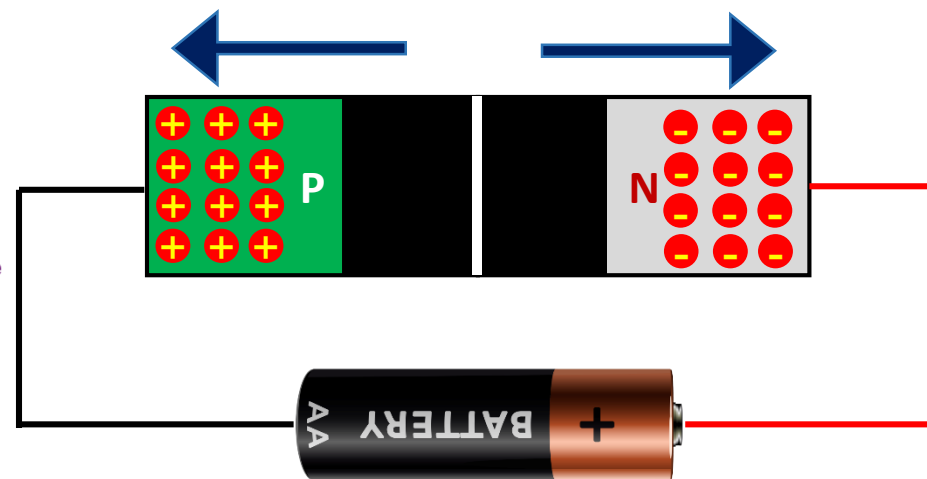

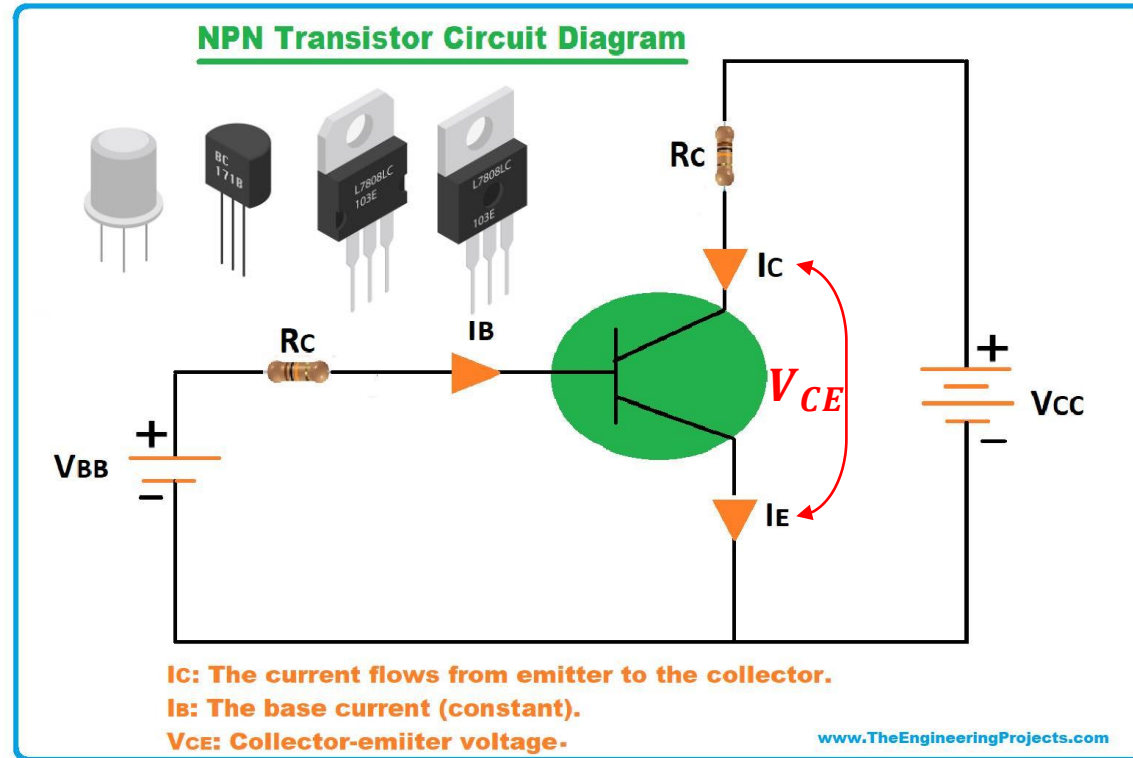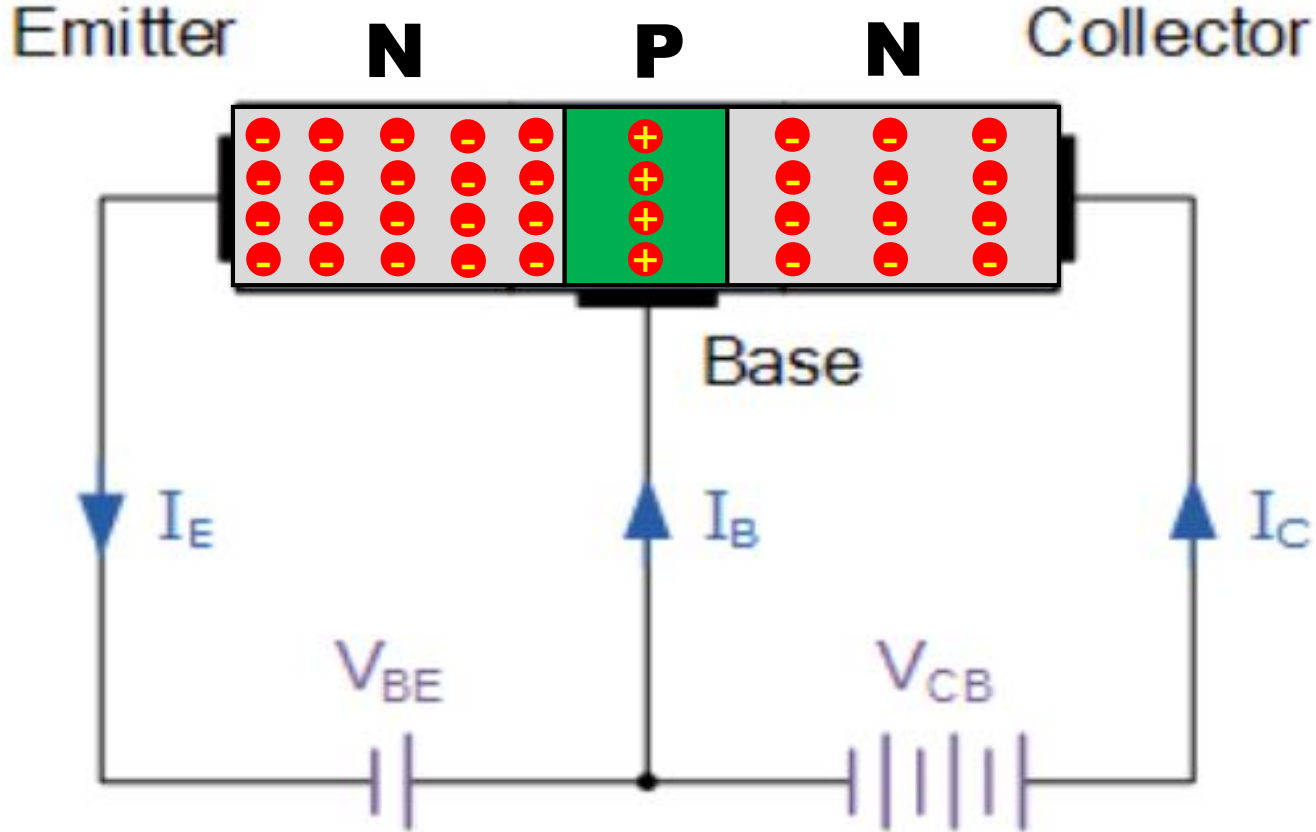
# Power Bipolar Junction Transistor (BJT) Principle






$$I_C + I_B = I_E$$

$$\beta = \frac{I_C}{I_B}$$

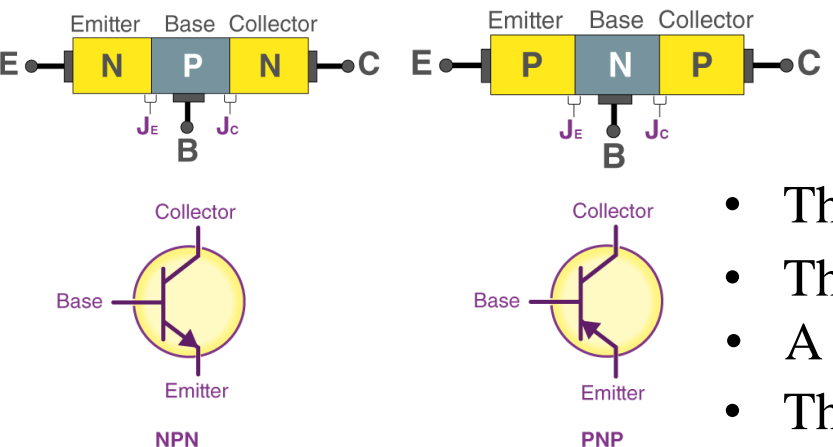


- The transistor consists of **three layers**: NPN or PNP.
- The collector current ( $I_C$ ) is **dependent** on the base current ( $I_B$ ).
- A change in base current  $I_B$  results in an **amplified** change in collector current  $I_C$ .
- The **ratio** of these currents ranges from 15 to 100 and called beta  $\beta$ .

# Characteristics of (BJTs)

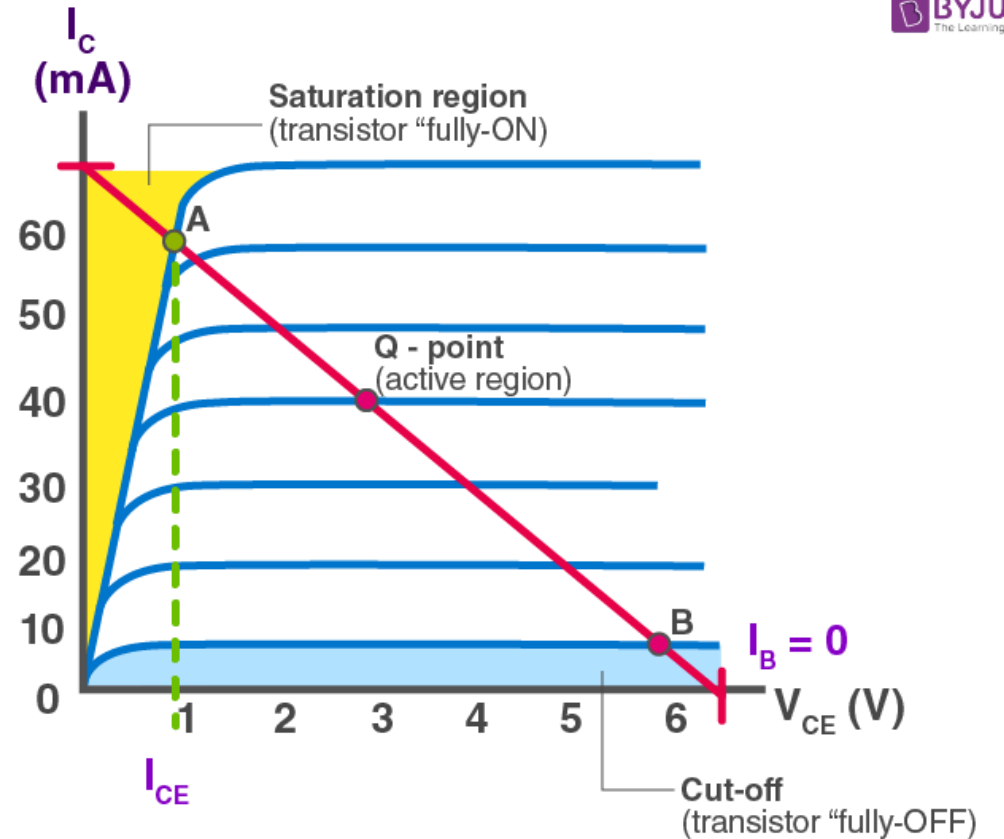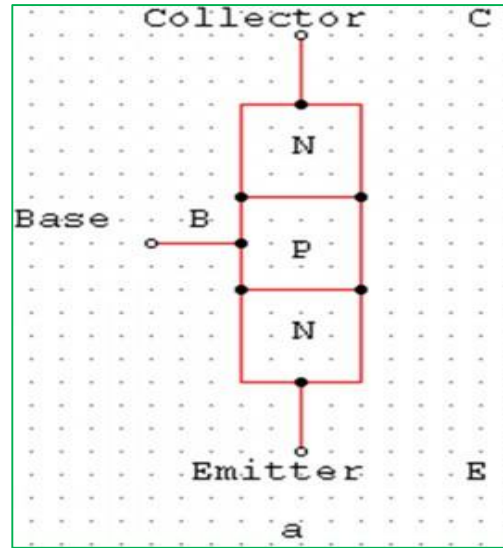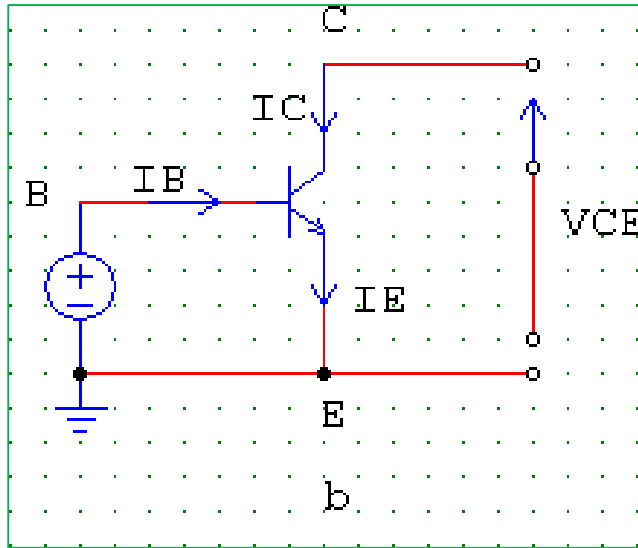

- The transistor is used as **a switch** (Saturation + cut-off region) and as **amplifier** (active region) in **power applications**
- It has **controlled** turn-on and turn-off characteristics.
- Operates in the saturation region to **reduce on-state voltage drop**.
- **Switching speed** is **higher** than that of **thyristors**.
- **Voltage** and **current** ratings are **lower** than those of thyristors.

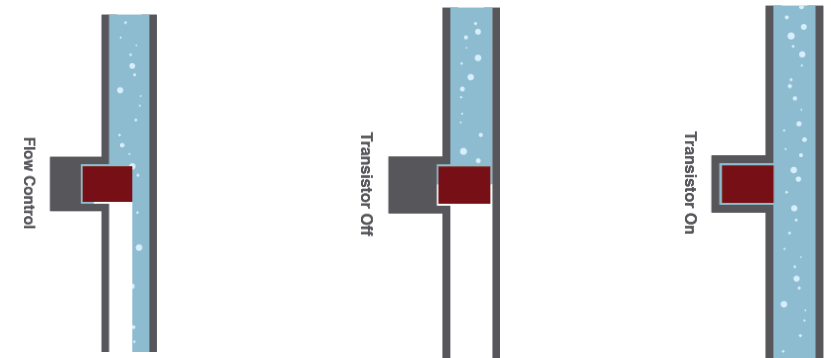

## Input Circuit

$$V_{BB} = I_B R_B + V_{BE}$$

$$V_{BB} - V_{BE} = I_B R_B$$

$$\div I_B$$

$$\therefore R_B = \frac{V_{BB} - V_{BE}}{I_B} \quad (1)$$

## Output Circuit

$$V_{CC} = I_C R_C + V_{CE}$$

$$V_{CC} - V_{CE} = I_C R_C$$

$$\div I_C$$

$$\therefore R_C = \frac{V_{CC} - V_{CE}}{I_C} \quad (2)$$

The equation above can be used to draw the dc load line by choosing two points as follows:

**At cut off region:**

$$I_C (\text{cut off}) = 0$$

$$V_{CE} (\text{cut off}) = V_{CC}$$



**At saturation region:**

$$V_{CE} (\text{sat}) = 0 \quad I_C (\text{sat}) = \frac{V_{CC}}{R_C}$$

$$\beta = \frac{I_C (\text{sat})}{I_B (\text{sat})} \quad \text{where } \beta \text{ represents the DC current gain}$$

The perfect switch condition is:  $I_{B(\text{per})} > 3 \times I_{B(\text{sat})}$

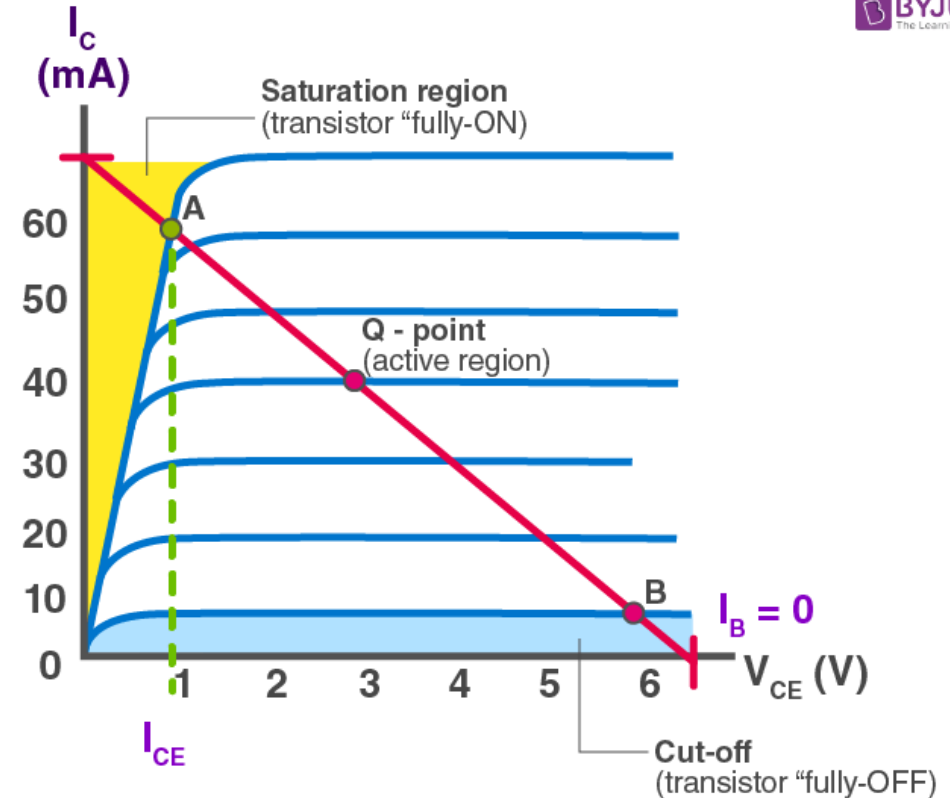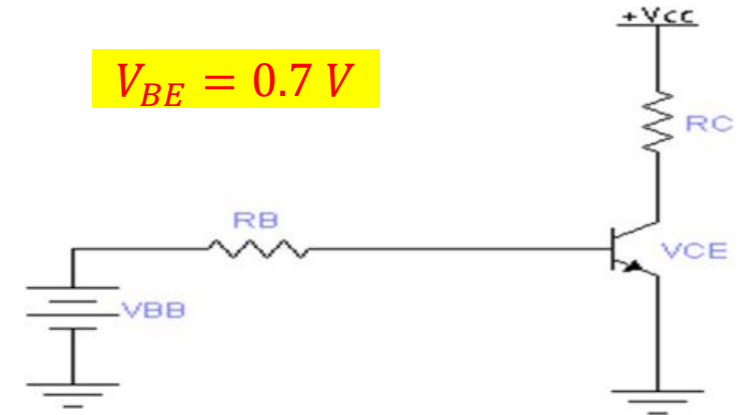$I_1 = 2 \times I_{B(\text{sat})}$  resistor current if connect parallel with base



**EX:1**/For transistor as a switch if the transistor has the following specification ( $V_{CE(sat)} = 1.5$ ;  $V_{BE(sat)} = 0.65$ ;  $\beta = 45$ ;  $V_{in} = 1.5$  V) calculate the value of  $R_B$  which make the transistor works in saturation region.

**Sol:**


$$I_{C(sat)} = \frac{V_{CC} - V_{CE}}{R_C} = \frac{30 - 1.5}{2k} = 14mA$$
$$I_{B(sat)} = \frac{I_{C(sat)}}{\beta} = \frac{14mA}{45} = 0.3mA.$$

$$I_{B(per)} = 3 \times I_{B(sat)}$$

$$I_{B(per)} = 3 \times 0.3mA = 0.9mA$$

$$R_B = \frac{V_{BB} - V_{BE}}{I_B} = \frac{1.5 - 0.65}{0.9mA}$$

$$= 944 \Omega \cong 1k\Omega$$

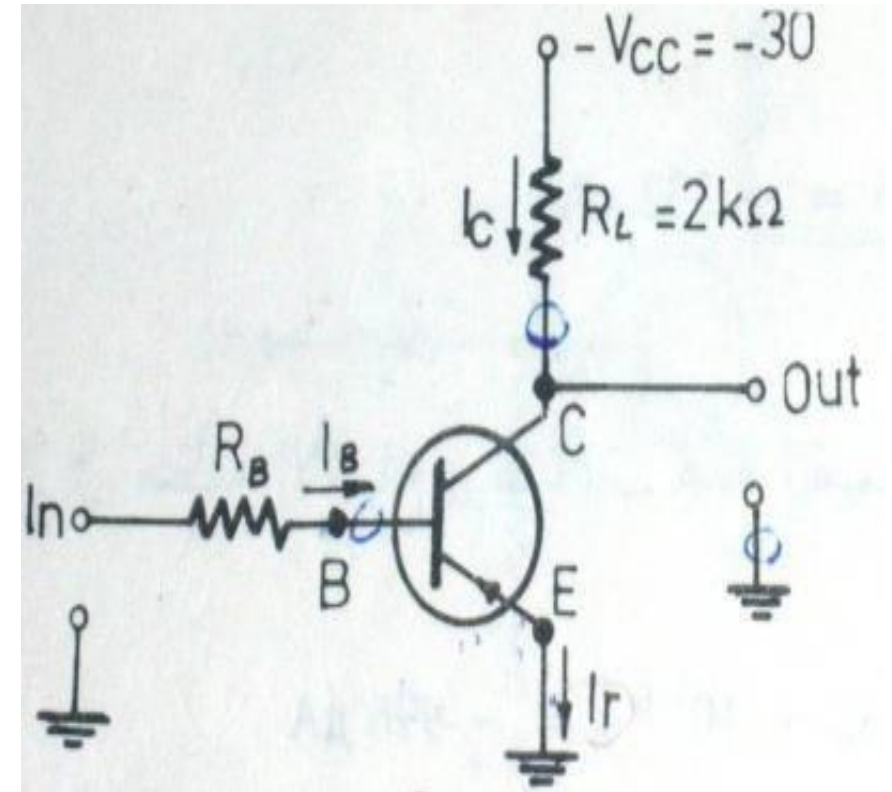

**EX: 2** For the circuit shown below ( $V_{BE} = 0.65 \text{ V}$ ,  $\beta = 50$ , and  $V_{in} = 1 \text{ V}$ ) Calculate the value of ( $R_1$ ,  $R_B$ ) which make the transistor works in saturation region.

$$I_{C(sat)} = \frac{V_{CC} - V_{CE}}{R_C} = \frac{15}{500} = 30 \text{ mA}$$

$$I_{B(sat)} = \frac{I_{C(sat)}}{\beta} = \frac{30 \text{ mA}}{50} = 0.6 \text{ mA}$$

$$I_{B(per)} = 3 \times I_{B(sat)} \Rightarrow I_{B(per)} = 3 \times 0.6 \text{ mA} = 1.8 \text{ mA}$$


To certify the operation of the transistor in saturation region we may use

$$I_1 = 2 \times I_{B(sat)} \Rightarrow I_1 = 2 \times 0.6 = 1.2 \text{ mA}$$

$$R_1 = \frac{V_{BB} - V_{BE}}{I_1} = \frac{5 - 0.65}{1.2 \text{ mA}} \Rightarrow R_1 = 3.625 \text{ k}\Omega$$


$$I_B = I_{B(per)} - I_1 = 1.8 - 1.2 = 0.6 \text{ mA}$$
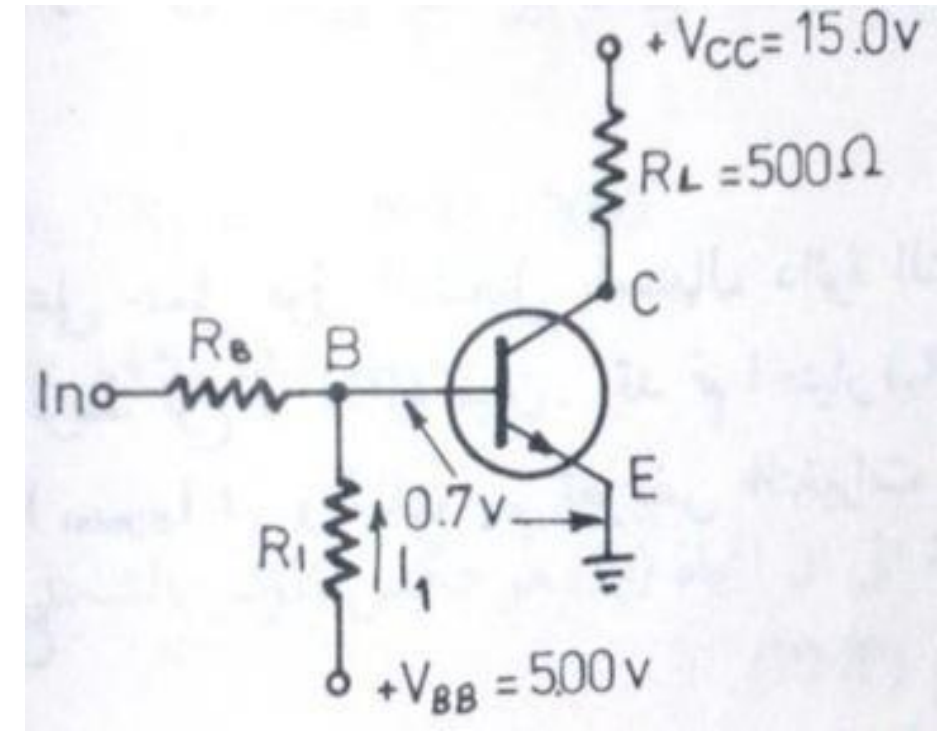
$$R_B = \frac{V_{BB} - V_{BE}}{I_B} = \frac{1 - 0.65}{0.6 \text{ mA}} \Rightarrow R_B = 0.583 \text{ k}\Omega$$


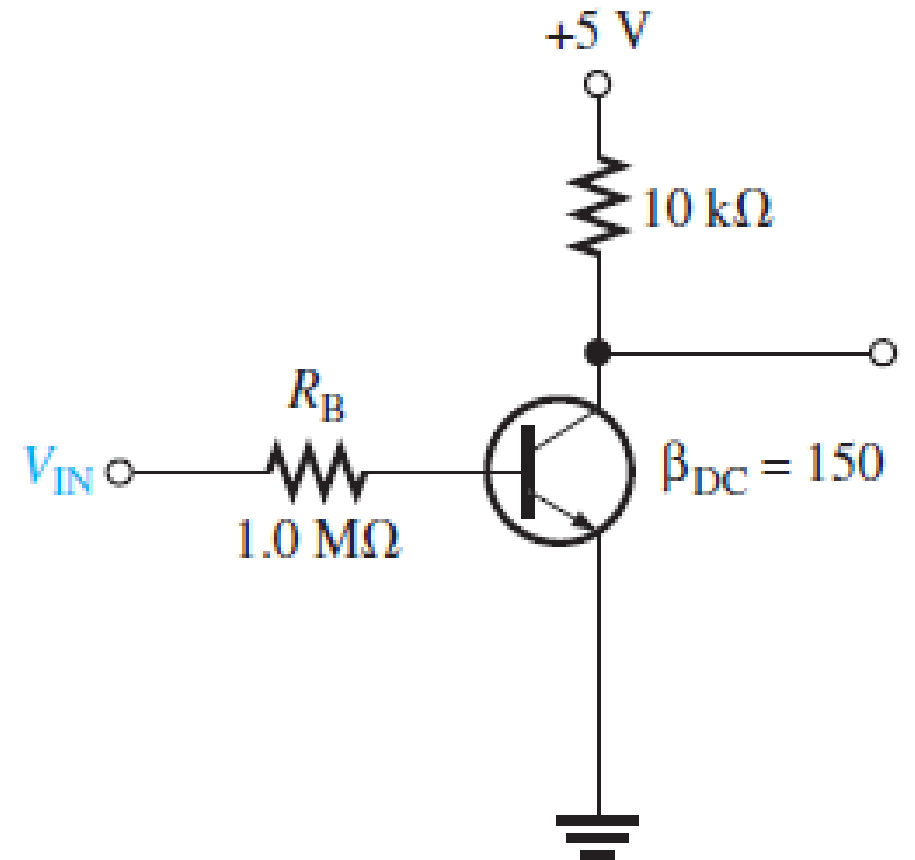
## H.W

Determine  $I_{C(\text{sat})}$  for the transistor in Figure 4–58. What is the value of  $I_B$  necessary to produce saturation? What minimum value of  $V_{\text{IN}}$  is necessary for saturation? Assume  $V_{\text{CE}(\text{sat})} = 0 \text{ V}$ .





# Dynamic Switching Characteristics:

- **Time delay ( $t_d$ ):**

Is the time taken for  $I_C$  to reach 10 % of its final value  $I_{C(sat)}$ .

- **Rise time ( $t_r$ ):**

Is the time taken for ( $I_C$ ) to change from 10% to 90 % of Its final value  $I_{C(sat)}$ .

- **Conduction time ( $T_{ON}$ ) =  $t_d + t_r$**


- **Storage time ( $t_s$ ):**

Is the time interval between the input and the point at which  $I_C$  reaches 90% of its final value  $I_C(sat)$ .


- **Fall time ( $t_f$ ):**

Is the time taken for ( $I_C$ ) to fall from 90% to 10% of its final value  $I_C(sat)$ .

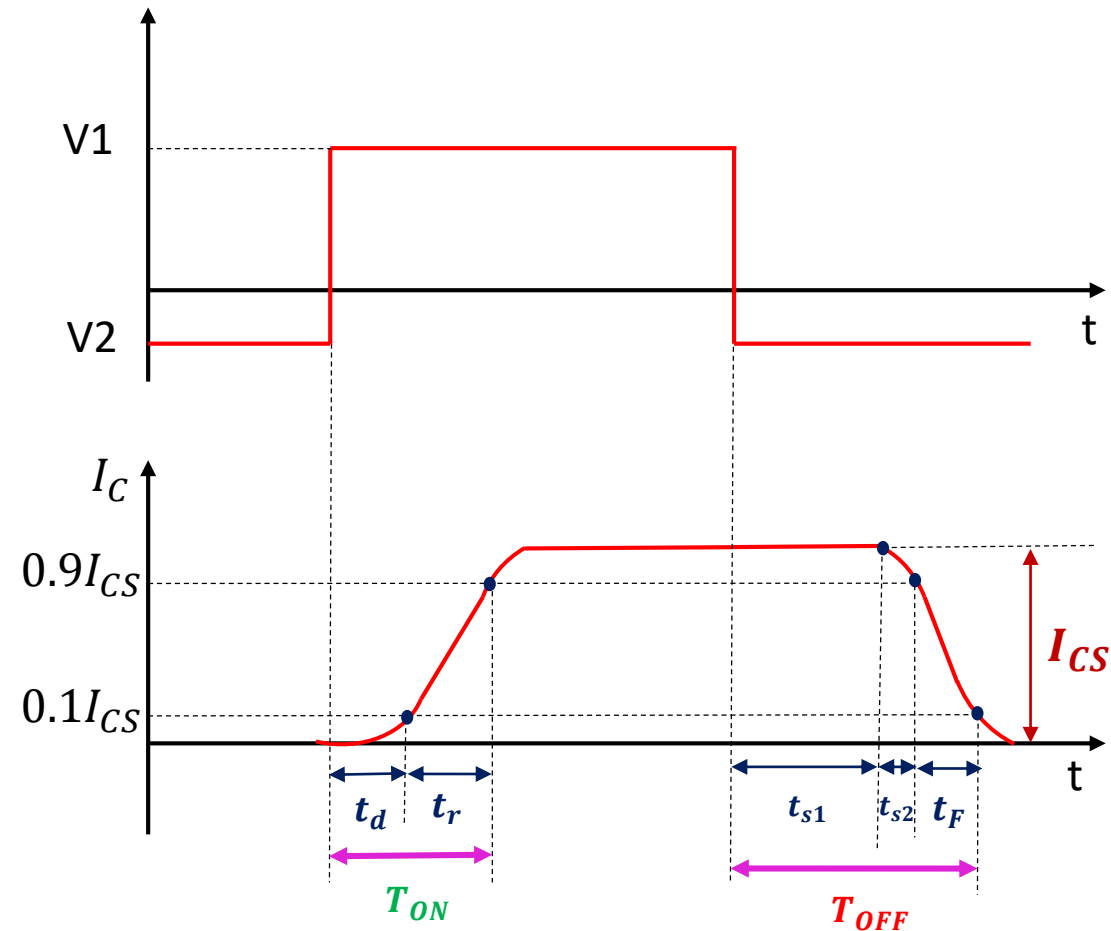- **Cut off time ( $T_{OFF}$ ) =  $t_s + t_f$**




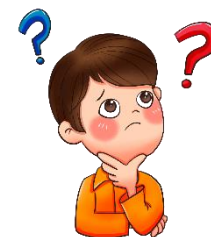It is important to Reduce Cut off time in switching Mode transistor . HOW?


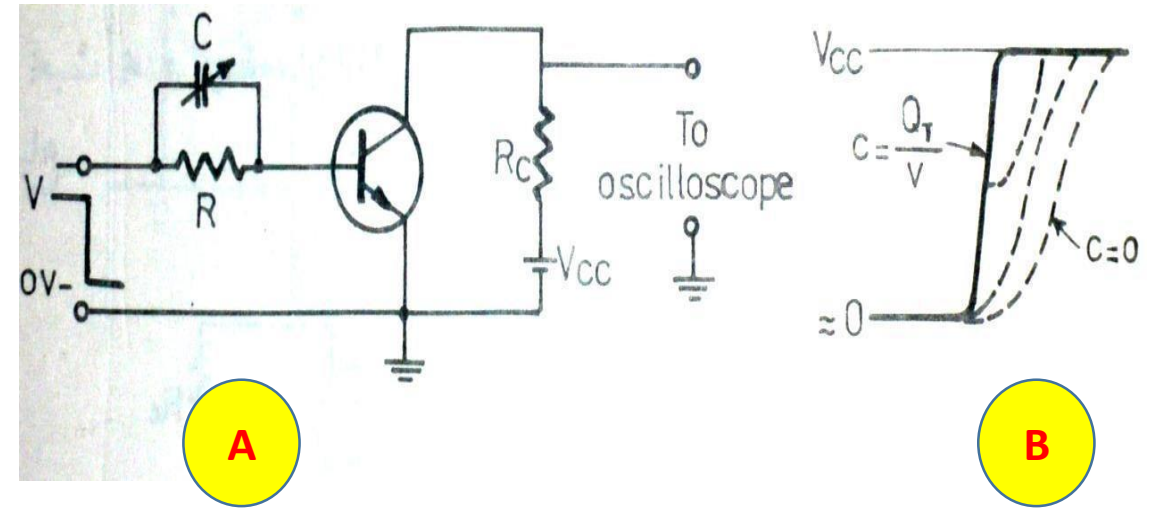
## Improvement of Switching Time:

- Cut-off Time  $T_{OFF}$  can be improved by connecting a capacitor in parallel with the base resistor  $R_B$ .
- The capacitor helps to attract and remove the base charge more quickly.
- This reduces the storage time ( $t_S$ ), which in turn shortens the cut-off time.
- Faster removal of base charge leads to faster switching from ON to OFF states.



# BJT applications in Medical Field

- **Pacemakers** and Implants for regulating and amplifying electrical impulses.
- Medical Imaging (**MRI, Ultrasound**) to process and amplify signals for accurate diagnostics.
- Wearable Devices like **glucose monitors** and **fitness trackers** to process health data.
- **ECG/EEG** systems to amplify heart and brain signals for monitoring.

