



**Ministry of Higher Education
University of Al-Maarif
Medical Instruments Engineering Techniques Department**



Medical electronic systems

*For
Students of Third class*

**Unit ONE
Regulated power supplied**


**By
Mr. Abdulla Saleh**

Regulated power supply

A **regulated power supply** converts AC to a **stable** DC output, ensuring consistency despite input fluctuations. Also called a linear power supply, it consists of various circuit blocks to maintain a constant DC output from an AC input.

The basic building blocks of a regulated DC power supply are as follows:

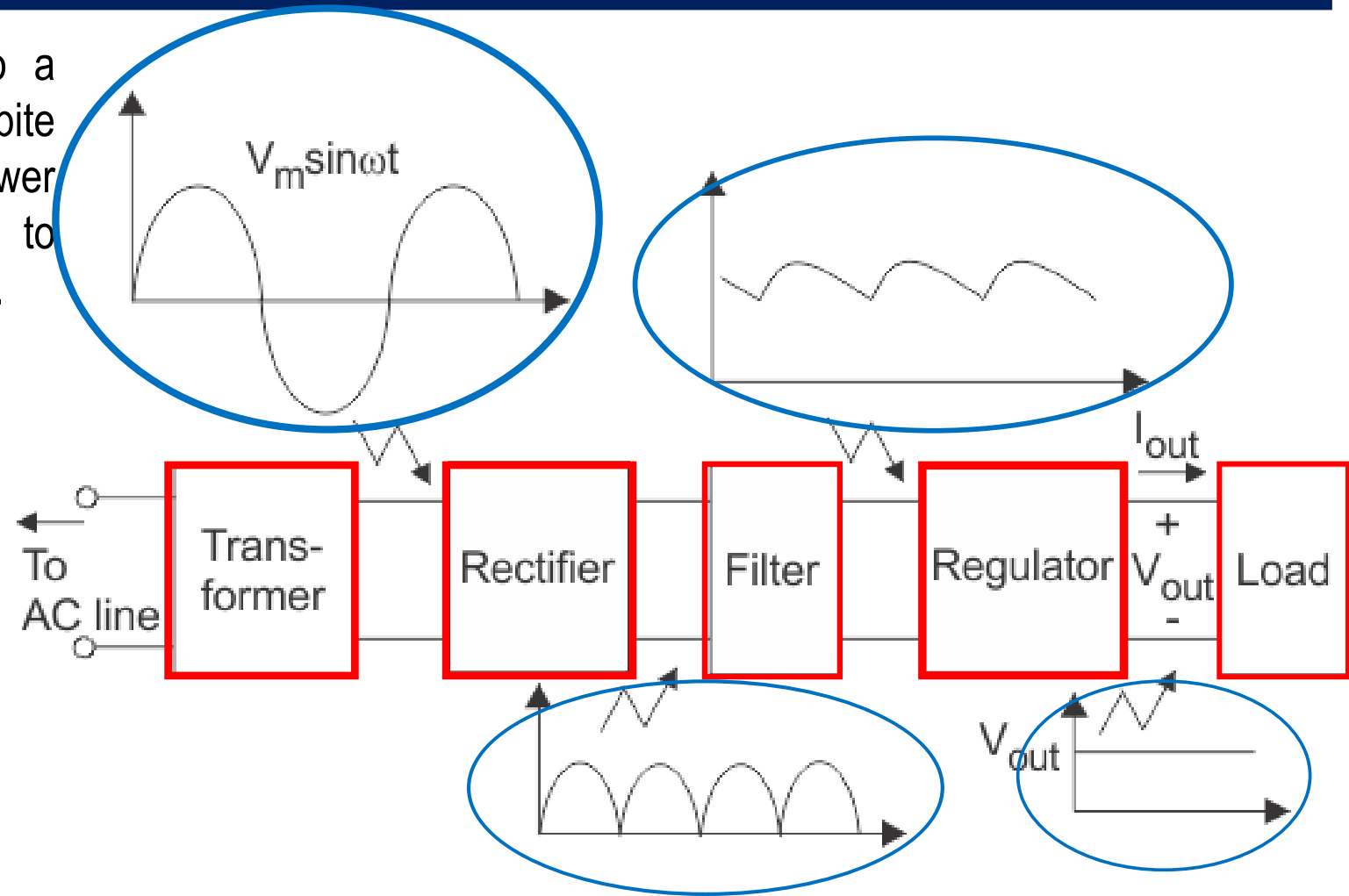1. A **step-down transformer**
2. A **rectifier**
3. A **DC filter**
4. A **regulator**






Components of typical linear power supply

Regulated power supply

A **step-down transformer** reduces AC mains voltage to the required level for the rectifier circuit.

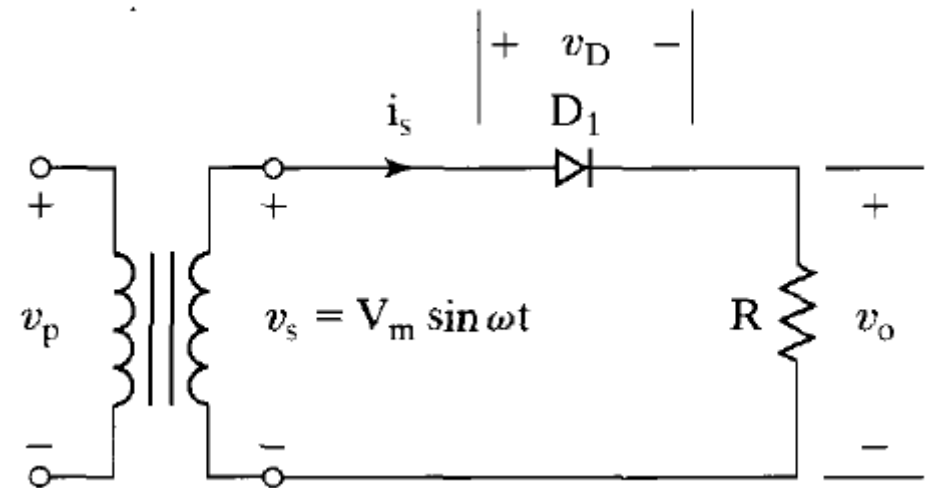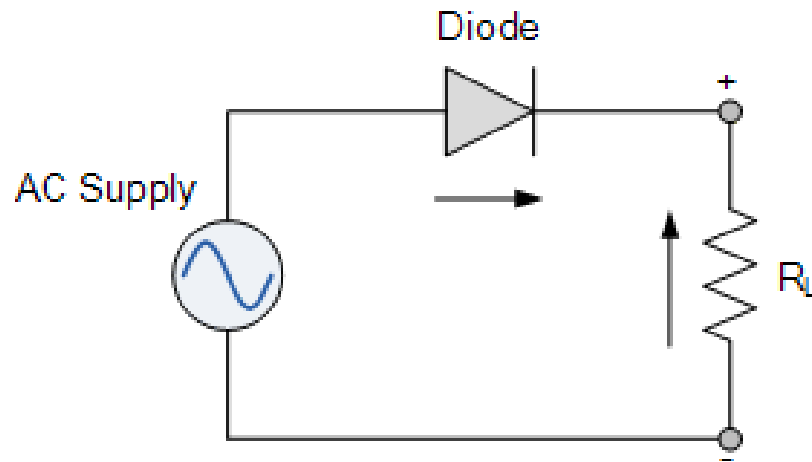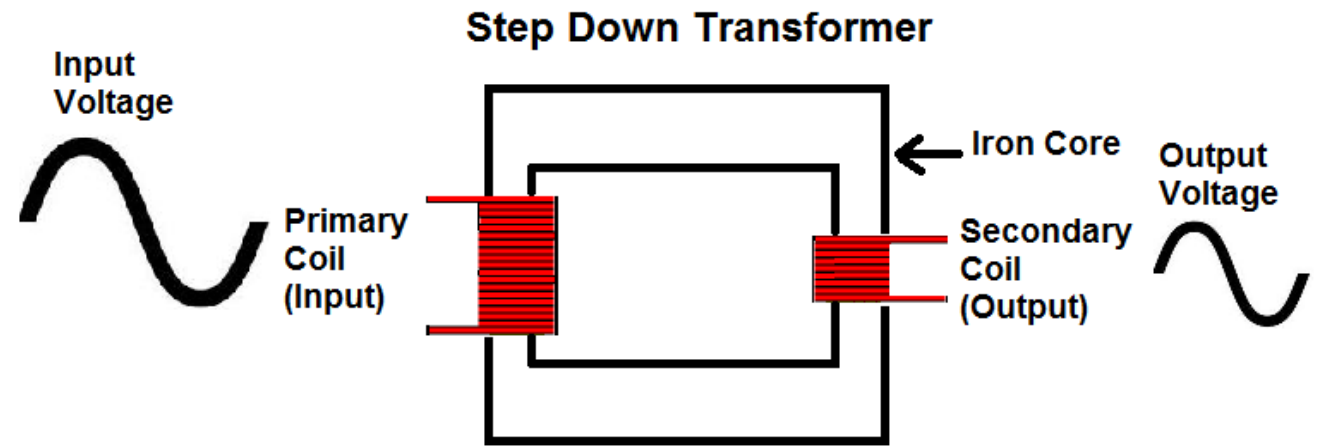
$$\therefore \frac{V_{s1 \max}}{V_{s2 \max}} = \frac{n_1}{n_2}$$




Regulated power supply

A **rectifier** is a circuit with diodes that converts AC into pulsating DC. It transforms alternating voltage or current into direct current. Key voltage measures include **peak voltage**, **peak-to-peak voltage**, **average voltage**, and **root-mean-square voltage**. Peak and peak-to-peak voltages are visible on plots, while average and RMS voltages are less apparent.
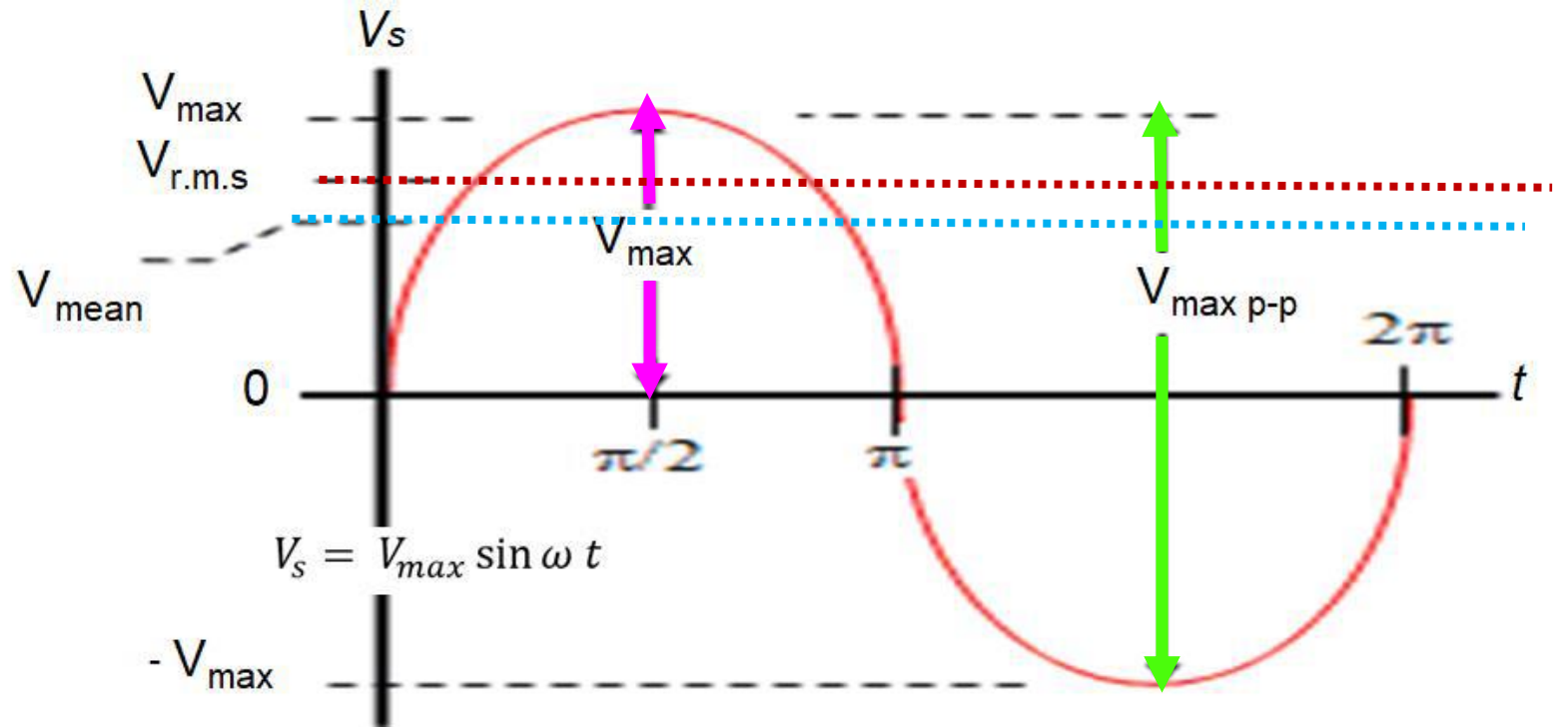
$$V_s \text{ rms} = \frac{V_s \text{ max}}{\sqrt{2}}$$



Single phase Half wave Rectifier

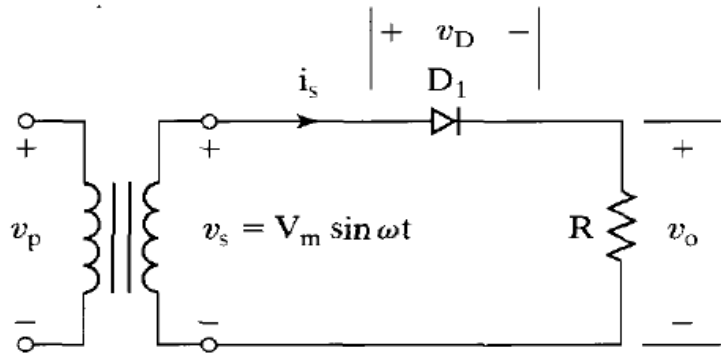

$$V_{L\text{ mean}} = \frac{1}{T} \int_0^T f(t) dt$$

$$V_{L\text{ mean}} = \frac{1}{2\pi} \int_0^\pi V_s \text{ max } \sin\theta d\theta$$

$$V_{L\text{ mean}} = \frac{V_s \text{ max}}{2\pi} \int_0^\pi \sin\theta d\theta$$

$$V_{L\text{ mean}} = \frac{V_s \text{ max}}{2\pi} \cdot -\cos\theta \Big|_0^\pi$$

$$V_{L\text{ mean}} = \frac{V_s \text{ max}}{2\pi} \cdot -(-1 - 1)$$

$$V_{L\text{ mean}} = \frac{V_s \text{ max}}{2\pi} \cdot 2$$

$$V_{L\text{ mean}} = \frac{V_s \text{ max}}{\pi}$$

$$I_{L\text{ mean}} = \frac{V_{L\text{ mean}}}{R}$$

$$V_{o\text{ rms}} = \sqrt{\frac{1}{T} \int_0^T f(t)^2 dt}$$

$$V_{o\text{ rms}} = \sqrt{\frac{1}{2\pi} \int_0^\pi (V_s \text{ max } \sin\theta)^2 d\theta}$$

$$V_{o\text{ rms}} = \sqrt{\frac{V_s \text{ max}^2}{2\pi} \int_0^\pi \sin^2\theta d\theta}$$

$$V_{o\text{ rms}} = \sqrt{\frac{V_s \text{ max}^2}{2\pi} \int_0^\pi \sin^2\theta d\theta}$$

Hint $\sin^2\theta = \frac{1}{2}(1 - \cos 2\theta)$

$$V_{o\text{ rms}} = \sqrt{\frac{V_s \text{ max}^2}{2\pi} \int_0^\pi \frac{1}{2}(1 - \cos 2\theta) d\theta}$$

$$V_{o\text{ rms}} = \sqrt{\frac{V_s \text{ max}^2}{2\pi} \cdot \frac{1}{2} \int_0^\pi (1 - \cos 2\theta) d\theta}$$


$$V_{o\text{ rms}} = \sqrt{\frac{V_s \text{ max}^2}{2\pi} \cdot \frac{1}{2} \cdot (\theta - \frac{1}{2} \sin 2\theta) \Big|_0^\pi}$$

$$V_{o\text{ rms}} = \sqrt{\frac{V_s \text{ max}^2}{2\pi} \cdot \frac{1}{2} \cdot (\pi - \frac{1}{2} \sin 2\pi - [0 - \frac{1}{2} \sin 0])}$$

$$V_{o\text{ rms}} = \sqrt{\frac{V_s \text{ max}^2}{2\pi} \cdot \frac{\pi}{2}} \Rightarrow V_{o\text{ rms}} = \sqrt{\frac{V_s \text{ max}^2}{4}}$$

$$V_{o\text{ rms}} = \frac{V_s \text{ max}}{2}$$
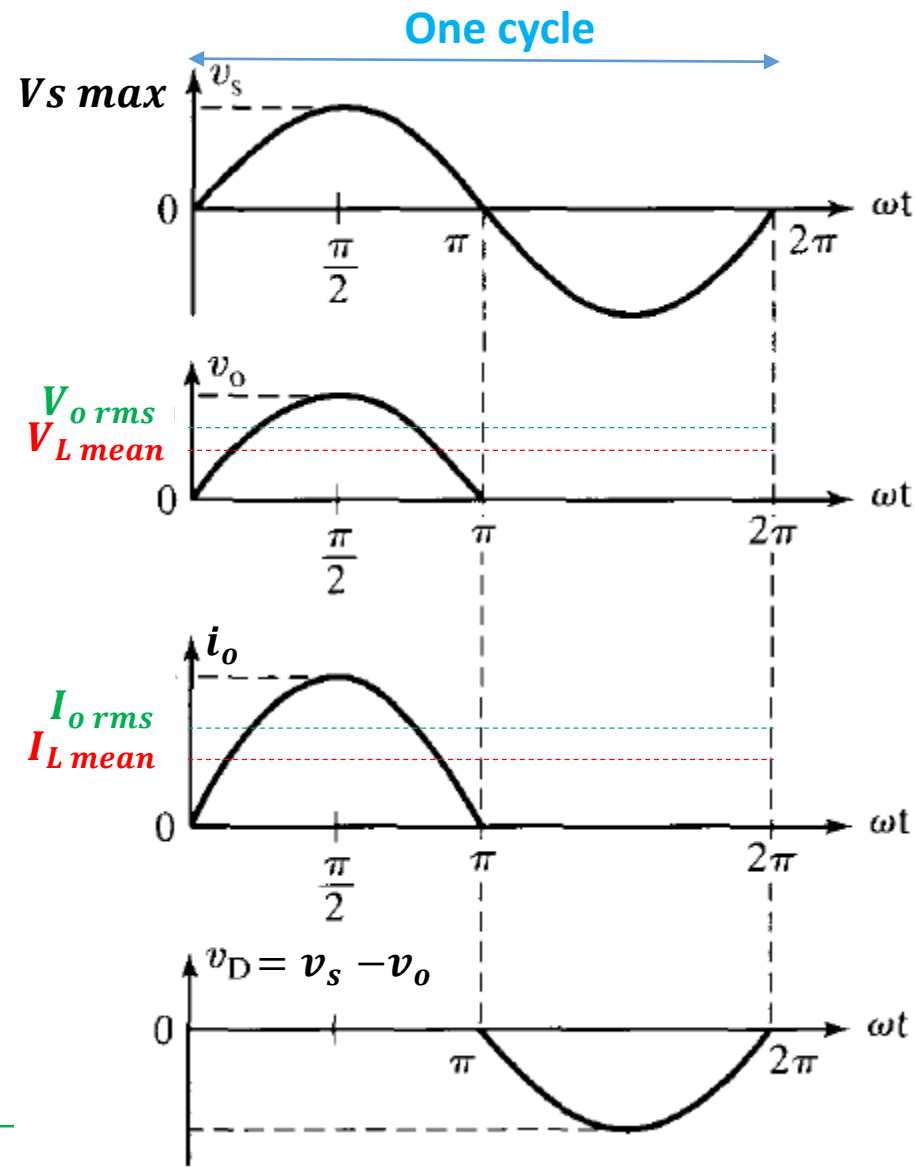
$$I_{o\text{ rms}} = \frac{V_{o\text{ rms}}}{R}$$



$$\text{Form Factor, } FF = \frac{V_{rms}}{V_{L\text{ mean}}}$$

$$\text{Ripple Factor, } RF = \sqrt{\left(\frac{V_{rms}}{V_{L\text{ mean}}}\right)^2 - 1}$$

$$RF = \sqrt{FF^2 - 1}$$

$$\text{Rectification efficiency } \eta = \frac{P_{dc}}{P_{ac}} = \frac{I_{L\text{ mean}}V_{L\text{ mean}}}{I_{o\text{ rms}}V_{o\text{ rms}}}$$

$V_{L\text{ mean}}$ or V_{av} or V_{DC}



Ex1: For the 1- ϕ half wave rectifier circuit shown in Figure below, $R = 1.3K\Omega$, $V_s = 150 \sin\omega t$. Calculate V_{Lmean} , I_{Lmean} , $v_{sr.m.s}$, $v_{or.m.s}$, $i_{or.m.s}$, form factor (FF) and ripple factor (RF).

Sol: الحل بعد الاشتقاق

$$V_{Lmean} = \frac{V_s \max}{\pi}$$

$$V_{Lmean} = \frac{150}{\pi}$$

$$V_{Lmean} = 47.7 \text{ V}$$

$$V_{or.m.s} = \frac{V_s \max}{2}$$

$$V_{or.m.s} = \frac{150}{2}$$

$$V_{or.m.s} = 75 \text{ V}$$

$$\text{Form Factor, } FF = \frac{V_{r.m.s}}{V_{Lmean}}$$

$$\text{Form Factor, } FF = \frac{75}{47.7} = 1.572$$

$$I_{or.m.s} = \frac{V_{or.m.s}}{R}$$

$$I_{or.m.s} = \frac{75}{1.3K}$$

$$I_{or.m.s} = 57.7 \text{ mA}$$

$$I_{Lmean} = \frac{V_{Lmean}}{R}$$

$$I_{Lmean} = \frac{47.7}{1.3K}$$

$$I_{Lmean} = 36.7 \text{ mA}$$

$$RF = \sqrt{\left(\frac{V_{r.m.s}}{V_{Lmean}}\right)^2 - 1}$$

$$RF = \sqrt{\left(\frac{75}{47.7}\right)^2 - 1}$$

$$RF = 1.213$$


$$\eta = \frac{P_{dc}}{P_{ac}} = \frac{I_{Lmean} V_{Lmean}}{I_{or.m.s} V_{or.m.s}}$$

$$\eta = \frac{P_{dc}}{P_{ac}} = \frac{36.7 \times 47.7}{57.7 \times 75}$$


$$\eta = \frac{P_{dc}}{P_{ac}} = 40\%$$

$$V_{s.r.m.s} = \frac{V_s \max}{\sqrt{2}}$$
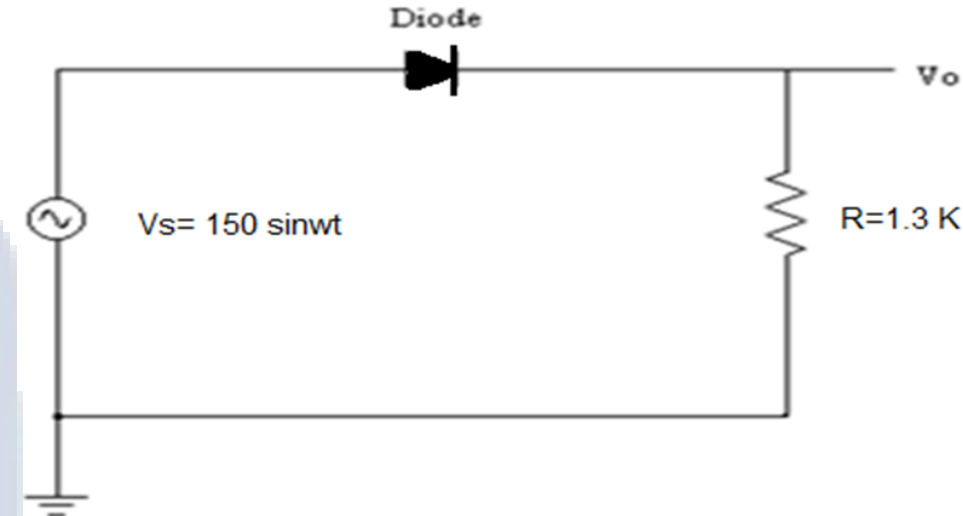
$$V_{s.r.m.s} = \frac{150}{\sqrt{2}} = 106.06 \text{ V}$$



Single phase Full wave Rectifier

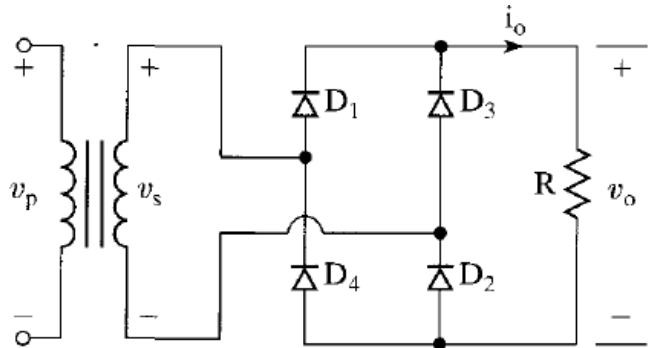

$$V_{L\text{ mean}} = \frac{1}{T} \int_0^T f(t) dt$$

$$V_{L\text{ mean}} = \frac{1}{2\pi} \int_0^\pi V_s \text{ max } \text{Sin}\theta \times 2 d\theta$$

$$V_{L\text{ mean}} = \frac{2V_s \text{ max}}{2\pi} \int_0^\pi \text{Sin}\theta d\theta$$

$$V_{L\text{ mean}} = \frac{V_s \text{ max}}{\pi} \cdot -\cos\theta \Big|_0^\pi$$

$$V_{L\text{ mean}} = \frac{V_s \text{ max}}{\pi} \cdot -(-1 - 1)$$

$$V_{L\text{ mean}} = \frac{V_s \text{ max}}{\pi} \cdot 2$$

$$V_{L\text{ mean}} = \frac{2V_s \text{ max}}{\pi}$$

$$I_{L\text{ mean}} = \frac{V_{L\text{ mean}}}{R}$$

$$V_{o\text{ rms}} = \sqrt{\frac{1}{T} \int_0^T f(t)^2 dt}$$

$$V_{o\text{ rms}} = \sqrt{\frac{1}{2\pi} \int_0^\pi (V_s \text{ max } \text{Sin}\theta)^2 \times 2 d\theta}$$

$$V_{o\text{ rms}} = \sqrt{\frac{2V_s \text{ max}^2}{2\pi} \int_0^\pi \text{Sin}\theta^2 d\theta}$$

$$V_{o\text{ rms}} = \sqrt{\frac{V_s \text{ max}^2}{\pi} \int_0^\pi \text{Sin}\theta^2 d\theta}$$

Hint $\text{Sin}\theta^2 = \frac{1}{2}(1 - \text{Cos}2\theta)$

$$V_{o\text{ rms}} = \sqrt{\frac{V_s \text{ max}^2}{\pi} \int_0^\pi \frac{1}{2}(1 - \text{Cos}2\theta) d\theta}$$

$$V_{o\text{ rms}} = \sqrt{\frac{V_s \text{ max}^2}{\pi} \cdot \frac{1}{2} \int_0^\pi (1 - \text{Cos}2\theta) d\theta}$$


$$V_{o\text{ rms}} = \sqrt{\frac{V_s \text{ max}^2}{\pi} \cdot \frac{1}{2} \cdot (\theta - \frac{1}{2} \text{Sin}2\theta) \Big|_0^\pi}$$

$$V_{o\text{ rms}} = \sqrt{\frac{V_s \text{ max}^2}{\pi} \cdot \frac{1}{2} \cdot (\pi - \frac{1}{2} \text{Sin}2\pi - [0 - \frac{1}{2} \text{Sin}0])}$$

$$V_{o\text{ rms}} = \sqrt{\frac{V_s \text{ max}^2}{\pi} \cdot \frac{\pi}{2}} \Rightarrow V_{o\text{ rms}} = \sqrt{\frac{V_s \text{ max}^2}{2}}$$

$$V_{o\text{ rms}} = \frac{V_s \text{ max}}{\sqrt{2}}$$
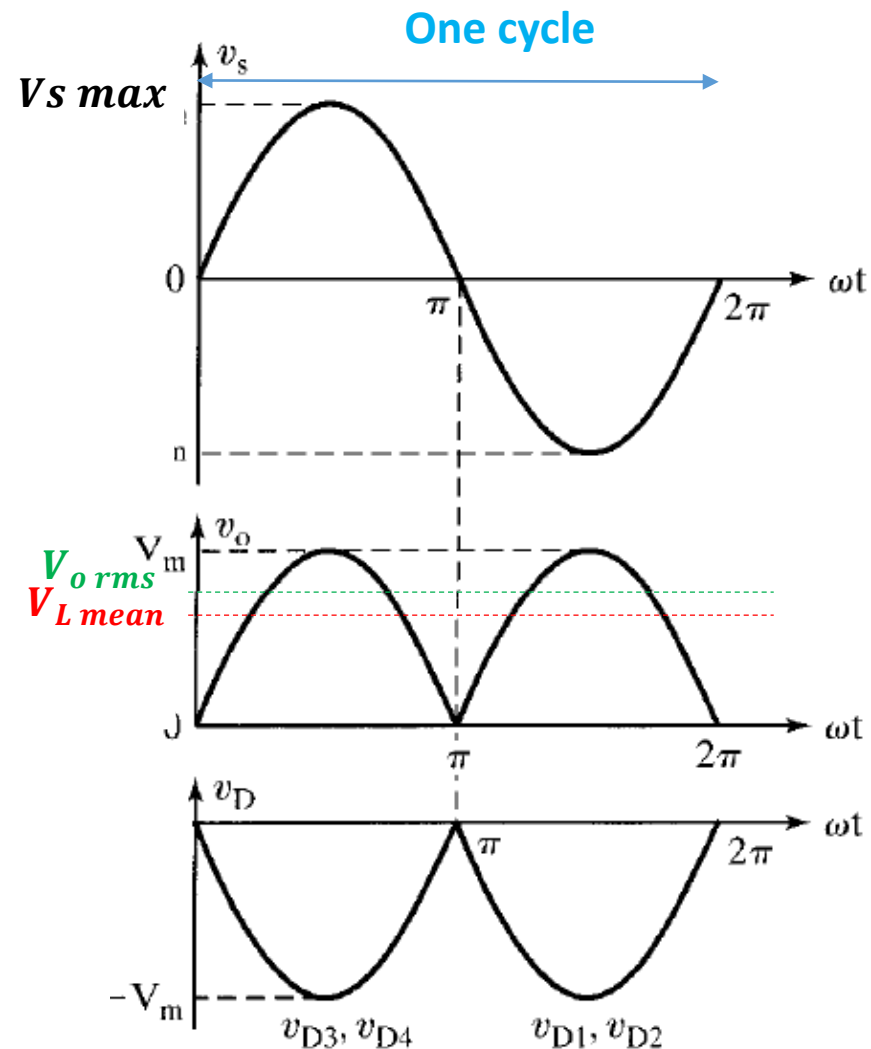
$$I_{o\text{ rms}} = \frac{V_{o\text{ rms}}}{R}$$



$$\text{Form Factor, } FF = \frac{V_{rms}}{V_{L\text{ mean}}}$$

$$\text{Ripple Factor, } RF = \sqrt{\left(\frac{V_{rms}}{V_{L\text{ mean}}}\right)^2 - 1}$$

$$RF = \sqrt{FF^2 - 1}$$

$$\text{Rectification efficiency } \eta = \frac{P_{dc}}{P_{ac}} = \frac{I_{L\text{ mean}}V_{L\text{ mean}}}{I_{o\text{ rms}}V_{o\text{ rms}}}$$

$V_{L\text{ mean}}$ or V_{av} or V_{DC}



Ex2: For the 1- ϕ full wave rectifier circuit shown in Figure below, $R = 10k\Omega$, $V_{smax} = 200$ volt. Determine V_{Lmean} , I_{Lmean} , v_{orms} , i_{orms} , RF and rectifier efficiency.

Sol: الحل بعد الاشتقاق

$$V_{Lmean} = \frac{2V_{smax}}{\pi}$$

$$V_{Lmean} = \frac{2(200)}{\pi}$$

$$V_{Lmean} = 127.3 V$$

$$I_{Lmean} = \frac{V_{Lmean}}{R}$$

$$I_{Lmean} = \frac{127.3}{10 K}$$

$$I_{Lmean} = 12.73 mA$$

$$V_{orms} = \frac{V_{smax}}{\sqrt{2}}$$

$$V_{orms} = \frac{200}{\sqrt{2}}$$

$$V_{orms} = 141.4 V$$

$$I_{orms} = \frac{V_{orms}}{R}$$

$$I_{orms} = \frac{141.4}{10 K}$$

$$I_{orms} = 14.14 mA$$


$$\text{Form Factor, } FF = \frac{V_{rms}}{V_{Lmean}}$$

$$\text{Form Factor, } FF = \frac{141.4}{127.3} = 1.11$$

$$RF = \sqrt{\left(\frac{V_{rms}}{V_{Lmean}}\right)^2 - 1}$$

$$RF = \sqrt{\left(\frac{141.4}{127.3}\right)^2 - 1}$$

$$RF = 0.48$$

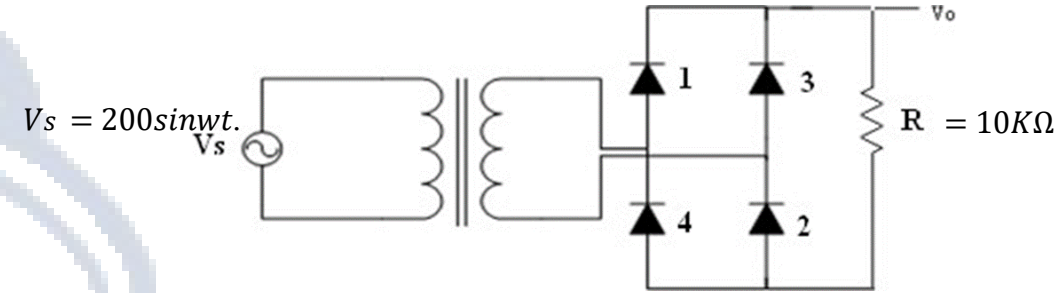

$$\eta = \frac{P_{dc}}{P_{ac}} = \frac{I_{Lmean} V_{Lmean}}{I_{orms} V_{orms}}$$

$$\eta = \frac{P_{dc}}{P_{ac}} = \frac{12.73 \times 127.3}{14.14 \times 141.4}$$

$$\eta = \frac{P_{dc}}{P_{ac}} = 80\%$$

Summary

Comparison between half wave rectifier and full wave rectifier :

Half wave rectifier	Full wave rectifier
$V_s \text{ rms} = \frac{V_s \text{ max}}{\sqrt{2}}$	$V_s \text{ rms} = \frac{V_s \text{ max}}{\sqrt{2}}$
$V_L \text{ mean} = \frac{V_s \text{ max}}{\pi}$	$V_L \text{ mean} = \frac{2V_s \text{ max}}{\pi}$
$I_L \text{ mean} = \frac{V_L \text{ mean}}{R}$	$I_L \text{ mean} = \frac{V_L \text{ mean}}{R}$
$V_o \text{ rms} = \frac{V_s \text{ max}}{2}$	$V_o \text{ rms} = \frac{V_s \text{ max}}{\sqrt{2}}$
$I_o \text{ rms} = \frac{V_o \text{ rms}}{R}$	$I_o \text{ rms} = \frac{V_o \text{ rms}}{R}$
$FF = \frac{V_{rms}}{V_L \text{ mean}}$	$FF = \frac{V_{rms}}{V_L \text{ mean}}$
$RF = \sqrt{FF^2 - 1}$	$RF = \sqrt{FF^2 - 1}$
$\eta = \frac{P_{dc}}{P_{ac}} = \frac{I_L \text{ mean} V_L \text{ mean}}{I_o \text{ rms} V_o \text{ rms}}$	$\eta = \frac{P_{dc}}{P_{ac}} = \frac{I_L \text{ mean} V_L \text{ mean}}{I_o \text{ rms} V_o \text{ rms}}$