



Ministry of Higher Education  
University of Al-Maarif  
Medical Instruments Engineering Techniques Department



# Medical electronic systems

*For  
Students of Third class*



Unit ONE  
Regulated power supplied (PART 2)  
**DC Filtration Stage**

By  
**Mr. Abdulla Saleh**

# DC Filtration (Capacitor Filter)

- Rectified voltage from rectifier has **high ripple content**.
- Desired output is a pure, **ripple-free** DC waveform.
- Filters** are used to remove ripples.
- Types of filters: **capacitor filter**, **LC filter**, **choke input filter**,  **$\pi$  type filter**.
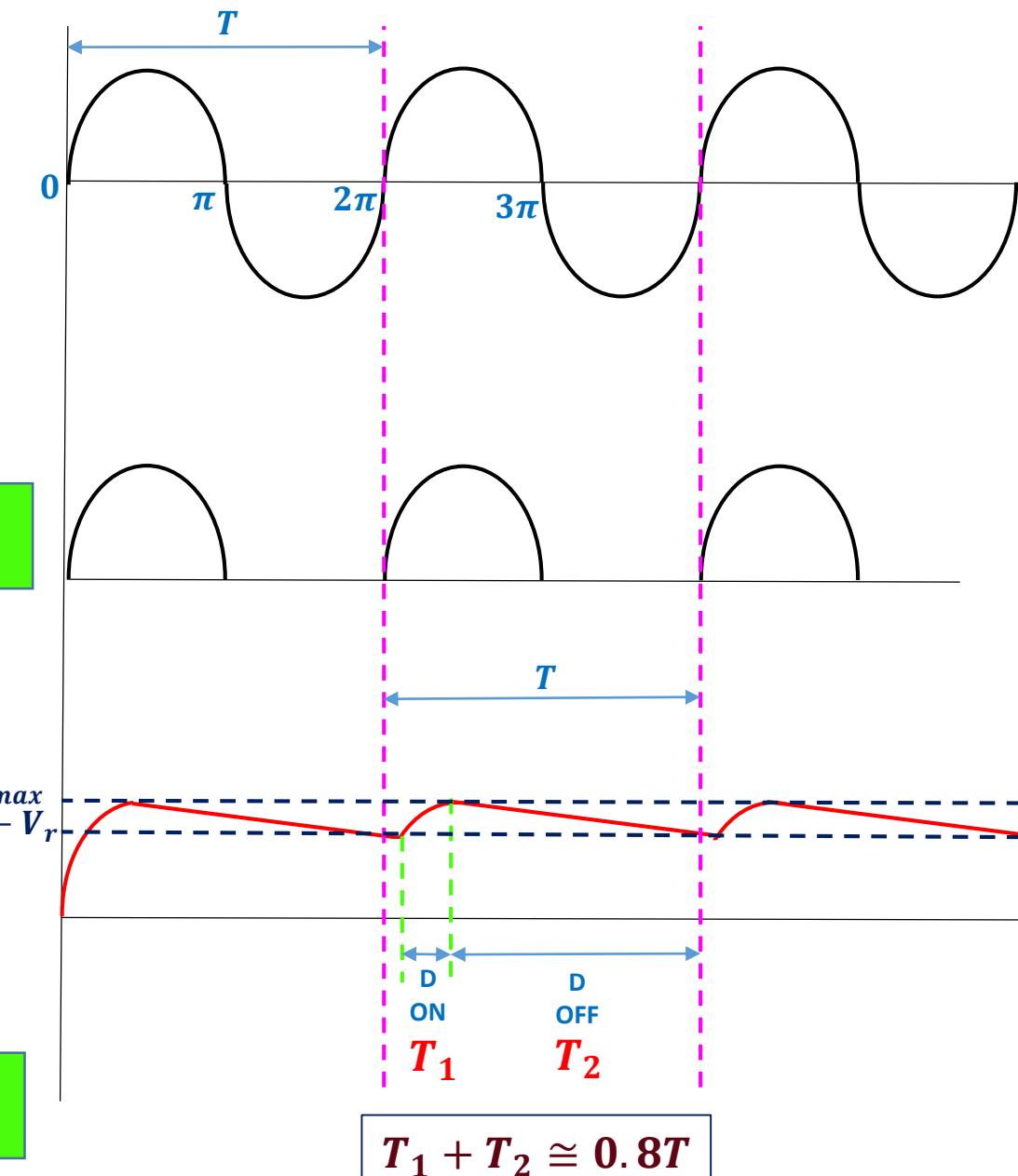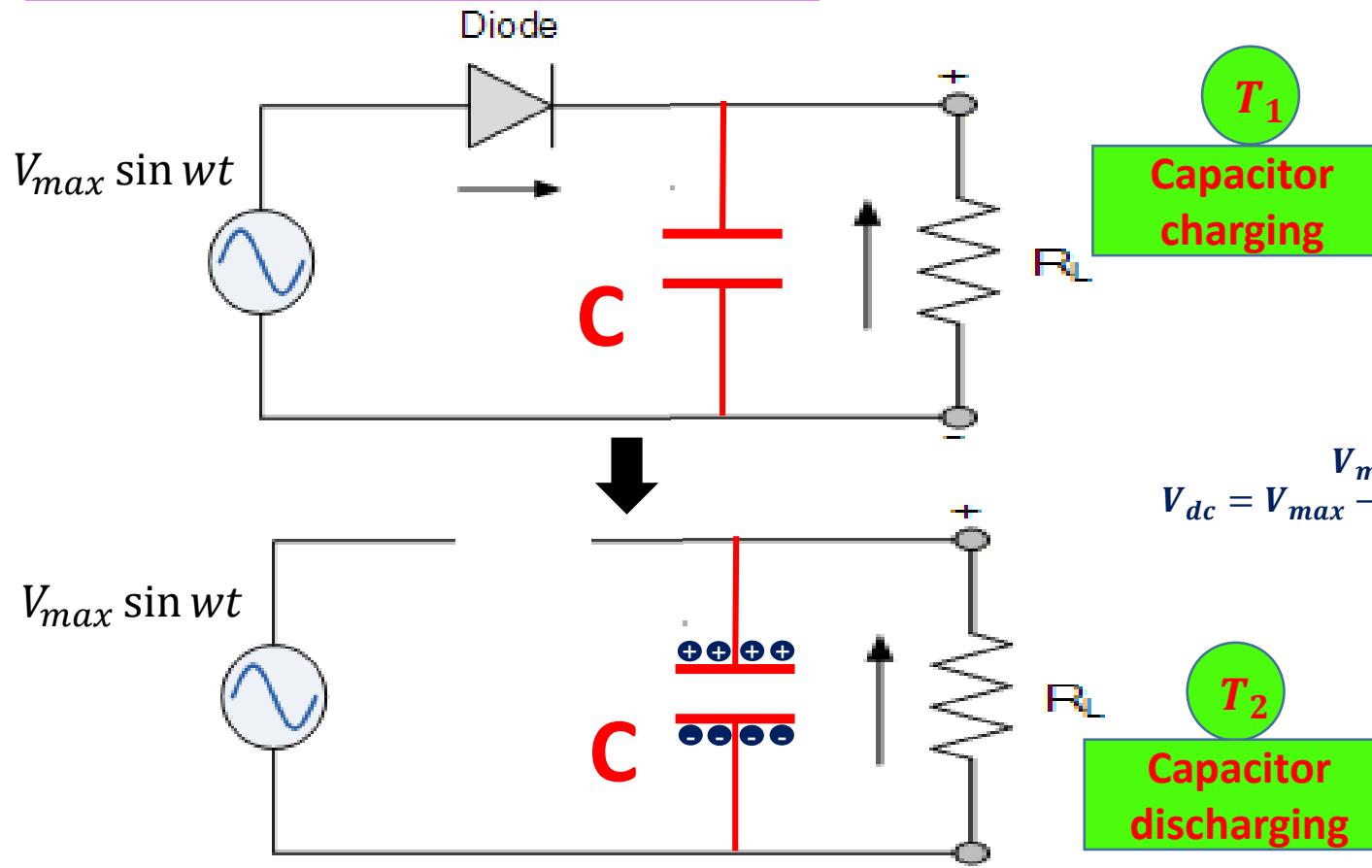
## half-wave rectifier with capacitor Filter



$$T_2 \gg T_1$$

$$T_2 \cong 0.8T$$

At  $T_2$  (discharging of C), the charge lost

$$Q = C V_{r(p.p)} \dots (1)$$

The current through C

$$i = \frac{dQ}{dt} \rightarrow dQ = idt \rightarrow \int dQ = \int_0^{T_2} idt \rightarrow Q = i \int_0^{T_2} dt$$

$$Q = I_{dc} t \Big|_0^{T_2} \rightarrow Q = I_{dc} T_2 \dots (2) \rightarrow \text{sub (2) in (1)}$$

$$\rightarrow I_{dc} T_2 = C V_{r(p.p)} \quad T_2 \cong 0.8T$$

$$I_{dc} \times 0.8T = C V_{r(p.p)} \quad \div C \rightarrow V_{r(p.p)} = \frac{I_{dc} \times 0.8T}{C}$$

$$V_{r(p.p)} = I_{dc} \times T \times \frac{0.8}{C} \rightarrow V_{r(p.p)} = \frac{V_{dc}}{R_l} \times \frac{1}{F} \times \frac{0.8}{C}$$

$$V_{r(p.p)} = \frac{V_{dc} \times 0.8}{R_l F C} \quad \div 0.8 \quad \div 0.8$$


$$V_{r(p.p)} = \frac{V_{dc}}{1.25 R_l F C} \dots (3)$$

$$V_{dc} = V_{max} - V_{r(p)} \dots (4)$$

$$V_{r(p)} = \frac{V_{r(p.p)}}{2} \dots (5)$$

$$V_{dc} = V_{max} - \frac{V_{r(p.p)}}{2} \dots (6)$$

sub (5) in (4)  $\rightarrow$

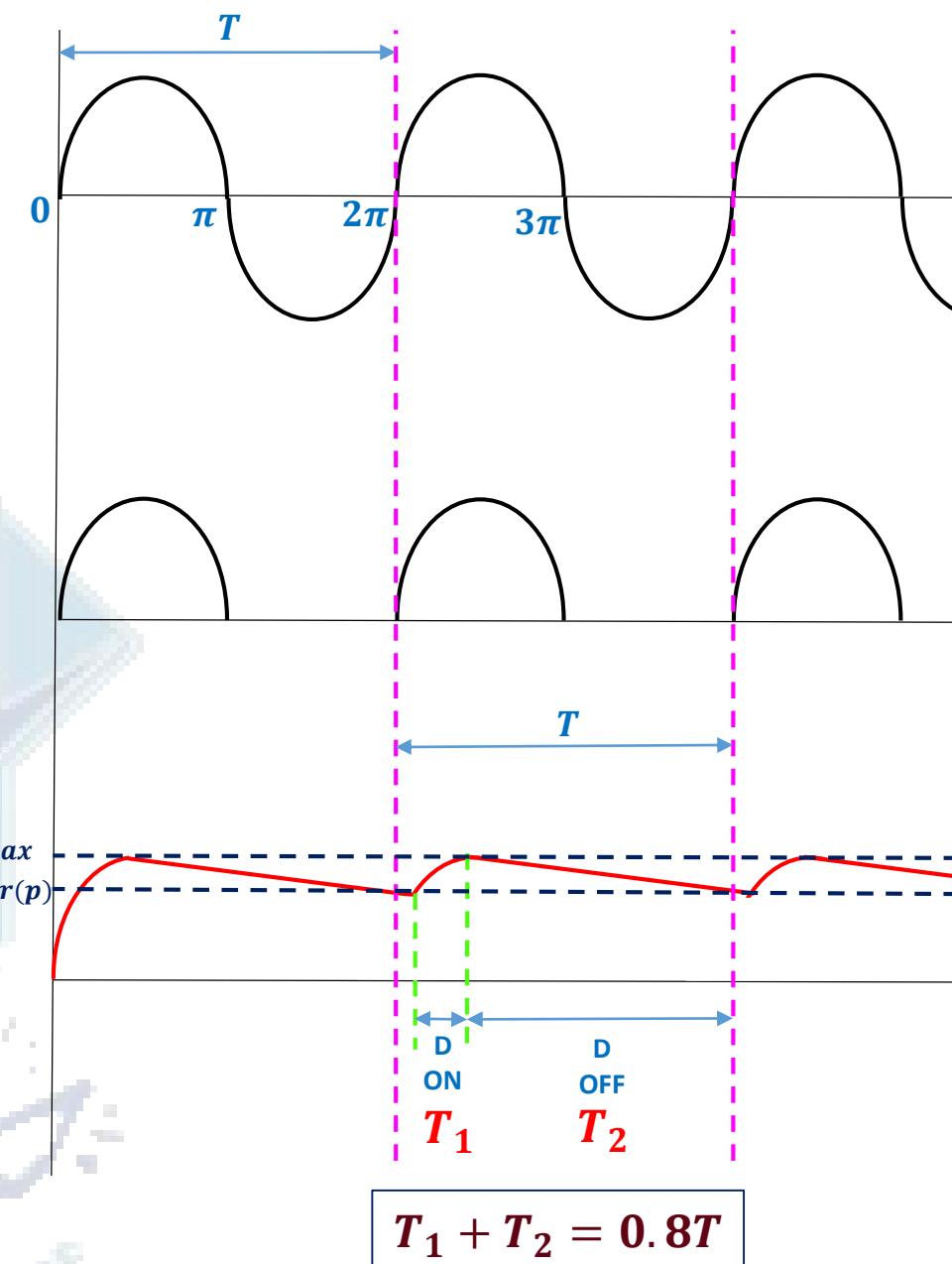

$$T_1 + T_2 = 0.8T$$

from above equations sub (3) in (6)

$$V_{rp.p} = \frac{V_{dc}}{1.25R_lFC} \dots (3)$$

$$V_{dc} = V_{max} - \frac{V_{dc}}{2.5R_lFC}$$

$$V_{dc} + \frac{V_{dc}}{2.5R_lFC} = V_{max} \Rightarrow V_{dc}(1 + \frac{1}{2.5R_lFC}) = V_{max}$$

$$V_{dc} = \frac{V_{max}}{1 + \frac{1}{2.5R_lFC}}$$

The r.m.s Voltage equal to :

$$V_{rms} = \frac{V_{rp.p}}{2\sqrt{3}}$$

Ripplefactor

$$R.F = \frac{V_{rms}}{V_{dc}}$$

$$\frac{V_{rp.p}}{2\sqrt{3}}$$

$$R.F = \frac{V_{rms}}{V_{dc}}$$

$$R.F = \frac{V_{rp.p}}{2\sqrt{3}}$$

$$R.F = \frac{V_{rp.p}}{2\sqrt{3}V_{dc}}$$

$$R.F = \frac{V_{rp.p}}{2\sqrt{3}V_{dc}}$$

$$R.F = \frac{\frac{V_{dc}}{1.25R_lFC}}{2\sqrt{3}V_{dc}}$$

$$R.F = \frac{1}{2.5\sqrt{3}R_lFC}$$

## Summary

$$V_s \text{ rms} = \frac{V_s \text{ max}}{\sqrt{2}}$$

$$V_{dc} = \frac{V_{max}}{1 + \frac{1}{2.5R_lFC}}$$

$$V_r(p.p) = \frac{V_{dc}}{1.25R_lFC}$$

$$V_{r(p)} = \frac{V_r(p.p)}{2}$$

$$R.F = \frac{1}{2.5\sqrt{3}R_lFC}$$

Ex1: For the half-wave rectifier circuit below, determine  $V_{dc}$ ,  $V_r$  (p.p) and ripple factor ( $r$ )

Sol:

$$V_s \text{ rms} = \frac{V_s \text{ max}}{\sqrt{2}}$$

$$24 = \frac{V_s \text{ max}}{\sqrt{2}}$$

$$V_s \text{ max} = 24\sqrt{2}$$

$$V_s \text{ max} = 33.94V$$


i

$$V_{dc} = \frac{V_{max}}{1 + \frac{1}{2.5R_lFC}}$$

$$V_{dc} = \frac{33.94V}{1 + \frac{1}{2.5 * 220 * 50 * 100 * 10^{-6}}}$$

$$V_{dc} = 24.96 V$$

$V_s \text{ rms} = 24V$   
50HZ

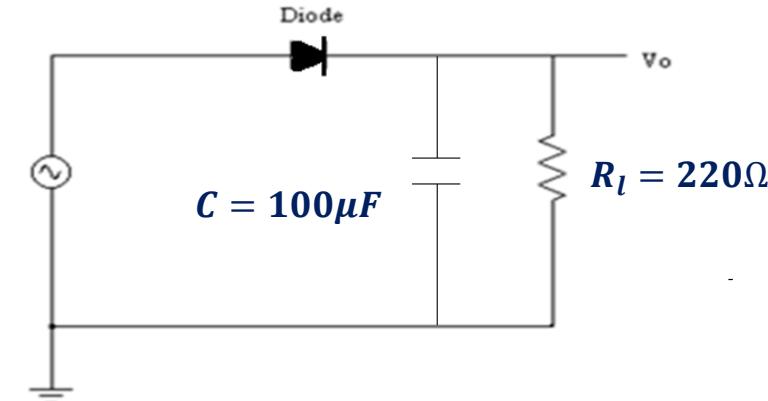

ii

$$V_r(p.p) = \frac{V_{dc}}{1.25R_lFC}$$

$$24.96$$

$$V_r(p.p) = \frac{1.25 * 220 * 50 * 100 * 10^{-6}}{1.25 * 220 * 50 * 100 * 10^{-6}}$$

$$V_r(p.p) = 18.1 V$$


iii

$$R.F = \frac{1}{2.5\sqrt{3}R_lFC}$$


$$R.F = \frac{1}{2.5\sqrt{3} * 220 * 50 * 100 * 10^{-6}}$$

$$R.F = 0.21$$

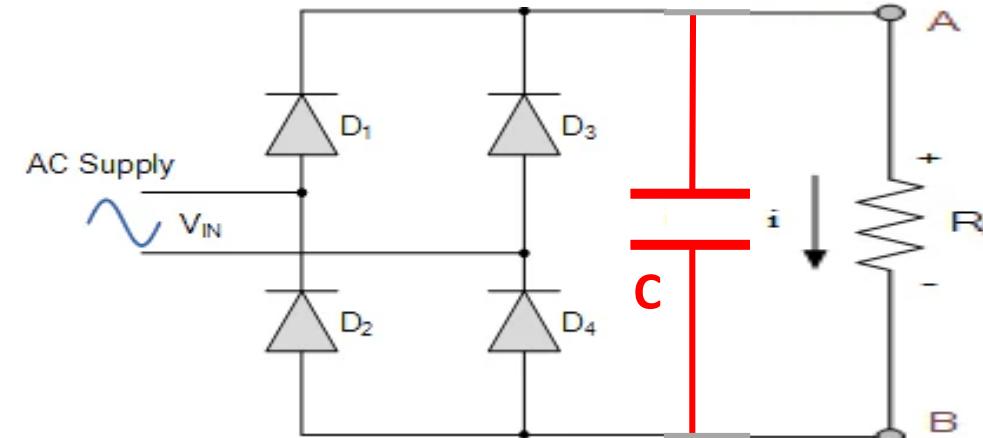
## full-wave rectifier with capacitor Filter



$T_1$   
Capacitor charging

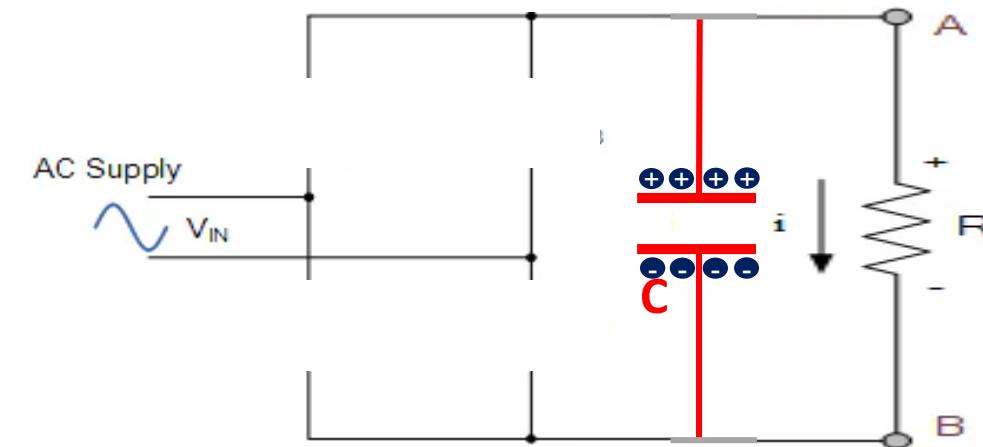

$T_2$   
Capacitor discharging

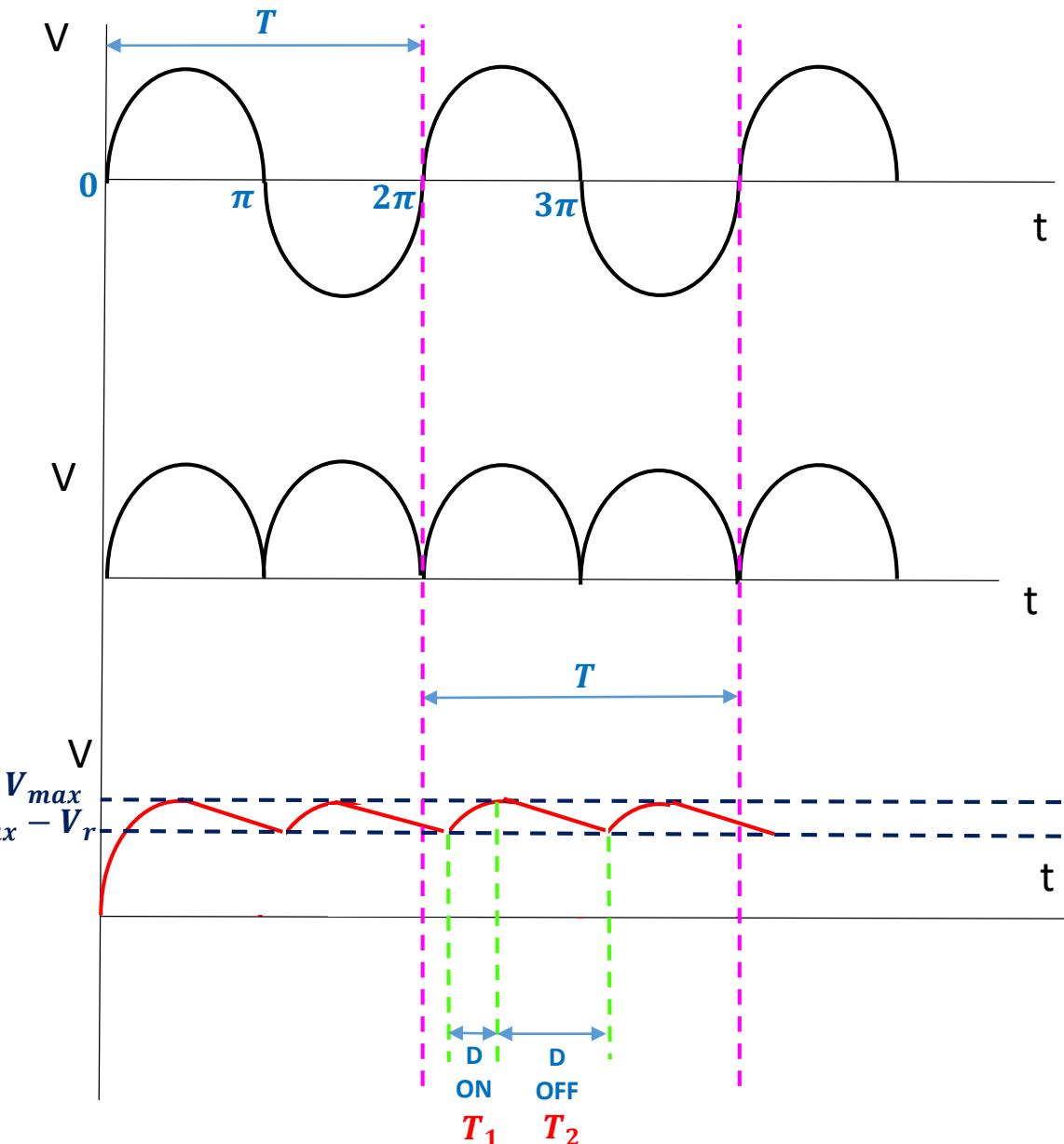

$$T_1 + T_2 = \frac{T}{2}$$

$$T_2 \gg T_1$$

$$T_2 \cong \frac{T}{2}$$

At  $T_2$  (discharging of C), the charge lost

$$Q = C V_{r(p.p)} \dots (1)$$

The current through C

$$i = \frac{dQ}{dt} \rightarrow dQ = idt \rightarrow \int dQ = \int_0^{T_2} idt \rightarrow Q = i \int_0^{T_2} dt$$

$$Q = I_{dc} t \Big|_0^{T_2} \rightarrow Q = I_{dc} T_2 \dots (2) \rightarrow \text{sub (2) in (1)}$$

$$\rightarrow I_{dc} T_2 = C V_{r(p.p)} \quad T_2 \cong \frac{T}{2}$$

$$I_{dc} \times \frac{T}{2} = C V_{r(p.p)} \quad \div C \rightarrow$$

$$V_{r(p.p)} = \frac{I_{dc} \times T}{2C}$$

$$V_{r(p.p)} = I_{dc} \times T \times \frac{1}{2C} \rightarrow V_{r(p.p)} = \frac{V_{dc}}{R_l} \times \frac{1}{F} \times \frac{1}{2C}$$

$$V_{r(p.p)} = \frac{V_{dc}}{2R_l F C}$$


$$V_{dc} = V_{max} - V_{r(p)} \dots (4)$$

$$V_{r(p.p)} = \frac{V_{dc}}{2R_l F C} \dots (3)$$

$$V_{r(p)} = \frac{V_{r(p.p)}}{2} \dots (5)$$

$$V_{dc} = V_{max} - \frac{V_{r(p.p)}}{2} \dots (6)$$

sub (5) in (4)  $\rightarrow$

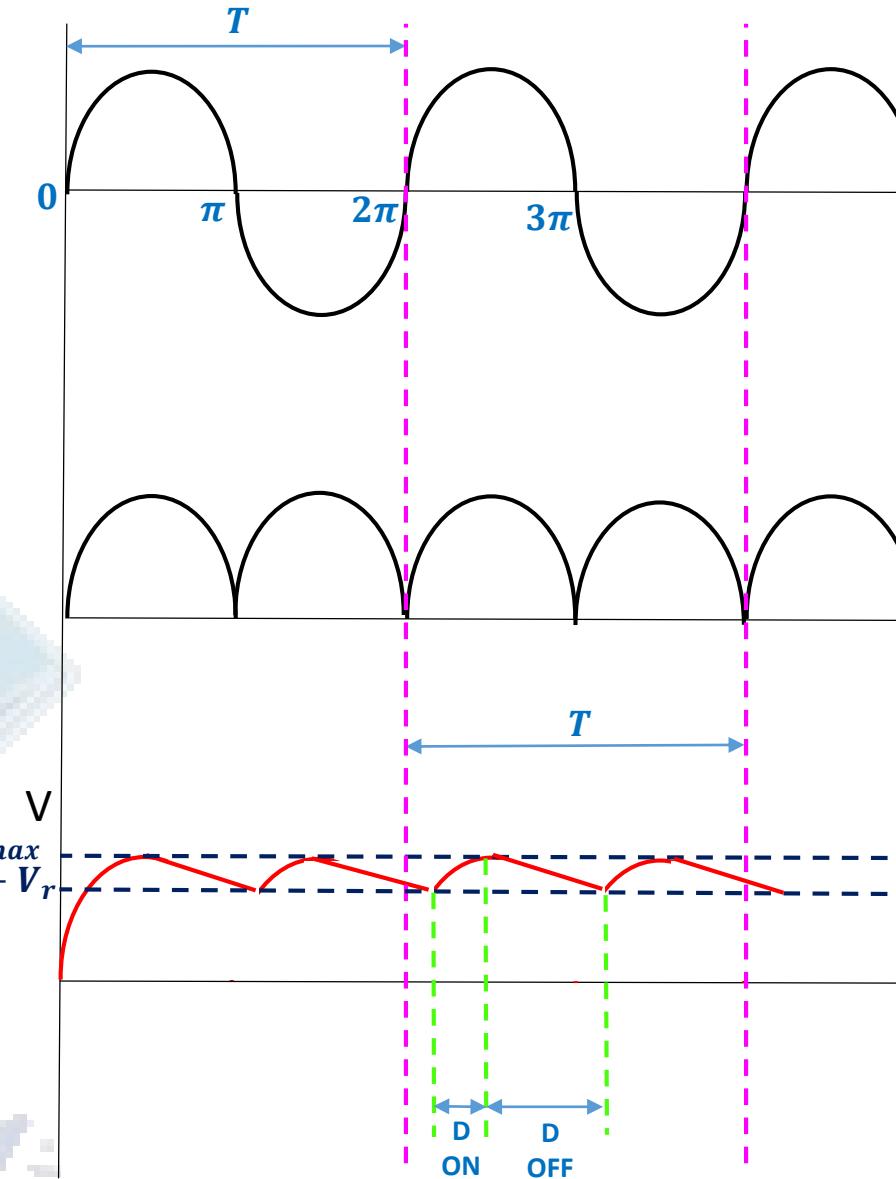

$$T_1 + T_2 = \frac{T}{2}$$

from above equations sub (3) in (6)

$$V_{r(p.p)} = \frac{V_{dc}}{2R_lFC} \dots (3)$$

$$V_{dc} = V_{max} - \frac{V_{dc}}{2R_lFC}$$

$$V_{dc} + \frac{V_{dc}}{4R_lFC} = V_{max}$$

$$V_{dc} = \frac{V_{max}}{1 + \frac{1}{4R_lFC}}$$

The r.m.s Voltage equal to :

$$V_{rms} = \frac{V_{r(p.p)}}{2\sqrt{3}}$$

$$V_{dc} = V_{max} - \frac{V_{r(p.p)}}{2} \dots (6)$$

$$V_{dc} = V_{max} - \frac{V_{dc}}{4R_lFC}$$

$$V_{dc}\left(1 + \frac{1}{4R_lFC}\right) = V_{max}$$

Ripplefactor

$$R.F = \frac{V_{rms}}{V_{dc}}$$

$$R.F = \frac{V_{r(p.p)}}{2\sqrt{3}}$$

$$\frac{V_{r(p.p)}}{2\sqrt{3}}$$

$$R.F = \frac{V_{rms}}{V_{dc}}$$

$$R.F = \frac{V_{r(p.p)}}{2\sqrt{3}}$$

$$R.F = \frac{V_{r(p.p)}}{2\sqrt{3}V_{dc}}$$

$$R.F = \frac{V_{r(p.p)}}{2\sqrt{3}V_{dc}}$$

$$R.F = \frac{\cancel{V_{dc}}}{2\sqrt{3}\cancel{V_{dc}}} \frac{2R_lFC}{2\sqrt{3}}$$

$$R.F = \frac{1}{4\sqrt{3}R_lFC}$$

## Summary

$$V_s \text{ rms} = \frac{V_s \text{ max}}{\sqrt{2}}$$

$$V_{dc} = \frac{V_{max}}{1 + \frac{1}{4R_lFC}}$$

$$Vr(p.p) = \frac{V_{dc}}{2R_lFC}$$

$$V_{r(p)} = \frac{Vr(p.p)}{2}$$

$$R.F = \frac{1}{4\sqrt{3}R_lFC}$$

Ex3: For the full-wave rectifier circuit below, determine  $V_r$  (p.p),  $V_{dc}$  and ripple factor ( $r$ )

Sol:

$$V_{s1 \text{ rms}} = \frac{V_{s1 \text{ max}}}{\sqrt{2}}$$

$$120 = \frac{V_{s1 \text{ max}}}{\sqrt{2}}$$


$$V_{s1 \text{ max}} = 120\sqrt{2}$$

$$V_{s1 \text{ max}} = 169.71 \text{ V}$$

$$\frac{V_{s1 \text{ max}}}{V_{s2 \text{ max}}} = \frac{n_1}{n_2}$$

$$\frac{169.71}{V_{s2 \text{ max}}} = \frac{10}{1}$$
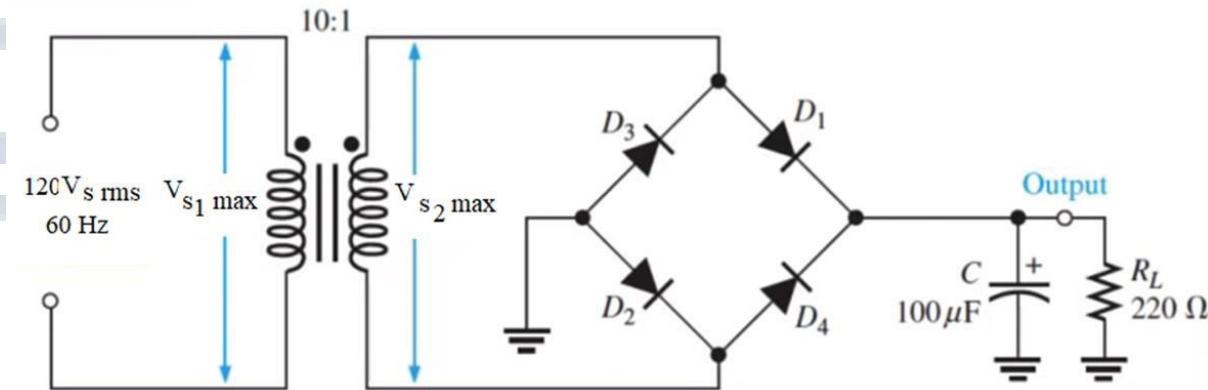
$$V_{s2 \text{ max}} = 16.971 \text{ V}$$



ii

$$Vr(p.p) = \frac{V_{dc}}{2R_lFC}$$

$$Vr(p.p) = \frac{14.2}{2 * 220 * 60 * 100 * 10^{-6}}$$

$$Vr(p.p) = 5.3 \text{ V}$$

i

$$V_{dc} = \frac{V_{max}}{1 + \frac{1}{4R_lFC}}$$

$$16.971 \text{ V}$$

$$V_{dc} = \frac{1}{1 + \frac{1}{4 * 220 * 60 * 100 * 10^{-6}}}$$

$$V_{dc} = 14.2 \text{ V}$$

iii



$$R.F = \frac{1}{4\sqrt{3}R_lFC}$$

$$R.F = \frac{1}{4\sqrt{3} * 220 * 60 * 100 * 10^{-6}}$$

$$R.F = 0.109$$

## Summary

### Comparison between capacitor filter in case of half wave rectifier and full wave rectifier
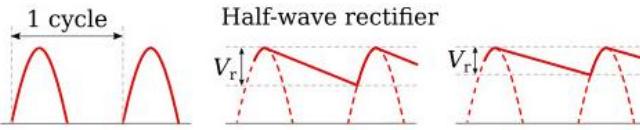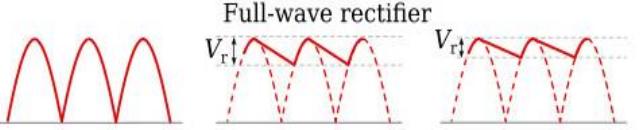
| Capacitor filter with <b>Half wave</b> rectifier   | Capacitor filter with <b>Full wave</b> rectifier  |
|--|---|
|  <p>Half-wave rectifier</p> |  <p>Full-wave rectifier</p> |
| $T_2 \approx 0.8T$   | $T_2 \approx \frac{T}{2}$   |
| $V_{r(p)} = \frac{V_{dc}}{1.25R_lCf}$  | $V_{r(p)} = \frac{V_{dc}}{2R_lCf}$  |
| $V_{dc} = \frac{V_{max}}{1 + \frac{1}{2.5R_lCf}}$  | $V_{dc} = \frac{V_{max}}{1 + \frac{1}{4R_lCf}}$   |
| $V_{rms} = \frac{V_{r(p.p)}}{2\sqrt{3}}$   | $V_{rms} = \frac{V_{r(p.p)}}{2\sqrt{3}}$  |
| $RF = \frac{1}{2.5\sqrt{3}R_lCf}$  | $RF = \frac{1}{4\sqrt{3}R_lCf}$   |