



Ministry of Higher Education
University of Al-Maarif
Medical Instruments Engineering Techniques Department



Medical electronic systems

*For
Students of Third class*



Unit ONE
Regulated power supplied (PART 3)
Regulation Stage



By
Mr. Abdulla Saleh

The Regulator

Zener Diode Regulator!




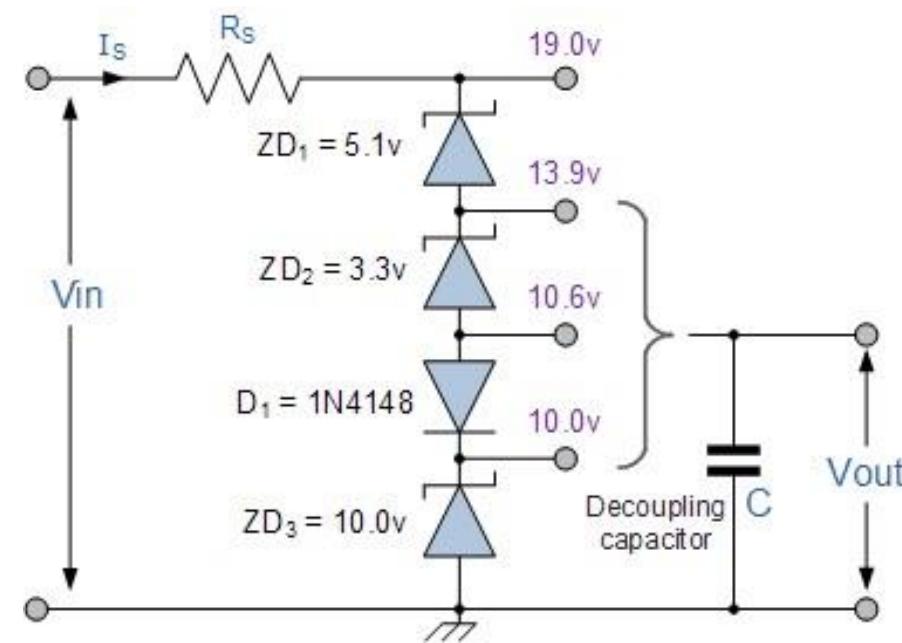
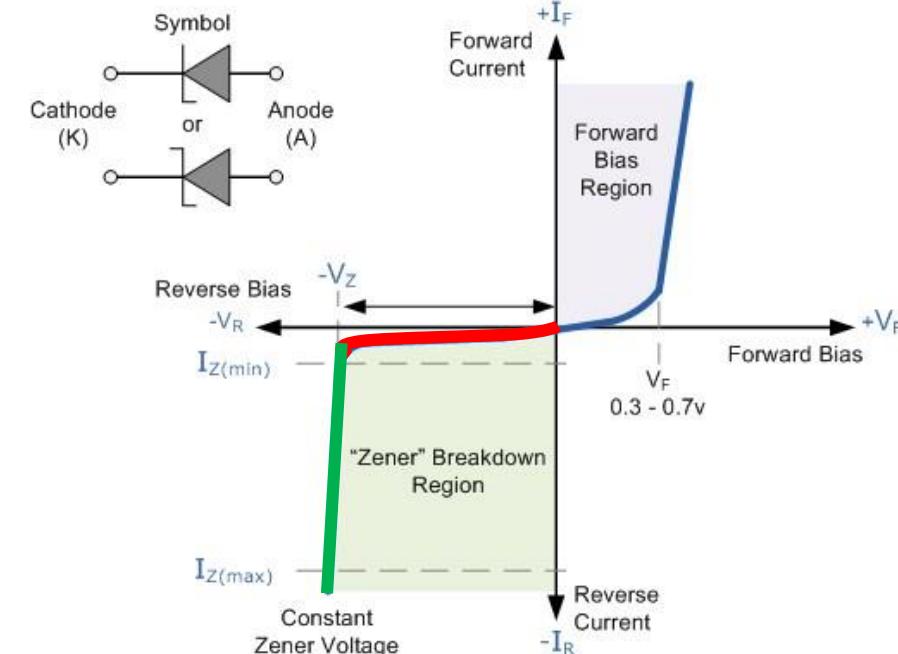
- A Zener diode allows current in the forward direction like a **regular diode**
- but also **conducts in reverse** when the voltage **exceeds** a specific **Zener breakdown voltage** (Zener voltage).
- **Common Zener diodes:** 500mW BZX55 and 1.3W BZX85, like BZX55C7V5 (7.5V).
- Zener diodes can be **series-connected** with silicon diodes for various reference voltages.



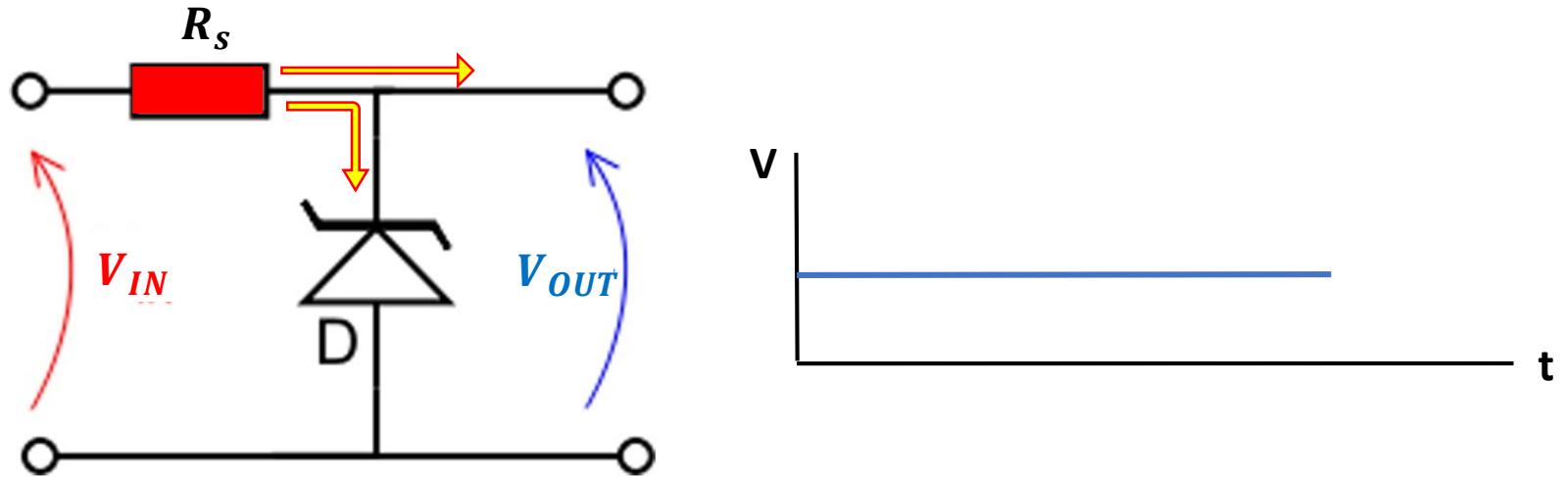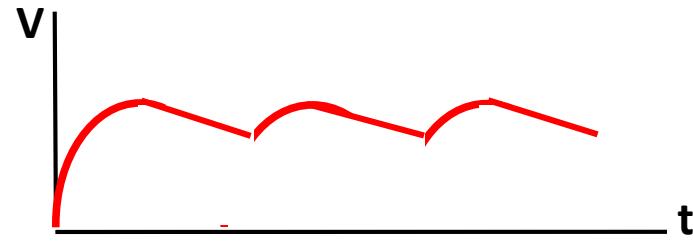


- Zener diodes provide a **stable output voltage** with **low ripple** under varying load currents.
- A current-limiting resistor (R_s) ensures the Zener diode conducts enough current to maintain V_{OUT} .
- Rectifier DC output has a **ripple**; connecting a **Zener stabilizer** circuit to the rectifier generates a more **stable voltage**.

Zener voltage V_Z

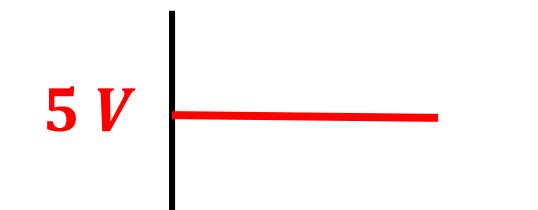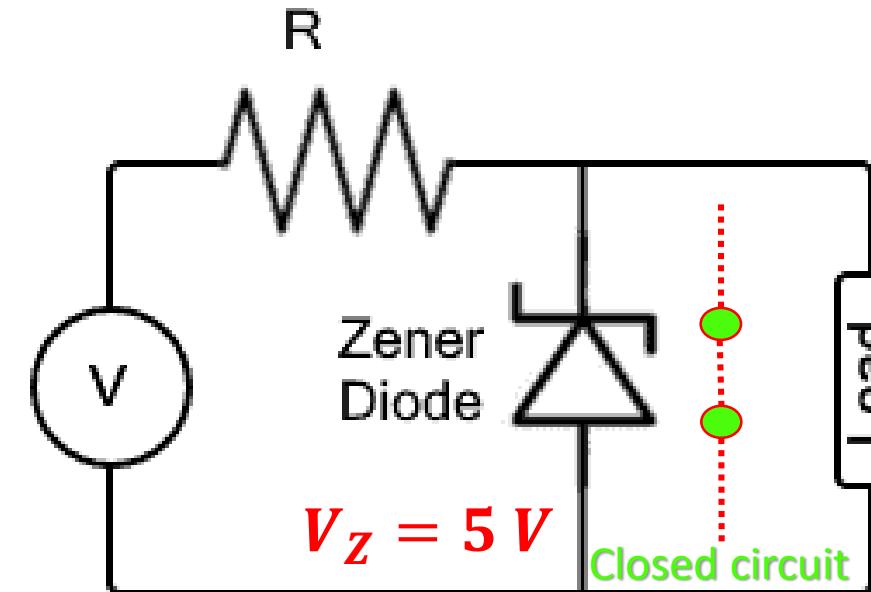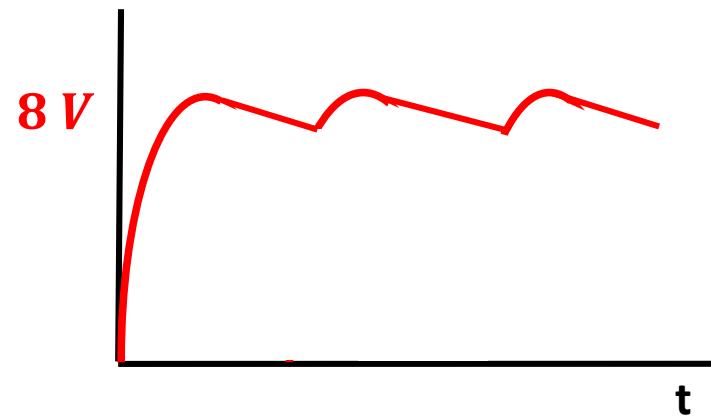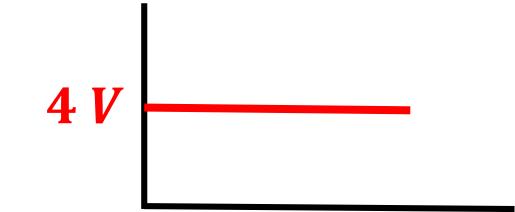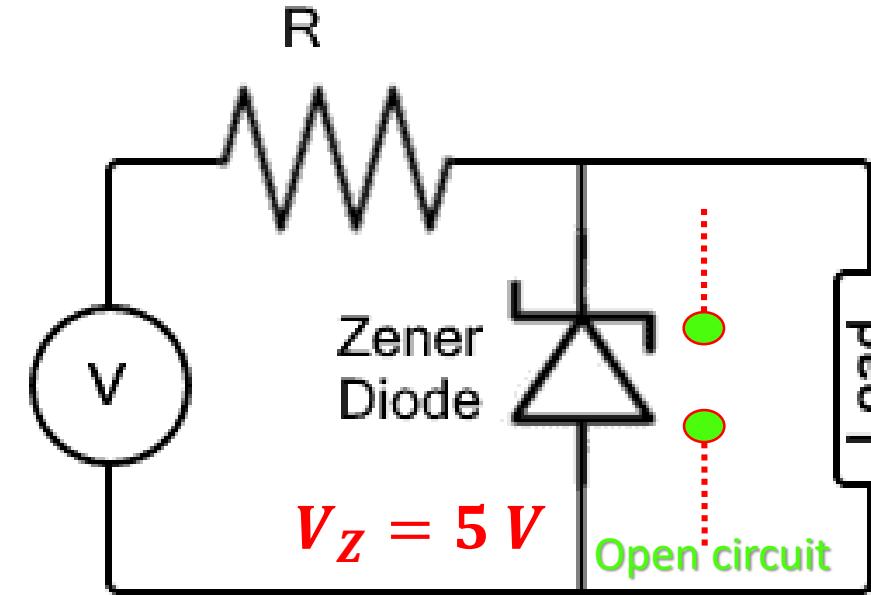

Stage 1: Fixed V_i and Fixed R_L

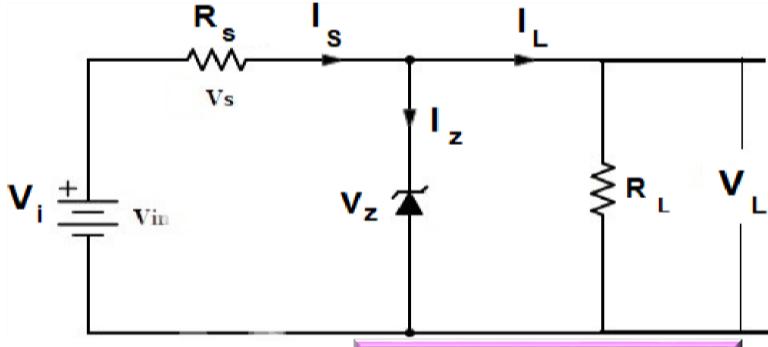

$$V_L = \frac{R_L}{R_L + R_s} V_i$$

When $V_L < V_z$ Zener is OFF

$$I_L = \frac{V_L}{R_L}$$

$$V_i - V_s - V_L = 0$$

$$I_s = \frac{V_s}{R_s}$$

$$I_z = 0$$



When $V_L > V_z$ Zener is ON

$$V_z = V_L$$


$$I_L = \frac{V_L}{R_L}$$

$$V_i - V_s - V_L = 0$$

$$I_s = \frac{V_s}{R_s}$$

$$I_z = I_s - I_L$$

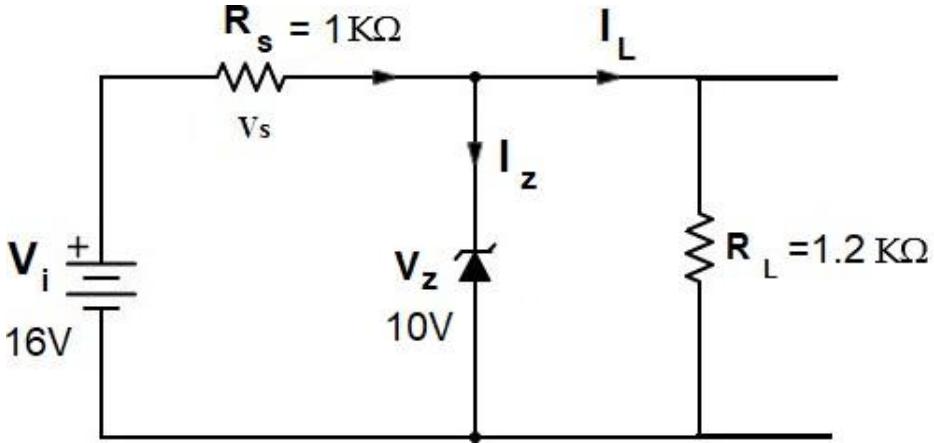EX:1 For the Zener circuit below, determine V_L , I_L , V_s , I_s and I_z



Sol:

$$\text{i} \quad V_L = \frac{R_L}{R_L + R_s} V_i \\ = \frac{1.2}{1.2 + 1} * 16$$

$$V_L = 8.72 \text{ V}$$

$\because V_L(8.72 \text{ V}) < V_z(10 \text{ V})$

Zener is OFF

$$\text{iii} \quad V_i - V_s - V_L = 0 \\ 16 - V_s - 8.72 = 0$$

$$V_s = 16 - 8.72$$

$$V_s = 7.27 \text{ V}$$

$$\text{V} \quad I_z = 0$$


$$\text{ii} \quad I_L = \frac{V_L}{R_L} \\ = \frac{8.72}{1.2 * 10^3}$$

$$I_L = 7.27 \text{ mA}$$

$$\text{IV} \quad I_s = \frac{V_s}{R_s} \\ I_s = \frac{7.27}{1 \text{ k}}$$

$$I_s = 7.27 \text{ mA}$$

Stage 1: Fixed V_i and Fixed R_L

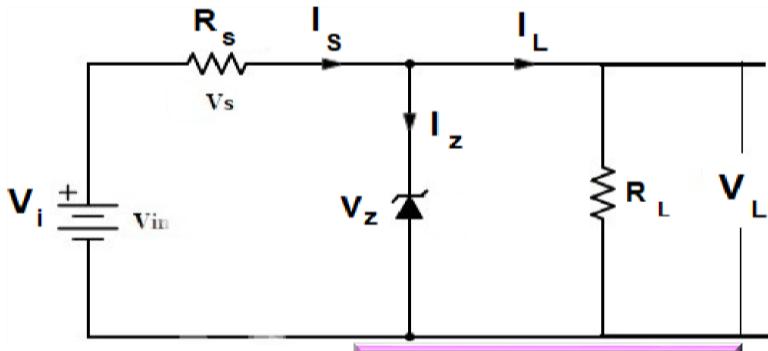

$$V_L = \frac{R_L}{R_L + R_S} V_i$$

When $V_L < V_z$ Zener is OFF

$$I_L = \frac{V_L}{R_L}$$

$$V_i - V_s - V_L = 0$$

$$I_S = \frac{V_S}{R_S}$$

$$I_z = 0$$

When $V_L > V_z$ Zener is ON

$$V_z = V_L$$

$$I_L = \frac{V_L}{R_L}$$

$$V_i - V_s - V_L = 0$$


$$I_S = \frac{V_S}{R_S}$$

$$I_S = I_z + I_L$$



EX:2

Repeat Ex.1 with $R_L = 3 K\Omega$

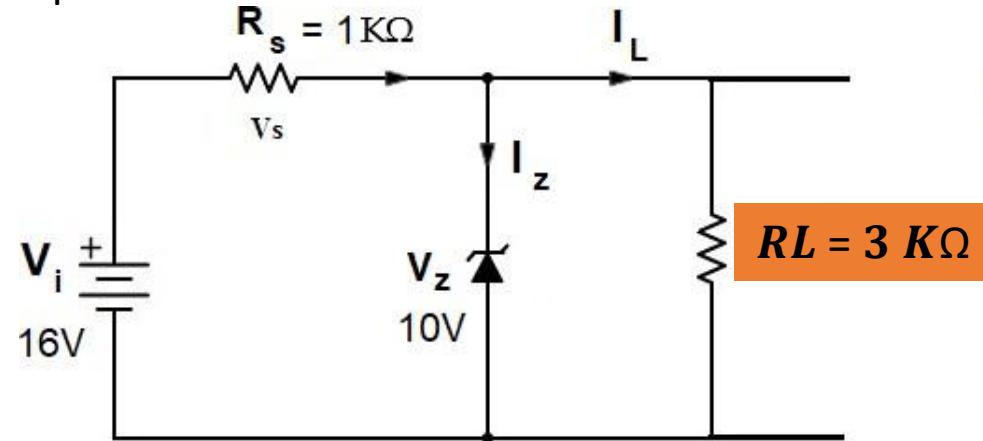

Sol:

i

$$V_L = \frac{R_L}{R_L + R_S} V_i \\ = \frac{3}{3 + 1} * 16 \\ V_L = 12V$$

$\because V_L(12V) > V_z(10V)$

Zener is on

$$\therefore V_z = V_L = 10V$$

iii

$$V_i - V_s - V_L = 0 \\ 16 - V_s - 10 = 0 \\ V_s = 16 - 10$$

$$V_s = 6V$$

v

$$I_S = I_Z + I_L \\ 6 = I_Z + 3.33 \\ I_Z = 2.67mA \\ I_S = 6mA$$

ii

$$I_L = \frac{V_L}{R_L} = \frac{10}{3 * 10^3}$$

$$I_L = 3.33mA$$


iv

$$I_S = \frac{V_S}{R_S}$$

$$I_S = \frac{6V}{1k}$$

$$I_S = 6mA$$

Stage 2: Fixed V_i and Variable R_L

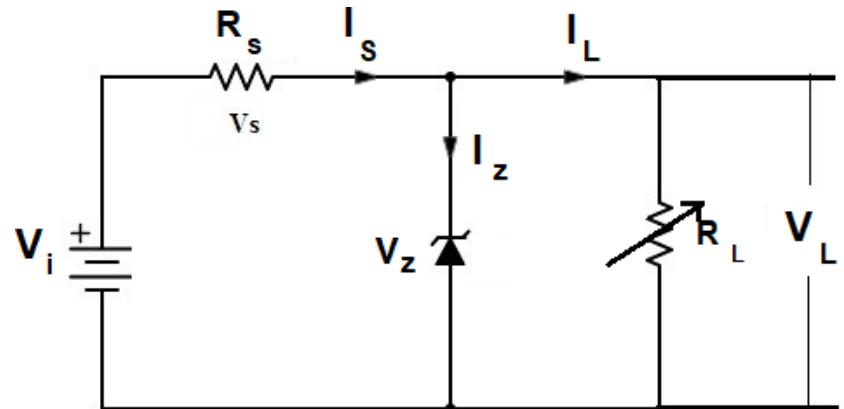

$$R_{Lmin} = \frac{V_z}{V_i - V_z} R_s$$

$$V_L = V_z$$

$$V_i - V_s - V_L = 0$$

$$I_s = \frac{V_s}{R_s}$$


$$I_{Lmin} = I_s - I_{Zmax}$$

$$R_{Lmax} = \frac{V_L}{I_{Lmin}}$$

$$I_{Lmax} = \frac{V_L}{R_{Lmin}}$$

EX:3

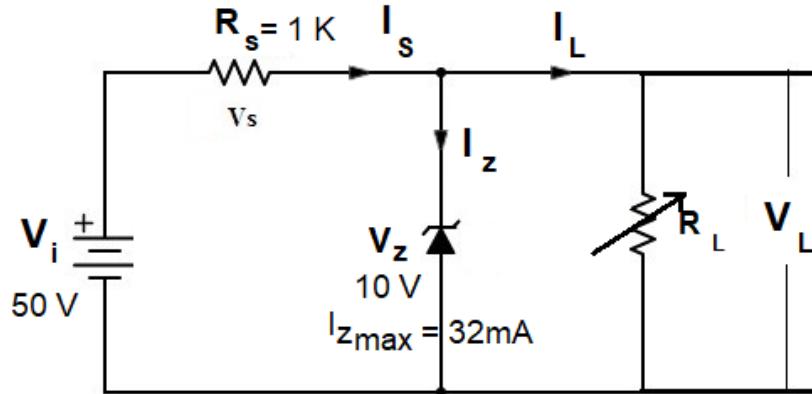For the Zener circuit below, determine the range of R_L and I_L



Sol:

i) $R_{Lmin} = \frac{V_z}{V_i - V_z} R_s$
 $= \frac{10}{50 - 10} * 1k$
 $R_{Lmin} = 0.25 k\Omega$

ii) $V_i - V_s - V_z = 0$
 $50 - V_s - 10 = 0$
 $V_s = 40V$


$I_s = \frac{V_s}{R_s} \rightarrow I_s = \frac{40}{1k}$
 $I_s = 40 mA$
 $I_{Lmin} = I_s - I_{Zmax}$
 $I_{Lmin} = 40mA - 32mA$

$I_{Lmin} = 8mA$

iii) $R_{Lmax} = \frac{V_z}{I_{Lmin}}$
 $R_{Lmax} = \frac{10}{8mA}$
 $R_{Lmax} = 1.25 k\Omega$

iv) $I_{Lmax} = \frac{V_L}{R_{Lmin}}$
 $I_{Lmax} = \frac{10}{0.25k}$
 $I_{Lmax} = 40 mA$

Stage 3: Variable V_i and Fixed RL

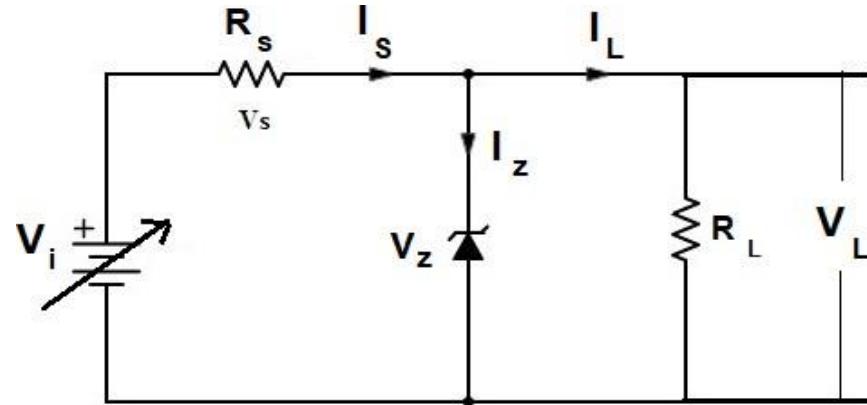

$$V_{i \min} = \frac{R_L + R_s}{R_L} V_Z$$

$$I_{S \max} = I_{Z \max} + I_L$$

$$V_{i \max} = I_{S \max} R_s + V_Z$$

$$V_{s \max} = I_{S \max} R_s$$

$$I_{S \min} = \frac{V_{i \min} - V_Z}{R_s}$$

$$V_{s \min} = I_{S \min} R_s$$

EX:4


Sol:

For the Following circuit, determine the range of the **input voltage** and V_s

i)
$$V_{i \min} = \frac{R_L + R_s}{R_L} V_Z$$

$$= \frac{1.2k + 220}{1.2k} * 20$$

$$V_{i \min} = 23.67 V$$

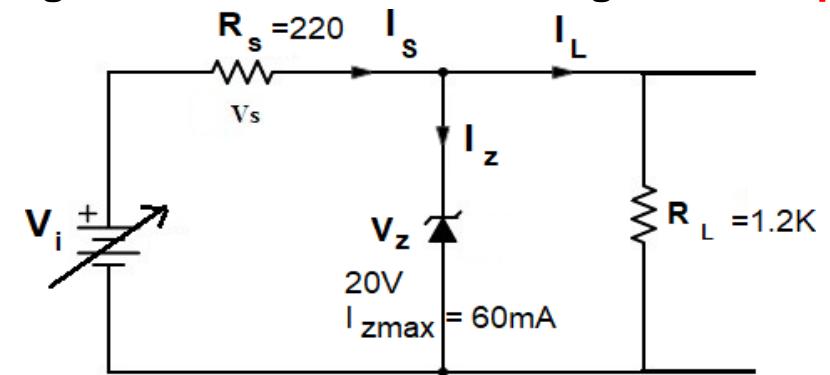

ii)
$$I_L = \frac{V_L}{R_L} \rightarrow = \frac{20}{1.2k}$$

$$I_L = 16.6 mA$$

$$I_{S \max} = I_{Z \max} + I_L$$

$$I_{S \max} = 60mA + 16.6mA$$

$$I_{S \max} = 76.6mA$$

$$V_{i \max} = I_{S \max} R_s + V_Z$$

$$V_{i \max} = (76.6mA)(220\Omega) + 20$$

$$V_{i \max} = 36.86 V$$

iii)
$$V_{s \max} = I_{S \max} R_s$$

$$V_{s \max} = (76.6mA)(220)$$

$$V_{s \max} = 16.852 V$$

IV)
$$I_{S \min} = \frac{V_{i \min} - V_Z}{R_s}$$

$$= \frac{23.67 - 20}{220}$$

$$= 16.68 mA$$

$$V_{s \min} = I_{S \min} R_s$$

$$V_{s \min} = (16.68 mA)(220\Omega)$$

$$V_{s \min} = 3.67 V$$