

1. The core building block in a modern FPGA from Xilinx is called a
 - a) **Logic cell (LC)**
 - b) Logic element (LE)
 - c) Logic block (LB)
 - d) Logic gate
2. In Xilinx, a logic cell (LC) comprises a
 - a) 2-input LUT and multiplexer
 - b) **4-input LUT, a multiplexer and a register**
 - c) Gates only
 - d) Registers only
3. The equivalent core building block in an FPGA from Altera is called a.....
 - a) Logic cell (LC)
 - b) **Logic element (LE)**
 - c) Logic block (LB)
 - d) Logic gate
4. A Xilinx slice contains.....
 - a) **Two logic cells**
 - b) Six logic cells
 - c) Four logic cells
 - d) Three logic cells
5. A Configurable logic block (CLB) in Xilinx contains.....
 - a) **Four slices**
 - b) Six slices
 - c) Ten slices
 - d) Eight slices
6. The LUTs within a single Configurable logic block (CLB) to be configured together to implement a shift register containing up to
 - a) 64 bits
 - b) 256 bits
 - c) **128 bits**
 - d) None of the above
7. FPGAs include relatively large chunks of embedded RAM called
 - a) e-RAM
 - b) block RAM
 - c) **A and B**
 - d) None of the above
8. Embedded RAM blocks can be used for a variety of purposes such as implementing
 - a) Single- or dual- port RAM
 - b) First-in first-out (FIFO) functions
 - c) State machines
 - d) **All of the above**
9. The main clock signal branches again and again in
 - a) **Clock tree**
 - b) Clock manager
 - c) Clock pin
 - d) Clock signal

10.generates a number of daughter clocks.
- a) Clock tree
 - b) **Clock manager**
 - c) Clock pin
 - d) Clock signal
11. Clock managers may also support
- a) Phase shift
 - b) Jitter removal
 - c) Frequency synthesis
 - d) **All of the above**
12. The operation when the clock manager is used to generate daughter clocks with frequencies that are derived by multiplying or dividing the original signal is called a.....
- a) Phase shifting
 - b) Jitter removal
 - c) **Frequency synthesis**
 - d) None of the above
13. The operation when the clock manager is used to generate daughter clocks that are phase shifted with respect to each other is called a.....
- a) **Phase shifting**
 - b) Jitter removal
 - c) Frequency synthesis
 - d) None of the above
14. contains the information that will be uploaded into the FPGA in order to program it to perform a specific function
- a) Block file
 - b) Erasing file
 - c) Injection file
 - d) **Configuration file**
15. Bits that are used to define the state of programmable logic elements directly are called
- a) Block data
 - b) **Configuration data**
 - c) Injection data
 - d) Erasing data
16. Instructions that tell the device what to do with the configuration data are called
- a) Block commands
 - b) Injection commands
 - c) **Configuration commands**
 - d) Erasing commands
17.declaration contains a list of all libraries to be used in the design. For example: ieee, std, work, etc.
- a) **library**
 - b) architecture
 - c) entity
 - d) package
18. Entity section in VHDL program, specifies
- a) How circuit behaves
 - b) **I/O pins of the circuits**

- c) List of libraries
d) All of the above

19.section in VHDL program, contains the VHDL code proper, which describes how the circuit should behave.

- a) library
b) **architecture**
c) entity
d) package

20. the ieee library contains several packages, including


- a) Std_logic_1164
b) Std_logic_signed
c) Std_logic_arith
d) **All of the above**

Q2: draw the equivalent logic circuit for the VHDL code shown below

1).

```
entity log_cct is
port ( a,b,c,d,e,:in bit;_y : out bit);
end log_cct;
architecture fin_logic of log_cct is
signal s1,s2,s3,s4: bit;
begin
s1 <= a or b;
s2 <= b nand c;
s3 <= d and e;
s4 <= s1 xor s2;
y <= s4 nor (not s3);
end fin_logic;
```


Sol:

 

2).

```
entity exam is
port ( a,b,c: IN bit; d: OUT bit);
end exam;
ARCHITECTURE behavior OF exam IS
signal x1,x2:bit;
begin
x1<= a and b;
x2<= x1 or not c;
d<= a nand x2;
end behavior;
```


Sol:

 

3).

```
entity mix_logic is
port (in1,in2,in3,in4,in5 : in bit;
      final : out bit);
end mix_logic;
architecture sec_logic of mix_logic is
signal w1,w2,w3 : bit;
begin
w1 <= in1 and in2;
w2 <= in3 or in4;
w3 <= in4 and (not in5);
final <= w1 or w2 or w3;
end sec_logic;
```


Sol:

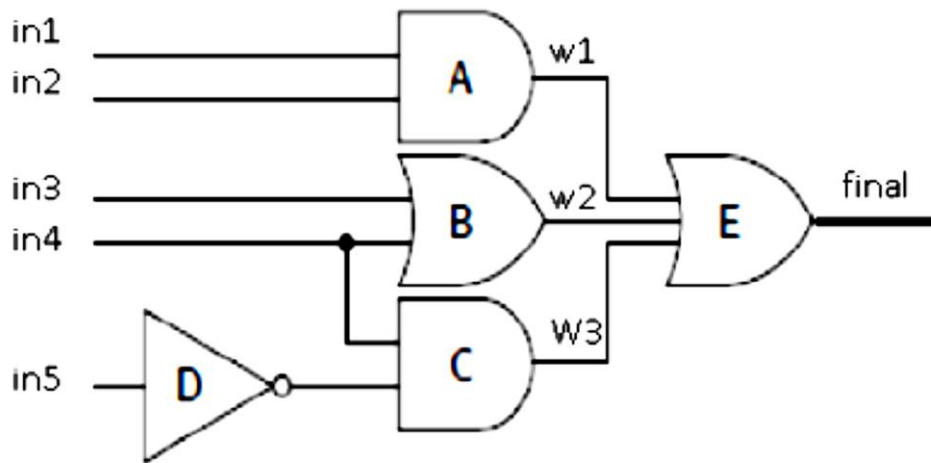

4).

```
entity cct1 is
port (x1,x2,x3,x4 : in bit;
      f,g : out bit);
end cct1;
architecture cct2 of cct1 is
signal sig1,sig2,sig3 , sig4: bit;
begin
sig1 <= x1 and x3;
sig2 <= x2 and x4 ;
sig3 <= x1 or (not x3);
sig4 <= x4 or ( not x2);
f <= sig1 or sig2;
g <= sig3 and sig4;
end cct2;
```

Sol:

 

5).

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity test1_s is
Port ( a,b,c : in STD_LOGIC;
d : out STD_LOGIC);
end test1_s;
architecture Behavioral of test1_s is
signal s1,s2,s3,s4:std_logic;
begin
s1<= (not a and b and c);
s2<= (not b and a and c) ;
s3<= (not c and a and b);
s4<= (a and b and c);
d<=( s1 or s2 or s3 or s4);
end Behavioral;
```

Sol:

