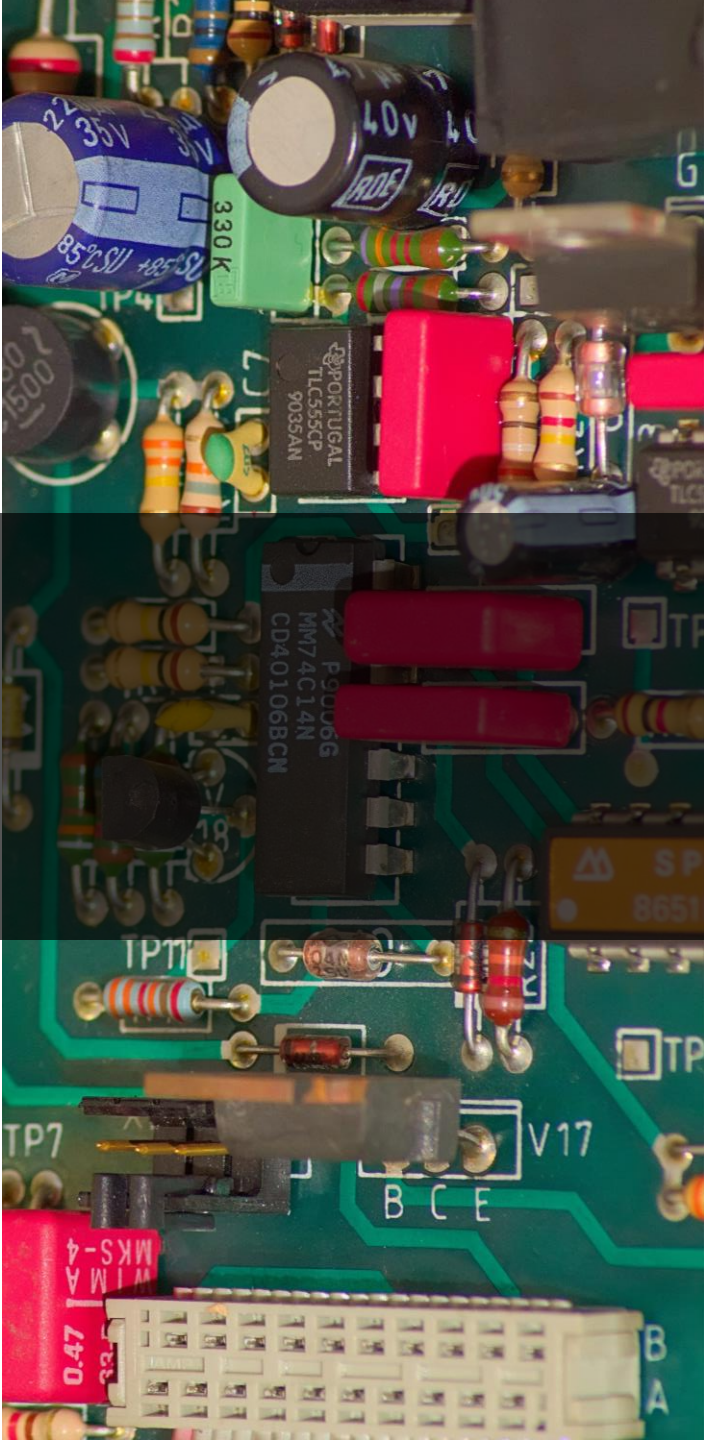





University of Al Maarif
Department of Medical Instruments
Techniques Engineering
Class: 2nd



Digital Electronics
MIET2203
Lecture 3: Logic gates

Lecturer: Mohammed Jabal
2024 - 2025


Objective

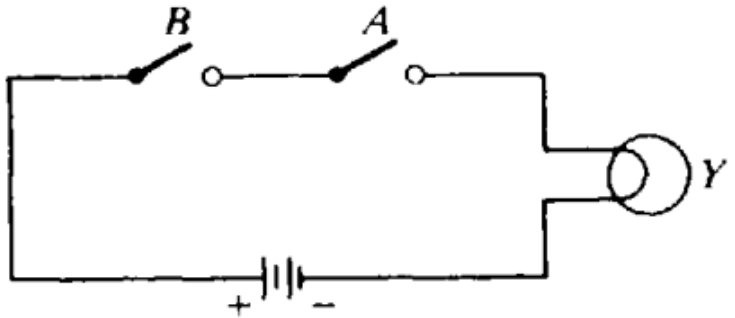

(a) AND circuit using switches

Input switches		Output light
<i>B</i>	<i>A</i>	<i>Y</i>
open	open	no
open	closed	no
closed	open	no
closed	closed	yes

(b) Truth table

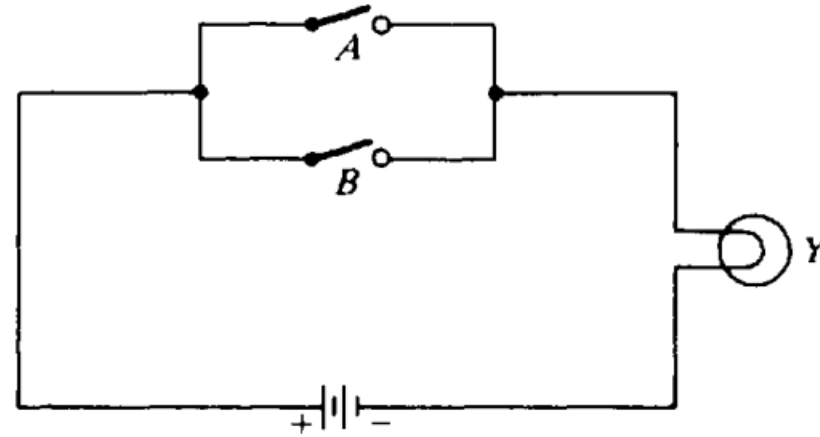

(a) OR circuit using switches

Input switches		Output light
<i>B</i>	<i>A</i>	<i>Y</i>
open	open	no
open	closed	yes
closed	open	yes
closed	closed	yes

(b) Truth table

1. AND gate

- The **AND** gate is an electronic circuit that gives a **high** output (1) only if **all its inputs are high**. A dot (.) is used to show the AND operation i.e. (A.B). Bear in mind that this dot is sometimes omitted i.e. AB

$$X = (A.B)$$

- $N = 2^n$

where N is the number of possible input combinations and n is the number of input variables. To illustrate,

For two input variables: $N = 2^2 = 4$ combinations

For three input variables: $N = 2^3 = 8$ combinations



Truth table for a 2-input AND gate.

Inputs		Output
A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

1 = HIGH, 0 = LOW

1. AND gate

EXAMPLE 3-2

TABLE 3-3

Inputs			Output
A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

(a) Develop the truth table for a 3-input AND gate.

(b) Determine the total number of possible input combinations for a 4-input AND gate.

Solution

(a) There are eight possible input combinations ($2^3 = 8$) for a 3-input AND gate. The input side of the truth table (Table 3-3) shows all eight combinations of three bits. The output side is all 0s except when all three input bits are 1s.


(b) $N = 2^4 = 16$. There are 16 possible combinations of input bits for a 4-input AND gate.

Related Problem

Develop the truth table for a 4-input AND gate.

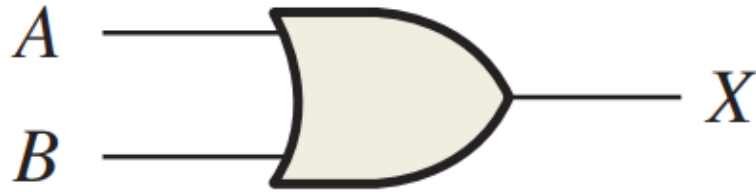2. OR gate

- The **OR** gate is an electronic circuit that gives a **high** output (1) if **one or more of its inputs are high**. A plus (+) is used to show the OR operation.



$$X = (A + B)$$


Truth table for a 2-input OR gate.

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	1
1	0	1
1	1	1

1 = HIGH, 0 = LOW

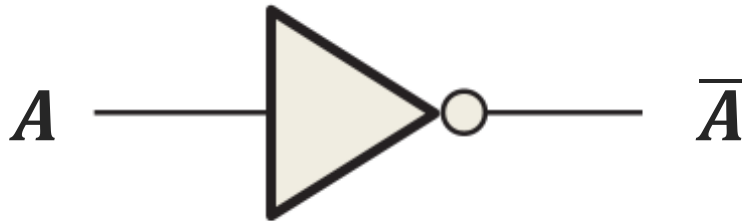3. NOT gate

- The **NOT** gate is an electronic circuit that produces an **inverted version** of the input at its output. It is also known as an **inverter**. If the input variable is A , the inverted output is known as **NOT A** . This is also shown as A' , or A with a bar over the top.



Inverter truth table.

Input	Output
LOW (0)	HIGH (1)
HIGH (1)	LOW (0)



3. NOT gate

- The diagrams below show two ways that the **NAND** logic gate can be configured to produce a **NOT** gate. It can also be done using **NOR** logic gates in the same way.



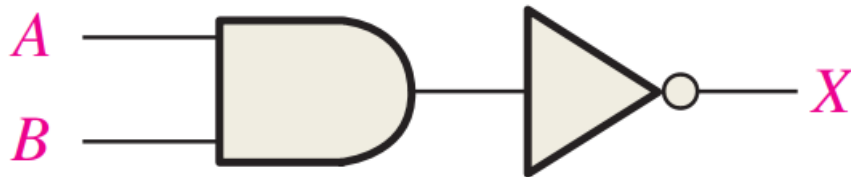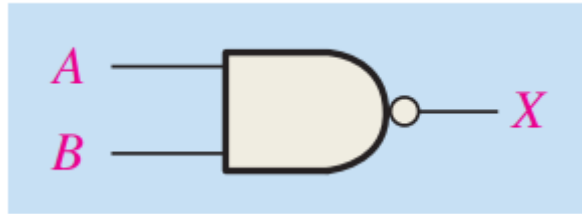4. NAND gate

- This is a **NOT-AND** gate which is equal to an **AND** gate followed by a **NOT** gate. The outputs of all **NAND** gates are **high** if any **of the inputs are low**. The symbol is an AND gate with a small circle on the output. The small circle represents inversion.



$$X = (\overline{A \cdot B})$$



Truth table for a 2-input NAND gate.

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	1
0	1	1
1	0	1
1	1	0

1 = HIGH, 0 = LOW.

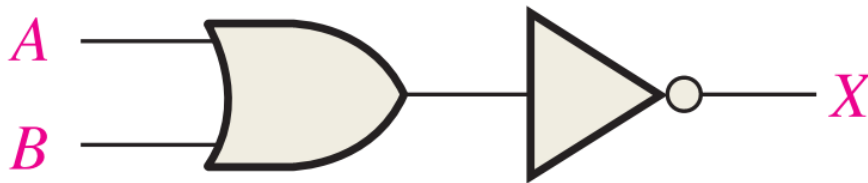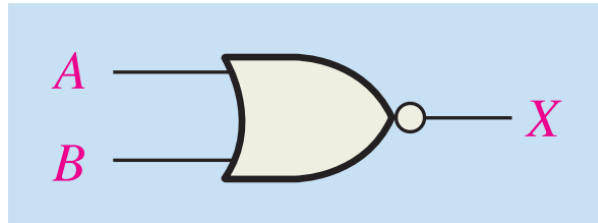5. NOR gate

- This is a **NOT-OR** gate which is equal to an **OR** gate followed by a **NOT** gate. The outputs of all **NOR** gates are **low** if any of the inputs are **high**. The symbol is an **OR** gate with a small circle on the output. The small circle represents inversion.



$$X = \overline{(A + B)}$$


Truth table for a 2-input NOR gate.

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	1
0	1	0
1	0	0
1	1	0

1 = HIGH, 0 = LOW.

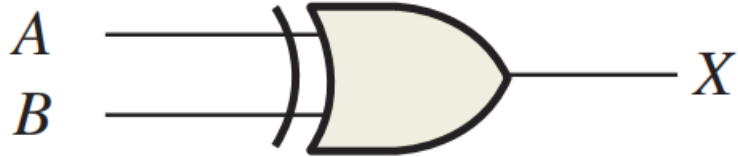6. EX-OR gate

- The '**Exclusive-OR**' gate is a circuit which will give a **high** output if either, but not both, **of its two inputs are high**. An encircled plus sign $\oplus$ is used to show the EX-OR operation.




$$X = (A \oplus B)$$

Truth table for an exclusive-OR gate.

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	1
1	0	1
1	1	0

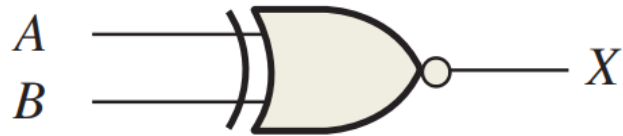7. EX-NOR gate

- The '**Exclusive-NOR**' gate circuit does the opposite to the **Ex-OR** gate. It will give a **low** output if either, but not both, of its two inputs are **high**. The symbol is an EXOR gate with a small circle on the output. The small circle represents inversion.



$$X = \overline{(A \oplus B)}$$

Truth table for an exclusive-NOR gate.

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	1
0	1	0
1	0	0
1	1	1

Timing diagram

- A **timing diagram** is basically a **graph** that **accurately** displays the relationship of two or more waveforms with **respect** to each other on a **time basis**.

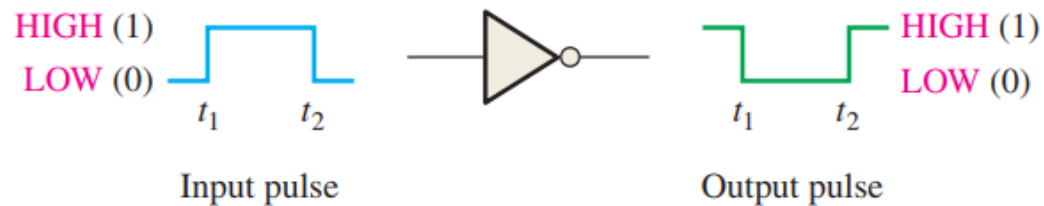


FIGURE 3-2 Inverter operation with a pulse input.


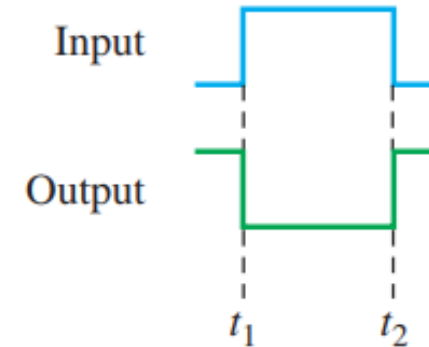


FIGURE 3-3 Timing diagram for the case in Figure 3-2.

Timing diagram

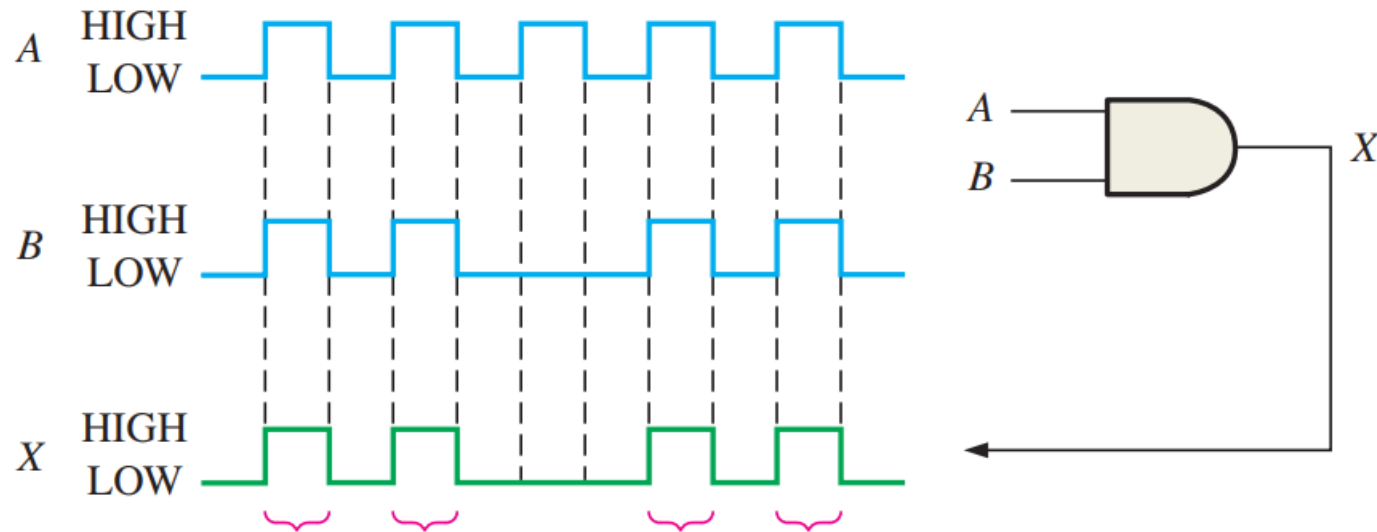EXAMPLE 3-3

If two waveforms, *A* and *B*, are applied to the AND gate inputs as in Figure 3-11, what is the resulting output waveform?




A and *B* are both HIGH during these four time intervals; therefore, *X* is HIGH.

FIGURE 3-11

Timing diagram

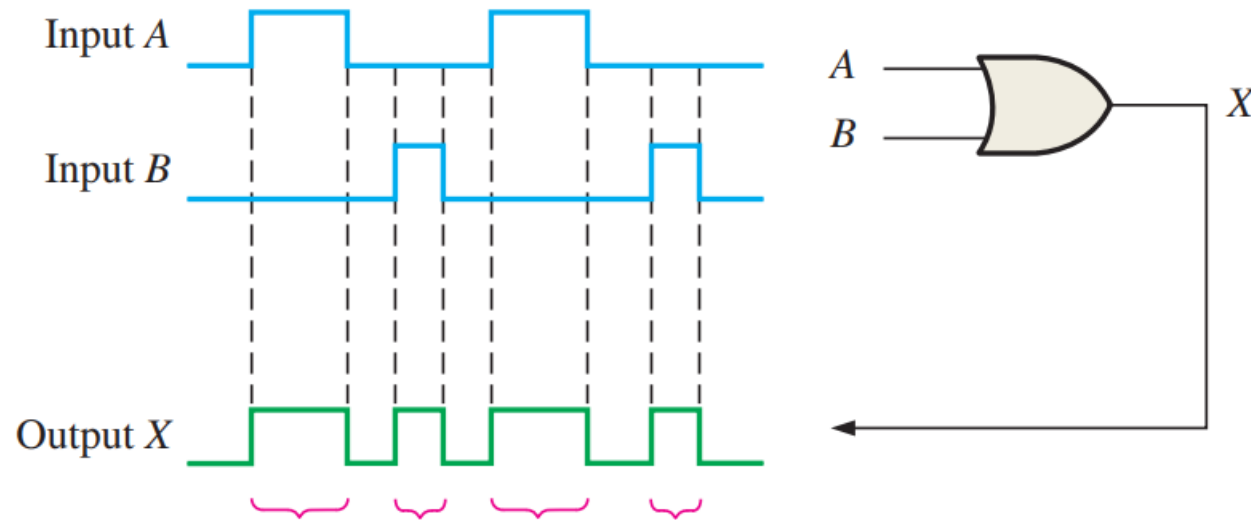EXAMPLE 3-7

If the two input waveforms, *A* and *B*, in Figure 3–21 are applied to the OR gate, what is the resulting output waveform?



When either input or both inputs are HIGH,
the output is HIGH.

FIGURE 3-21

Timing diagram

EXAMPLE 3-11

Show the output waveform for the 3-input NAND gate in Figure 3-29 with its proper time relationship to the inputs.


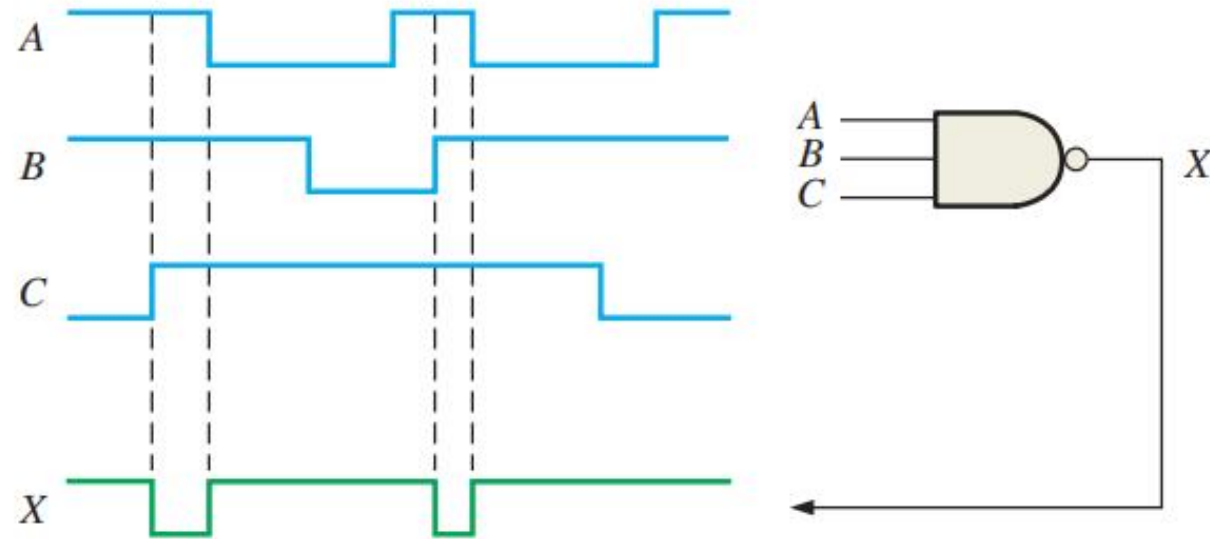



FIGURE 3-29

Describing logic circuits algebraically

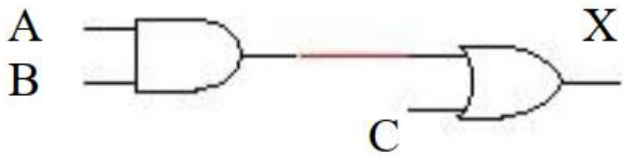
- Any **logic circuit**, no matter how **complex**, may be completely described using the **Boolean** operations previously defined. Determine the output expression for the logic shown below :-



$$X = A.B + C$$

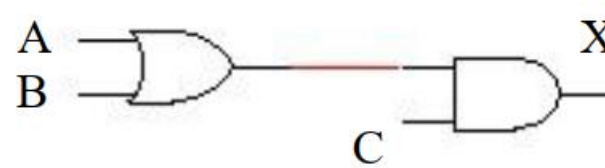

$$X = (A+B).C$$

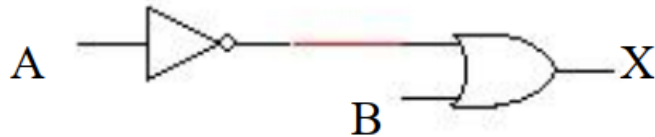

$$X = \bar{A} + B$$




$$X = \overline{A + B}$$

Implementing circuits from Boolean expressions

- If the operation of a circuit is defined by a **Boolean** expression, a **logic circuit** can be implemented directly from that **expression**.


Implement the logic circuits defined by the following Boolean expressions :

a) $Y = AC + B\bar{C} + \bar{A}BC$

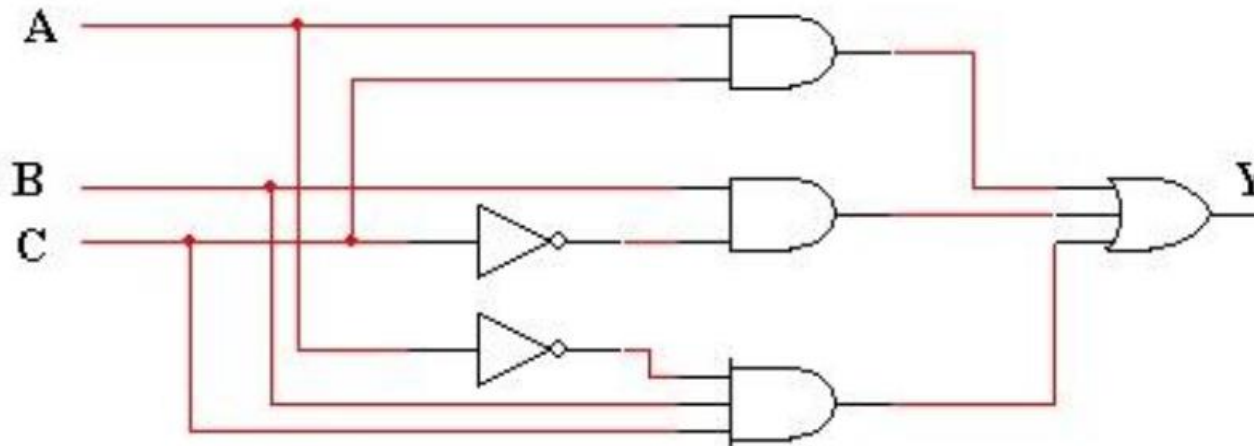


Implementing circuits from Boolean expressions

b) $X = AB + \bar{B}C$

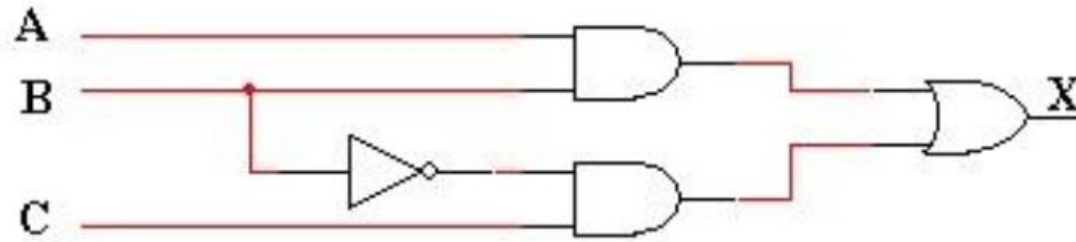

Exercise:

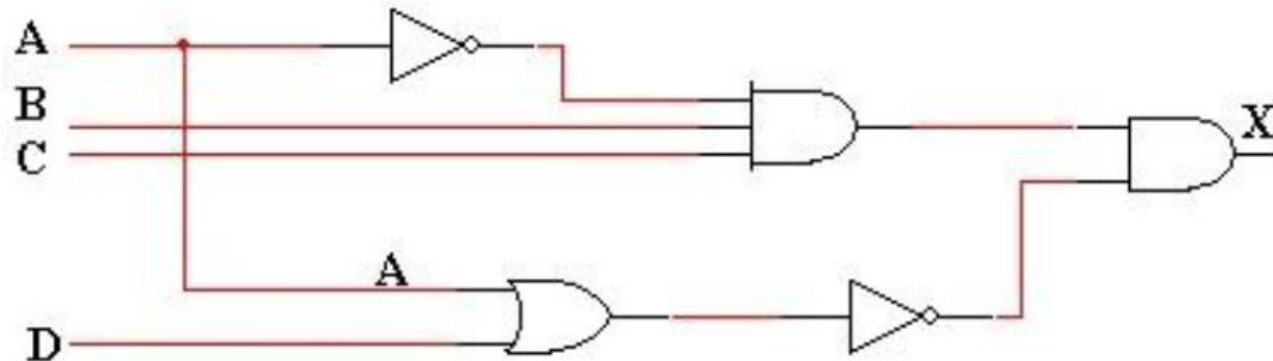- a) determine the output expression for the following circuit
- b) determine the output logic level if $A=1$, $B=0$ and $C=1$, $D=1$



References

[1] Digital fundamentals / Thomas L. Floyd. —Eleventh edition.

[2]